
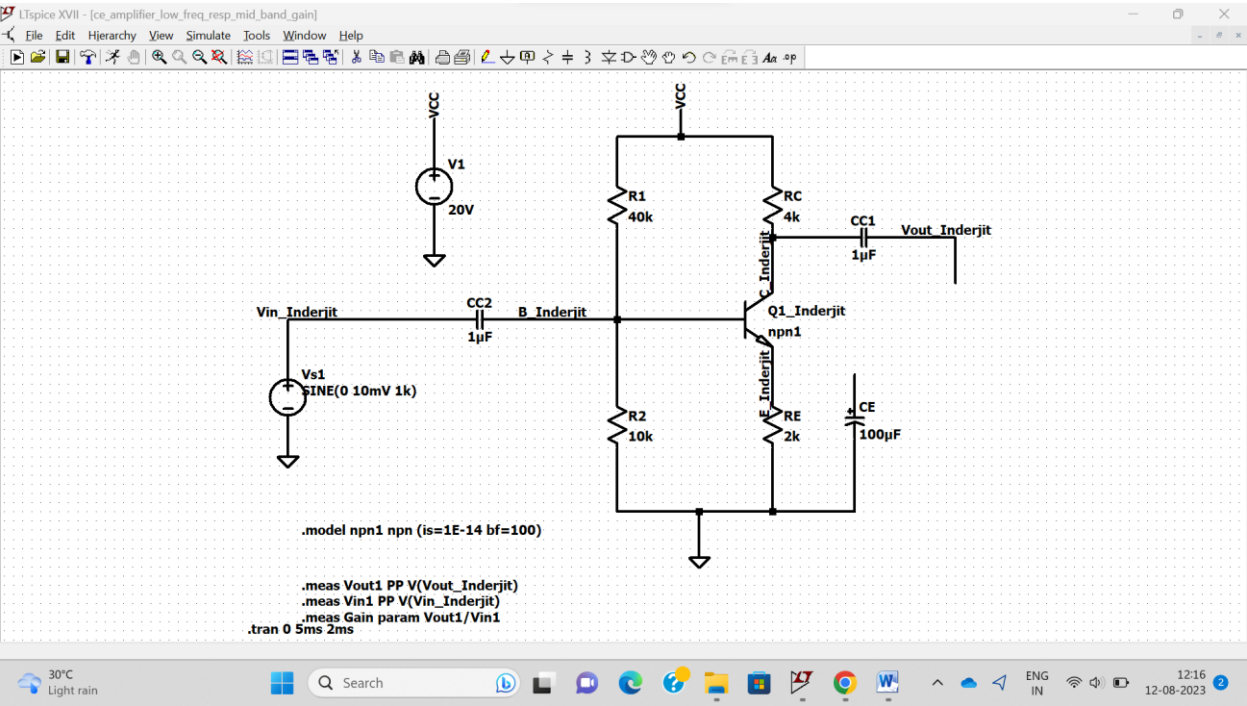


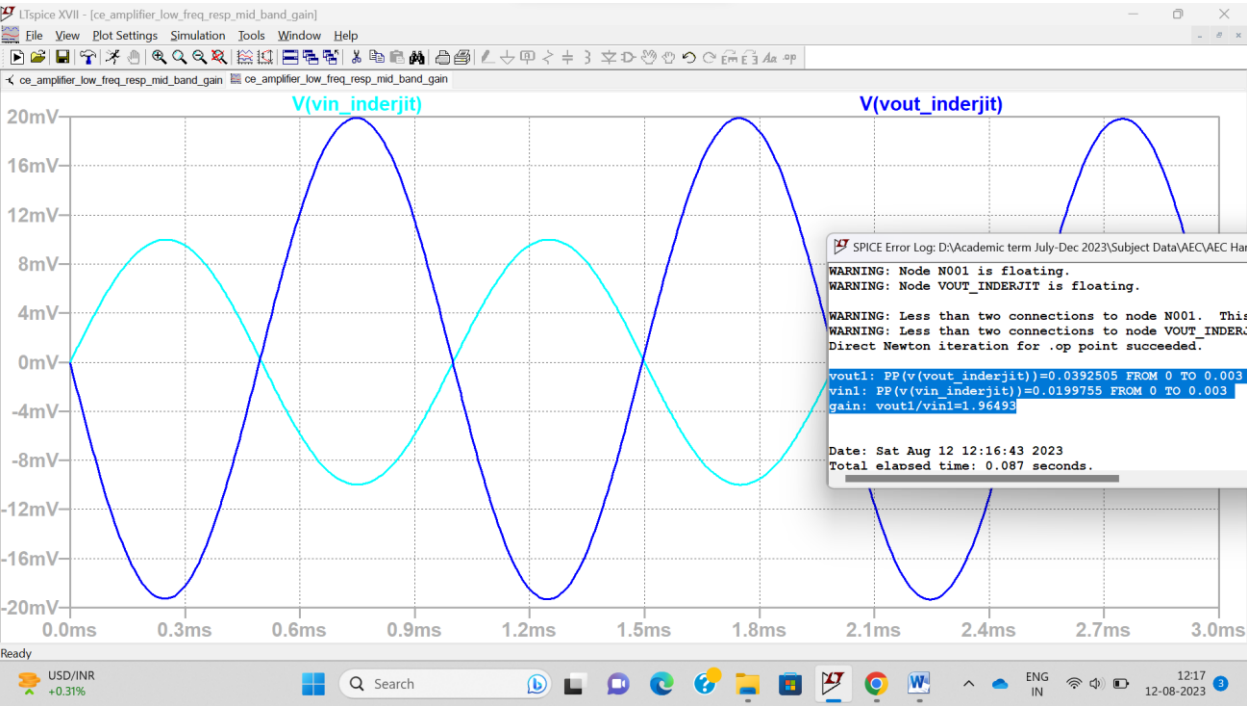
CE amplifier (numerical 12 simulation Results)



AV without CE




AV with CE connected

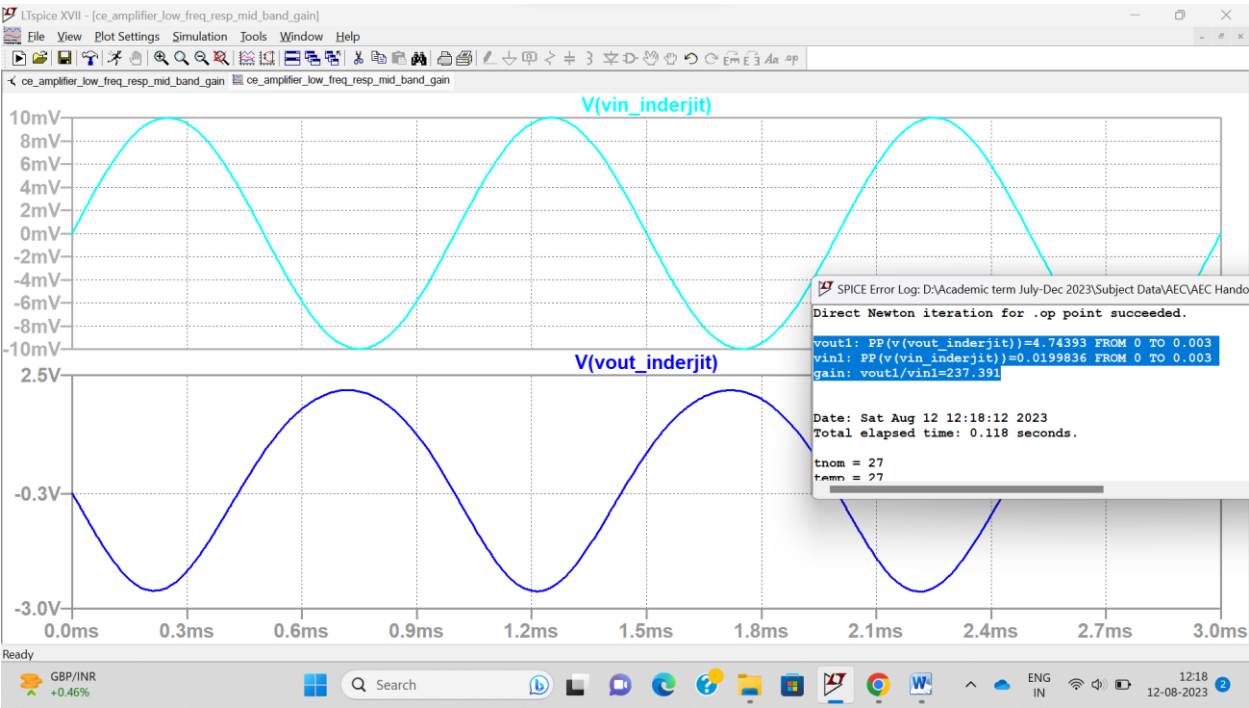

3] Common Base amplifier (npn BJT) :-

26

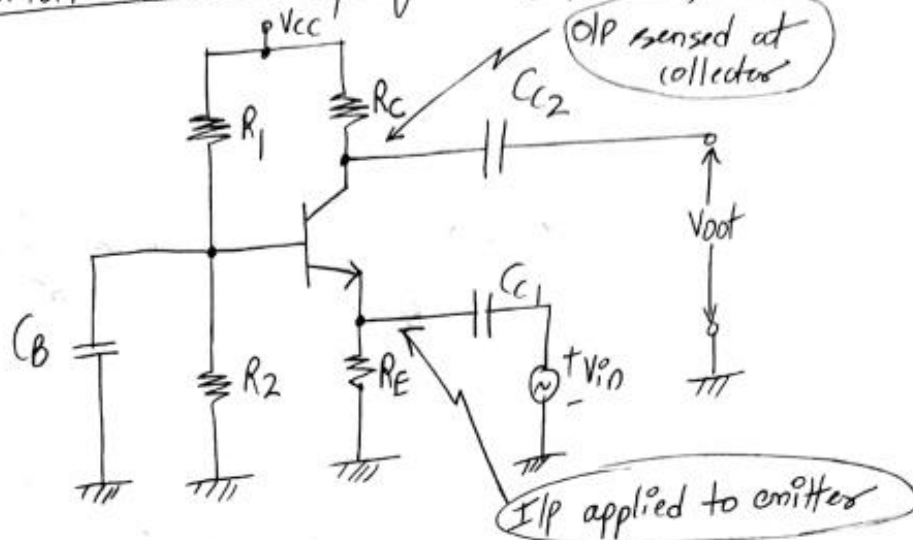

let say's, V_{in} ↑ s.e.s i.e. V_E ↑ s.e.s (as $V_E + V_{in}$ is at E terminal)
(DC) (AC)

V_B is a constant, as C_B blocks DC value
(DC)

i.e. $V_{BE} = (V_B - V_E) \downarrow$ s.e.s $\rightarrow I_B \downarrow$ s.e.s

$I_C = \beta I_B$; if $I_B \downarrow$ s.e.s $\rightarrow I_C \downarrow$ s.e.s


Also, $V_C = V_{CC} - I_C R_C$ i.e. If $I_C \downarrow$ s.e.s $\rightarrow V_C \downarrow$ s.e.s
i.e. $V_{out} \downarrow$ s.e.s

In summary, As $V_{in} \uparrow$ s.e.s $\rightarrow V_E \uparrow$ s.e.s $\rightarrow V_B$ constant $\rightarrow V_{BE} \downarrow$ s.e.s
 $(\text{i.e. } V_{out} \uparrow \text{ s.e.s} \leftarrow V_C \uparrow \text{ s.e.s} \leftarrow I_C \downarrow \text{ s.e.s} \leftarrow I_B \downarrow \text{ s.e.s})$

i.e. I/P & O/P signal in a CB amplifier are in phase with each other.

DERIVATION OF RIN and ROUT for Common Base amplifier:


AC Analysis:-

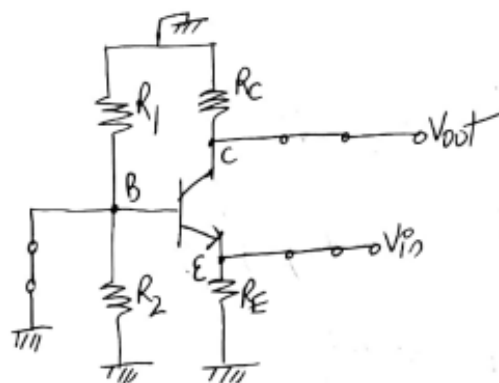

27


Assume
 $V_A = \infty$
 $i_c \approx i_e$

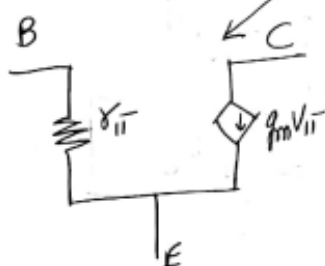Next, we replace BJT by its small-signal hybrid model,



Small-signal voltage gain: $A_v = \frac{V_{out}}{V_{in}}$

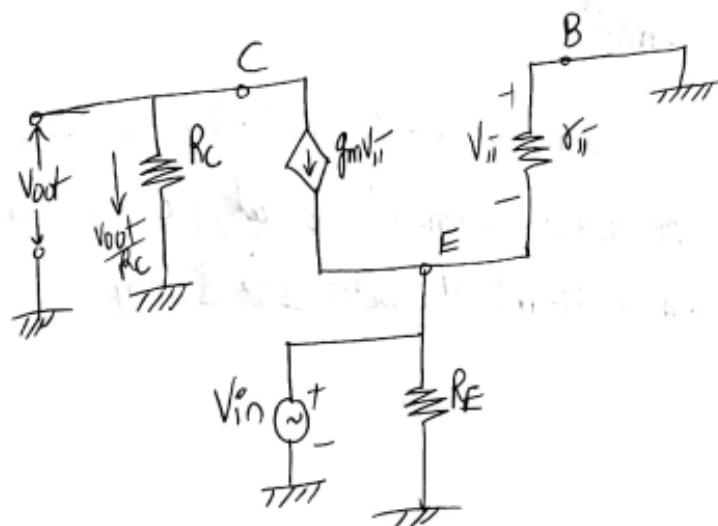we interchange B & C terminals for simplicity



ckt (b) : Small-sig equivalent ckt of CB amplifier

From ckt(b), $V_{ii} = -V_{in}$

KCL at 'c' node, gives

$$g_m V_{ii} + \frac{V_{out}}{R_c} = 0$$

$$\text{i.e. } -g_m V_{in} = -\frac{V_{out}}{R_c}$$


$$\text{i.e. } \frac{V_{out}}{V_{in}} = g_m R_c$$

$$\text{i.e. } \boxed{A_v = +g_m R_c} \quad \text{----- Small-sig voltage gain}$$

→ The +ve sign in gain formula indicates no phase difference betn the input and o/p signals. in a Common Base amplifier

→ It is called "Common-base" amplifier since, in AC analysis, the base terminal is at ac ground & act as common terminal betn I/P & o/p.


Input impedance: Z_i

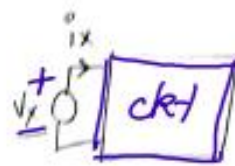

$$R_{in} = \frac{v_x}{i_x} \quad 29$$

$$Z_i = \frac{v_x}{i_x}$$

Redrawing ckt(b),

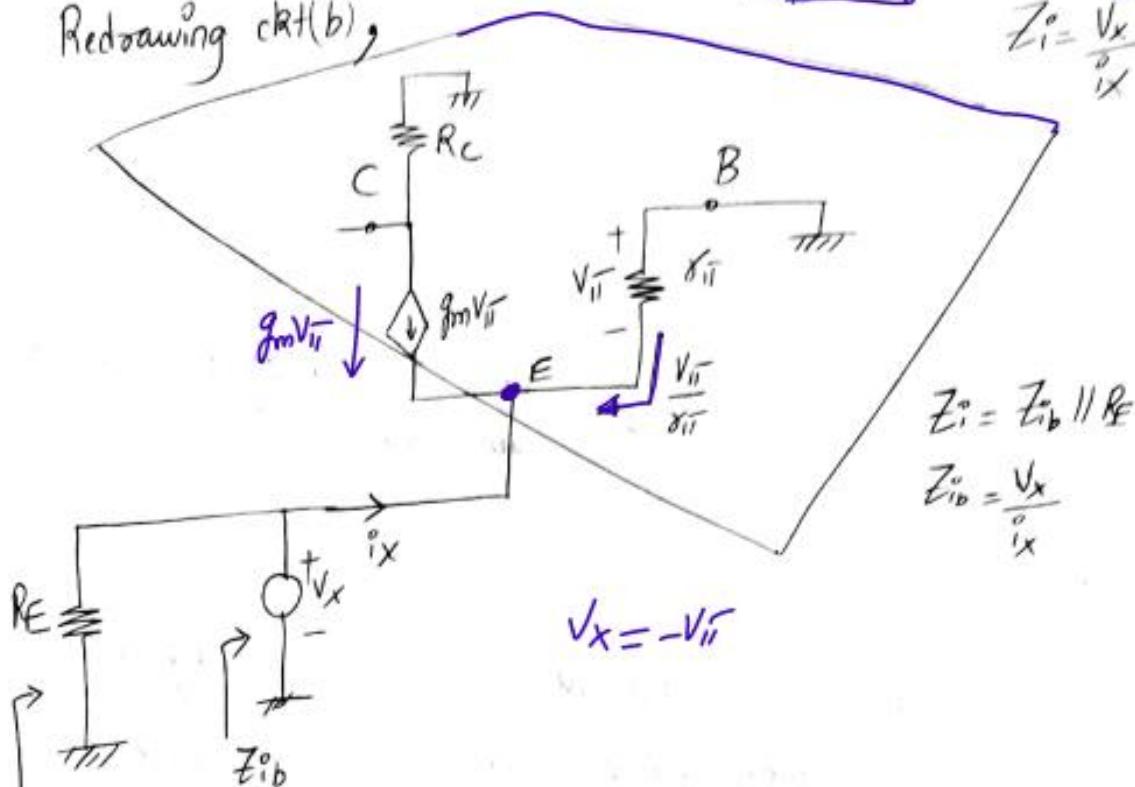

$$Z_i = Z_{ib} \parallel R_E$$

$$Z_{ib} = \frac{v_x}{i_x}$$

$$v_x = -v_{\pi}$$

From above ckt, $\frac{v_{\pi}}{i_x} = -v_x$

KCL at 'E' node, gives

$$\rightarrow i_x + g_m v_{\pi} + \frac{v_{\pi}}{r_{\pi}} = 0$$

$$i_x = -v_{\pi} \left(g_m + \frac{1}{r_{\pi}} \right)$$

$$i_x = v_x \left(1 + \frac{g_m r_{\pi}}{1} \right) \beta$$

$$i_x = v_x \left(\frac{1 + \beta}{r_{\pi}} \right)$$

$$r_{\pi} = \frac{\beta}{g_m}$$

$$g_m r_{\pi} = \beta$$

$$1 + \beta = \beta$$

$$\frac{\beta}{r_{\pi}} = g_m$$

$$i_x = V_x \left(\frac{\beta}{r_{\pi}} \right)$$

$$g_m = \frac{\beta}{r_{\pi}}$$

50

$$i_x = V_x g_m$$


$$\frac{V_x}{i_x} = \frac{1}{g_m}$$

Now, $Z_o = \frac{1}{g_m} \parallel R_E$
 or $R_{in} = \frac{1}{g_m} \parallel R_E$

Low I/P impedance in CB amplifier

Application :

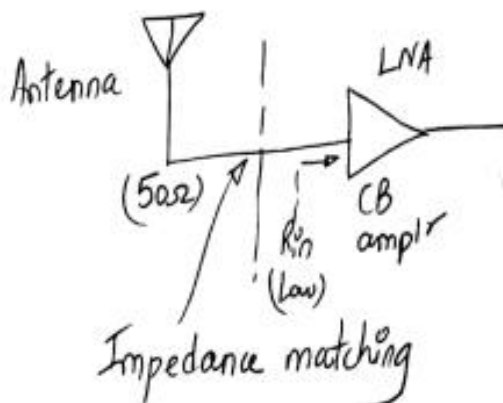↳ CB amplifier is used to be driven by a low impedance source such as an antenna.



which is also of low impedance of around 50Ω


O/p impedance: Z_o or out

31




Redrawing ckt (b) by making $V_{in} = 0$

$$Z_o = \frac{V_x}{i_x}$$

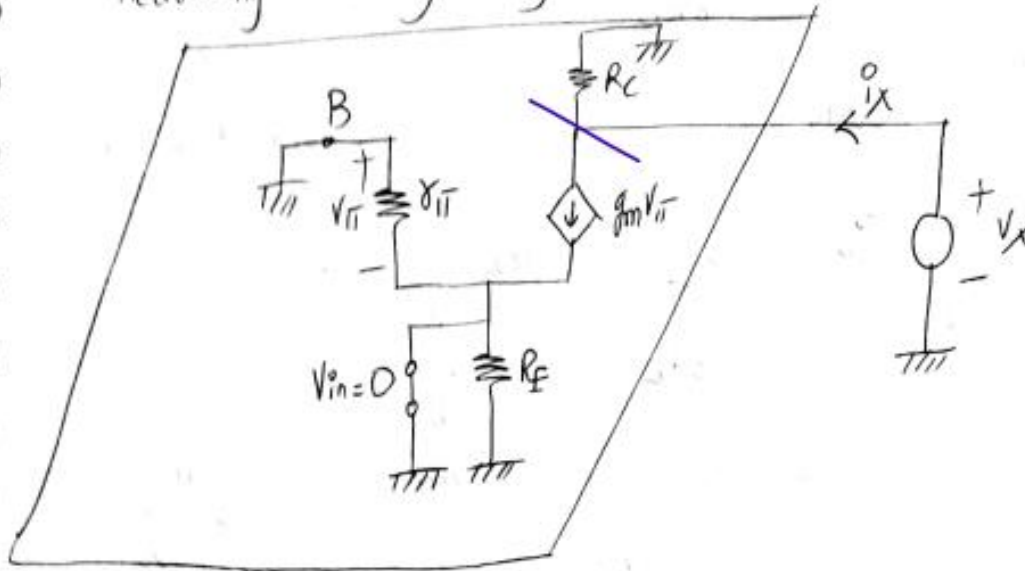

Since, $V_{in} = 0$ & $V_{BE} = -V_{in} = 0$

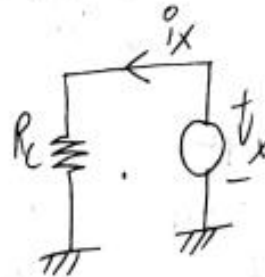i.e. $g_m V_{BE} = 0$ i.e. current source ($g_m V_{BE}$) is open-circuited
ckt reduces to



Root = $Z_o = \frac{V_x}{i_x} = R_C$

--- o/p impedance of CB ampl