

AEC 12.2 9/2/22

f_T : Unity-gain frequency/Bandwidth of MOSFET

- Transition frequency
- Definition: f_T is the frequency at which the short circuit current gain of MOSFET becomes unity (0dB)
- f_T is figure of merit for high frequency operation of MOSFET

Q. Is current gain possible in MOSFET?

- Yes, since now at extremely high frequencies, input impedance of MOSFET is not infinite
- It is finite due to the presence of parasitic capacitances C_{gs} and C_{gd}
- Thus, at high-frequencies, current gain of MOSFET is defined

So far, we have considered zero gate current for a MOSFET, because of very high resistance between gate and source terminals



$$X_C = \frac{1}{s(C_{gs} + C_{gd})}$$

$$X_{in} = \frac{1}{j\omega(C_{gs} + C_{gd})}$$
 At high ω value $\rightarrow X_{in}$ is finite

* f_T definition for MOSFET:

- The unity-gain frequency or bandwidth is a figure of merit for the MOSFET
- Next, we draw equivalent high frequency model for MOSFET



- Since the input impedance is no longer infinite at high frequency, we can define the short-circuit current gain

KCL at node G, gives

$$I_i = I_1 + I_2$$
 i.e. $I_1 = \frac{V_{gs}}{1/sC_{gs}} + \frac{V_{gs}}{1/sC_{gd}} = V_{gs}(sC_{gs} + sC_{gd})$
 i.e. $I_1 = V_{gs}(C_{gs} + C_{gd})s$ — (1.1)

KCL at node D, gives

$$I_2 + I_d = g_m V_{gs}$$
 i.e. $\frac{V_{gs}}{1/sC_{gd}} + I_d = g_m V_{gs}$
 i.e. $V_{gs}(g_m - sC_{gd}) = I_d$ — (1.2)

Short-circuit current gain A_i^* is

$$A_i^* = \frac{I_d}{I_i}$$
 i.e. $A_i^* = \frac{V_{gs}(g_m - sC_{gd})}{sV_{gs}(C_{gs} + C_{gd})} = \frac{g_m - sC_{gd}}{s(C_{gs} + C_{gd})}$

For physical frequencies, $s = j\omega$

$$A_i^* = \frac{g_m - j\omega C_{gd}}{j\omega(C_{gs} + C_{gd})}$$
 — (1.3)


Recalling that C_{gd} is small at the frequencies of interest

Typical values $\rightarrow g_m = \frac{1mA}{V}$, $C_{gd} = 10fF$
 $f = 1GHz$
 $\omega C_{gd} = 2\pi f C_{gd} = 0.628 \times 10^{-3}$
 i.e. $g_m \gg \omega C_{gd} \rightarrow g_m - \omega C_{gd} \approx g_m$

⑤ $|A_i| \approx \frac{g_m}{j2\pi f(C_{gs} + C_{gd})}$

⑥ At $f = f_T$, we have $|A_i| = 1$ (f_T is defined as the frequency at which the magnitude of the short circuit current gain goes to 1)

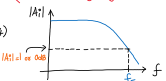i.e. $1 \approx \frac{g_m}{2\pi f_T(C_{gs} + C_{gd})}$
 i.e. $f_T \approx \frac{g_m}{2\pi(C_{gs} + C_{gd})}$ — (1.4)



⑩ Observation :-

- f_T is a parameter of the transistor, usually given in the datasheet.
- f_T is independent of the circuit
- $f_T \propto g_m$; $f_T \propto \frac{1}{C_{gs} + C_{gd}}$
- C_{gs} and C_{gd} limits the bandwidth
- Typical values, $f_T = 100MHz$ (For older technology, 5nm CMOS process)
 $f_T = 5-10GHz$ (For high-speed circuits, 0.13 μm CMOS process)

Numerical:

Consider an n-channel MOSFET with parameters $k_n = 0.2mA/V^2$, $V_{th} = 1V$, $\lambda = 0$, $C_{gd} = 0.02pF$, $C_{gs} = 0.25pF$. Assume the transistor is biased at $I_D = 0.4mA$. Calculate the unity-gain bandwidth of the MOSFET

Solution:

$$g_m = 2k_n(V_{GS} - V_{th})$$

$$g_m = 2 \times 0.2mA/V^2 \times 0.2V = 0.08mA/V$$

$$f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})} = \frac{0.08mA/V}{2\pi(0.25pF + 0.02pF)}$$

$$f_T = 833.46MHz$$