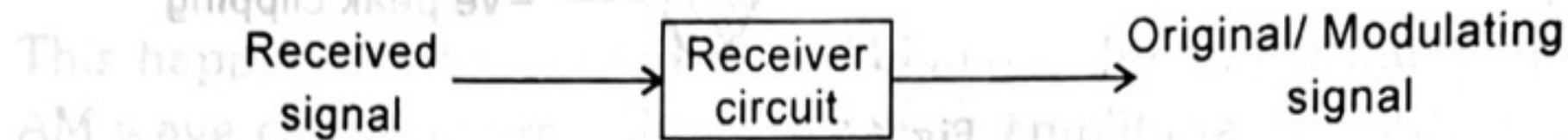


The main function of the receiver is to regenerate the original signal from the received signal.



According to our syllabus, we have to study two receiver circuits :

(i) TRF Receiver

(ii) SHR Receiver

7.1 Tuned Radio Frequency (TRF) Receiver

Q. *Sketch the block diagram of a TRF radio receiver and briefly describe its working. Explain its predominant disadvantages.*

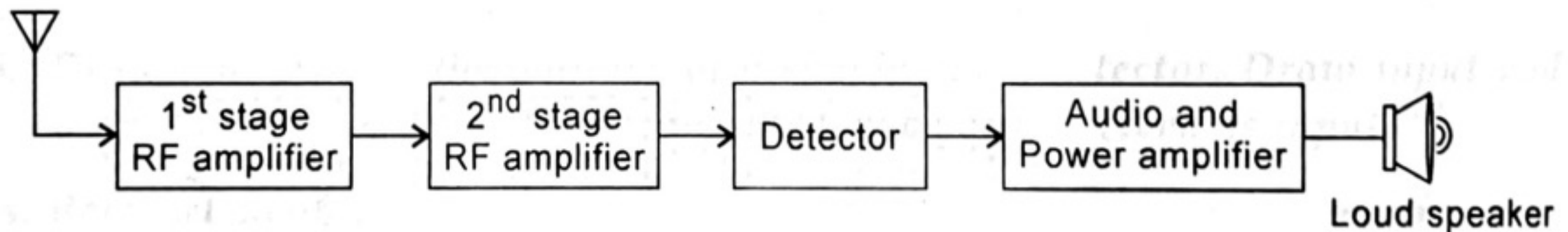


Fig. 7.1

Working

Figure 7.1 shows the block diagram of TRF receiver. The functions of different blocks are

(i) RF Amplifier

- Two or three RF amplifiers are used to select the desired frequency signal and reject all other frequencies.
- Also after selecting the signal, the signal is amplified.

(ii) Detector

- It consists of the detector circuit.
- Original signal is detected here.

(iii) Audio and Power Amplifier

- Used to amplify the detected signal.

Advantages

- Simple in design.

Disadvantages

(i) Instability

- The overall gain of RF amplifiers is extremely high.
- So, a small feedback from the output can make the RF amplifier work as an oscillator.

(ii) Variation in Bandwidth

- For better selectivity, the bandwidth of the receiver should always remain constant. But, in TRF bandwidth changes with the incoming frequency.

Note : Selectivity is a characteristic of a receiver covered in the later part of this chapter.

- Normally, bandwidth, $B.W. = \frac{f_r}{Q}$

f_r = Frequency of received signal

B.W = Bandwidth

Q = Quality factor of the circuit

Now, Q is constant.


Thus, when the frequency of received signal changes, the bandwidth also changes. This drawback is overcome in SHR with the concept of intermediate frequency.

(iii) Poor Selectivity

- As bandwidth varies with the variation in incoming frequency the selectivity degrades.

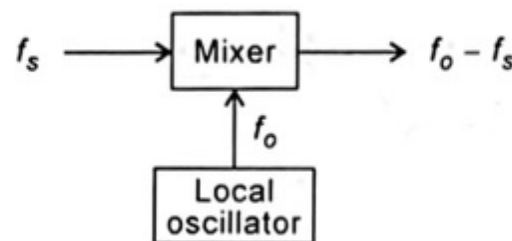
7.2 Concept of Intermediate Frequency in SHR Receiver

- The main drawback of TRF receiver is its variation in BW due to variation in frequency.
- SHR overcomes this drawback by converting every received signal frequency to a constant intermediate frequency called the *IF frequency* or (f_i).
- This is done with the help of a local oscillator and a mixer.
- Local oscillator* is a circuit which is used to generate signals of a particular frequency.
- Mixer*



Mixer just gives the difference of the two input frequencies.

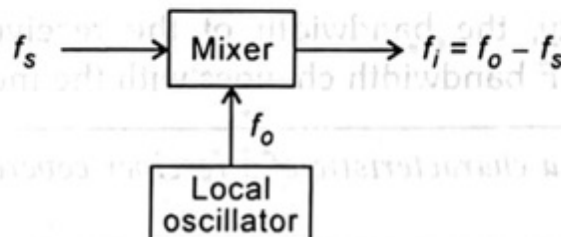7.2.1 How Does Local Oscillator and Mixer Work



f_s = Incoming frequency

f_o = Oscillator frequency

f_i = Intermediate frequency

- Our main aim is to keep the output i.e. f_i at a constant value.

Working

- As f_s changes, if f_o is also changed then, the difference will be constant.
- Hence, f_o is always changed with f_s using ganged tuning.

Note : The mixer circuit in practice gives many frequencies at its output but only the difference frequency is selected for the next stages.

