

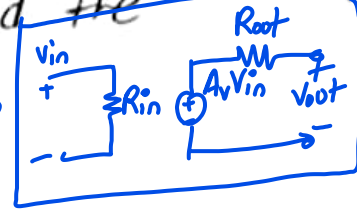


Objective: To find the closed-loop gain and the closed-loop input & o/p impedances

v. important

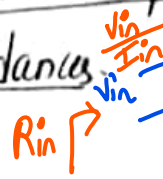

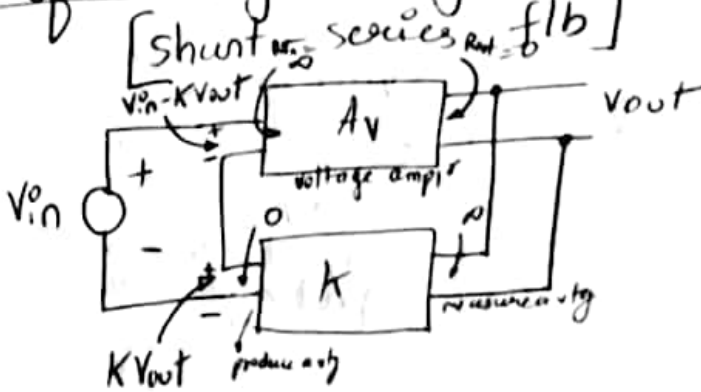
Analysis of Voltage-Voltage feedback :- (Voltage-series) topology



open loop gain = A_v

closed loop gain = $\frac{V_{out}}{V_{in}}$

General f/b system

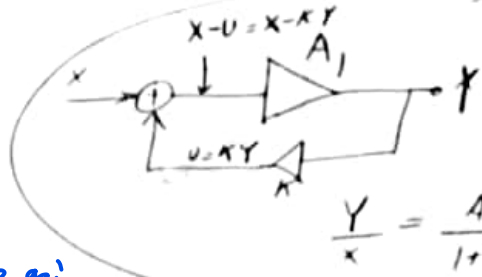

$$\frac{Y}{X} = \frac{A_1}{1 + KA_1}$$

$$V_{out} = A_v (V_{in} - K V_{out})$$

$$V_{out} + A_v K V_{out} = A_v V_{in}$$

$$V_{out} (1 + K A_v) = A_v V_{in}$$


closed loop gain

A_v - open-loop gain.

$$A_{vf} \rightarrow \frac{V_{out}}{V_{in}} = \frac{A_v}{1 + K A_v} \rightarrow \text{closed-loop gain}$$

Closed-loop Input Impedance - R_{in}^o

R_{in}^o

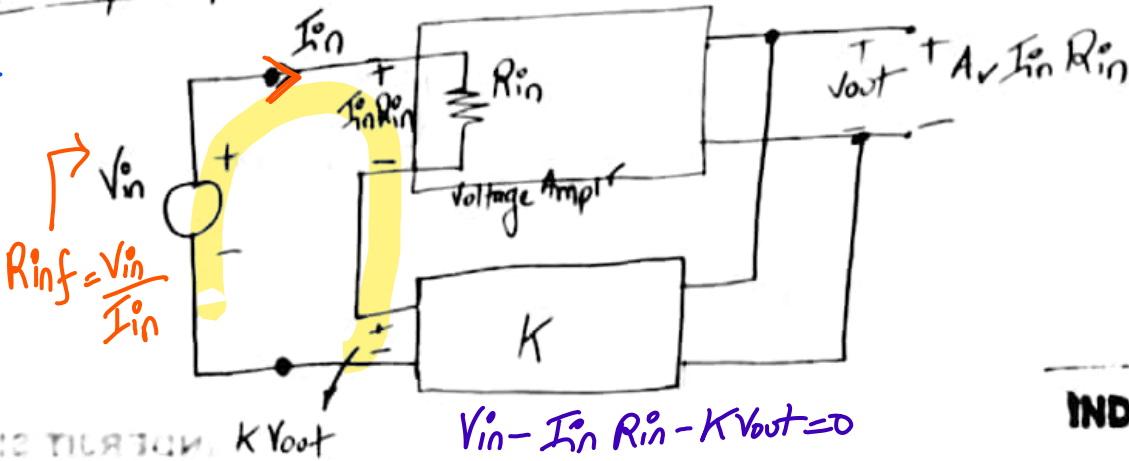

$$V_{in} - I_{in} R_{in} - K V_{out} = 0$$

$$V_{in} = I_{in} R_{in} + K V_{out}$$

INDERJIT SINGH

$$V_{out} = A_v \cdot I_{in} R_{in}$$

→ KVL at I/P side, $V_{in} - I_{in} R_{in} - K V_{out} = 0$

$$V_{in} = I_{in} R_{in} + K A_v R_{in} I_{in}$$

$R_{in} \rightarrow \left[\frac{V_{in}}{I_{in}} = R_{in} (1 + K A_v) \right] \rightarrow$ Closed-loop i/p impedance

$R_{in} -$ i/p impedance of open loop amplifier

$$R_{inf} = R_{in} (1 + K A_v)$$

Is this good or bad?

holds for vty feedback


I/P resistance/impedance \uparrow with intro. of vty feedback

Good thing for a voltage amplifier & overall system for sensing vty

$I_x = \frac{V_1 - V_2}{R_x} \rightarrow \frac{V_1}{R_x} \rightarrow I_x$

$I_x = \frac{V_x - A_v V_1}{R_{out}}$

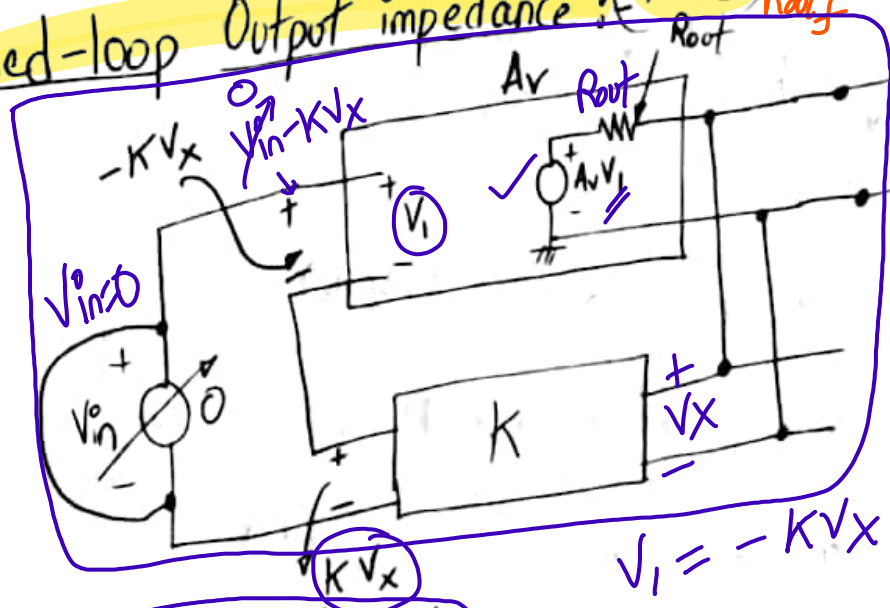Closed-loop Output impedance: $\left(\frac{R_{out f}}{R_{out}} \right)$



$R_{out f} = \frac{V_x}{I_x}$

To measure o/p resistance, set all independent source to zero.

$A_v V_1 = -A_v K V_x$

$V_x - A_v V_1 = \frac{V_x + A_v K V_x}{R_{out}}$

$I_x = \frac{V_x (1 + K A_v)}{R_{out}}$

$$\frac{V_x}{I_x} = \frac{R_{out}}{(1 + K A_v)} = R_{out f}$$

$$I_x R_{out} = V_x (1 + A_v K)$$

$R_{out} \rightarrow$ open-loop o/p impedance

$$\Rightarrow \boxed{\frac{V_x}{I_x} = \frac{R_{out}}{1 + A_v K}}$$

closed-loop o/p Impedance

$R_{out f}$ with -ve flb, R_{out} goes down

Good or Bad?

ckt deliver a v_{tg} (act as a v_{tg} source), so it shld have a low o/p resistance.
 Better v_{tg} ampl'r since R_{out} is lower.

As a result of negative feedback we sacrifice some voltage gain $\left(\frac{A_v}{1 + K A_v}\right)$; but we gained two important


benefits

1. I/p impedance went up by $(1 + K A_v)$ (good for better v_{tg} ampl'r)
2. O/p impedance went down by $(1 + K A_v)$ (-!!-)
3. Bandwidth also goes up by $(1 + K A_v)$

Improves performance of the system.

INDERJIT SINGH

Summary:- ① Voltage-Voltage feedback

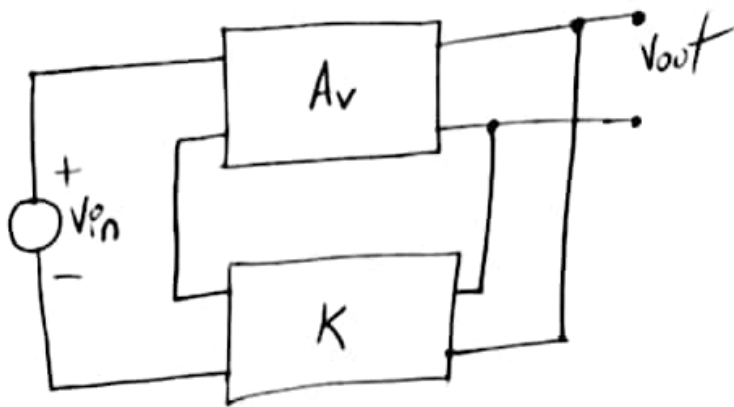

$$\rightarrow \checkmark A_{vf} = \frac{V_{out}}{V_{in}} = \frac{A_v}{1 + A_v K}$$

$$\rightarrow \checkmark \text{closed loop i/p impedance} = R_{in}(1 + K A_v)$$

$$\rightarrow \checkmark \text{closed loop o/p impedance} = \frac{R_{out}}{(1 + K A_v)}$$


- Sensing a vtg at the O/P

- Returning a vtg at the I/P \rightarrow Better vtg ampl^r, vtg sensor since its R_{inf} is higher

\rightarrow Stable voltage gain

INDERJIT SINGH

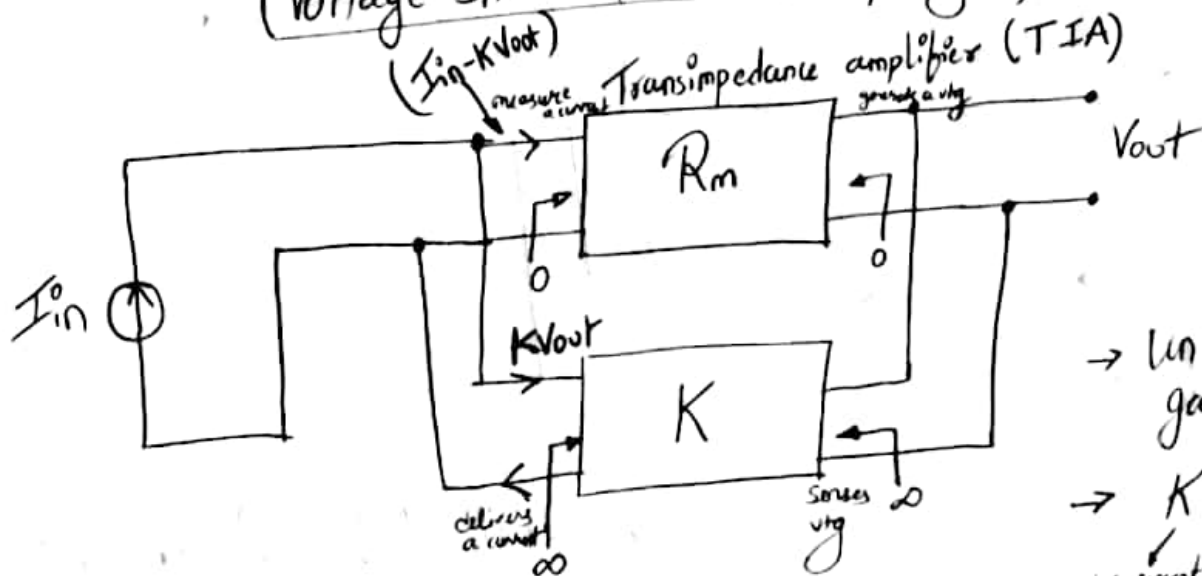• Voltage-Current (Shunt-Shunt) Feedback (Voltage-shunt feedback topologies):




R_m - open loop gain

→ Unit of gain R_m is Ω

→ K unit is $\left(\frac{1}{\Omega}\right)$
(current/voltage)

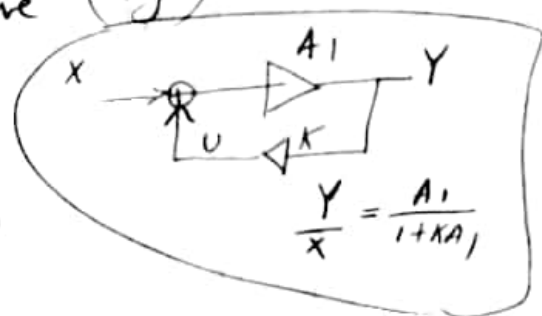Q. Does the unit of K always have to be $\frac{1}{\text{unit of } A_1}$? → Yes



• Closed-loop Gain : -- -- -- → $\frac{V_{out}}{I_{in}} = ?$

$$(I_{in} - K V_{out}) R_m = V_{out}$$

$$\rightarrow I_{in} R_m = V_{out} + K V_{out} R_m$$

$$\rightarrow I_{in} R_m = V_{out} (1 + K R_m)$$

$$\rightarrow \boxed{\frac{V_{out}}{V_{in}} = \frac{R_m}{1 + K R_m}}$$


→ R_{mf} → closed-loop gain

→ Gain with -ve f/b reduces by a factor of $(1 + K R_m)$

INDERJIT SINGH

Closed-loop Input impedance:-

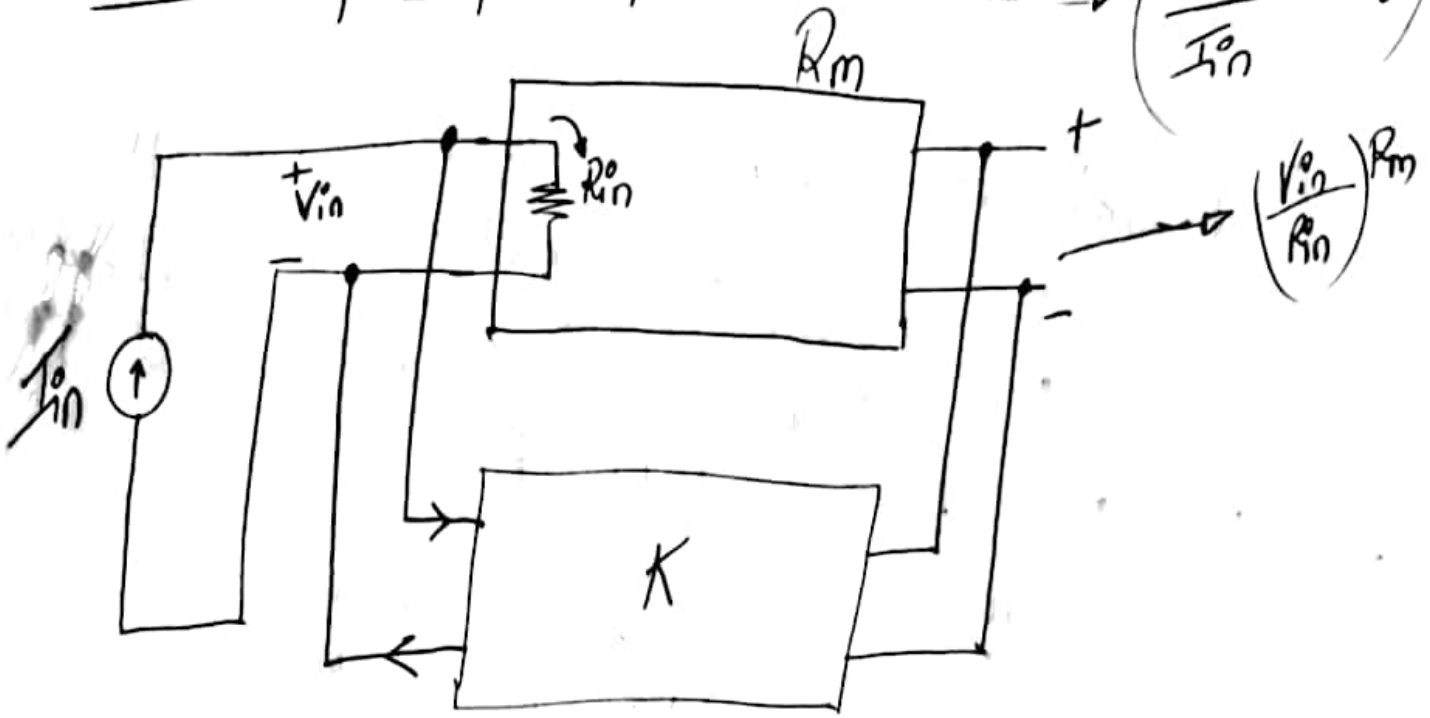$\rightarrow \left(\frac{V_{in}}{I_{in}} = ? \right)$ 02



$\left[\frac{V_{in}}{R_{in}} R_m \right] K \rightarrow$ current that comes out of f/b n/w.

KCL at i/p loop,

$$\left[I_{in} - \frac{V_{in}}{R_{in}} R_m K \right] R_{in} = V_{in}$$

$$I_{in} R_{in} - V_{in} R_m K = V_{in}$$

$$I_{in} R_{in} = V_{in} [1 + K R_m]$$

$$\rightarrow \boxed{\frac{V_{in}}{I_{in}} = \frac{R_{in}}{1 + K R_m}} \rightarrow R_{in_f}$$

As a result of returning a current to the i/p, $R_{in} \downarrow$ yes.

CRK is


Good current sensor

\rightarrow Closed-loop i/p impd has gone down by a factor of $(1 + K R_m)$

INDERJIT SINGH

Closed-loop Output Impedance :- $V_x/I_x = ?$

03

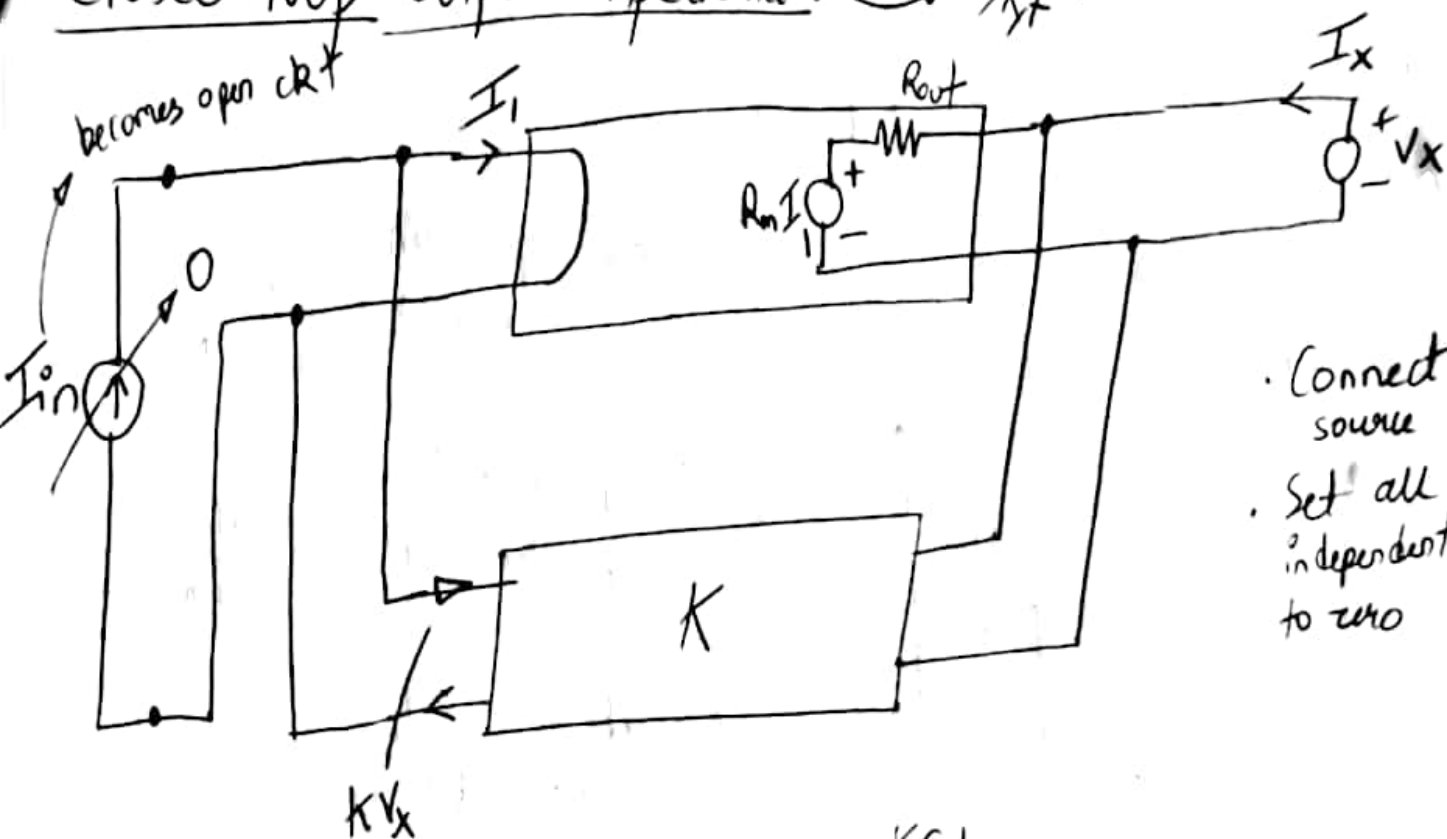

- Connect a test source V_x
- Set all independent sources to zero

$$I_1 = -KV_x \text{ ----- by KCL}$$

$$-KV_x R_m \approx R_m I_1$$

$$I_x = \frac{V_x - R_m I_1}{R_{out}} = \frac{V_x + KV_x R_m}{R_{out}}$$

$$I_x R_{out} = V_x (1 + K R_m)$$

$$\boxed{\frac{V_x}{I_x} = \frac{R_{out}}{1 + K R_m}}$$

R_{out}


closed-loop o/p impedance

INDERJIT SINGH

Summary.

Voltage-current feedback
(shunt)

04

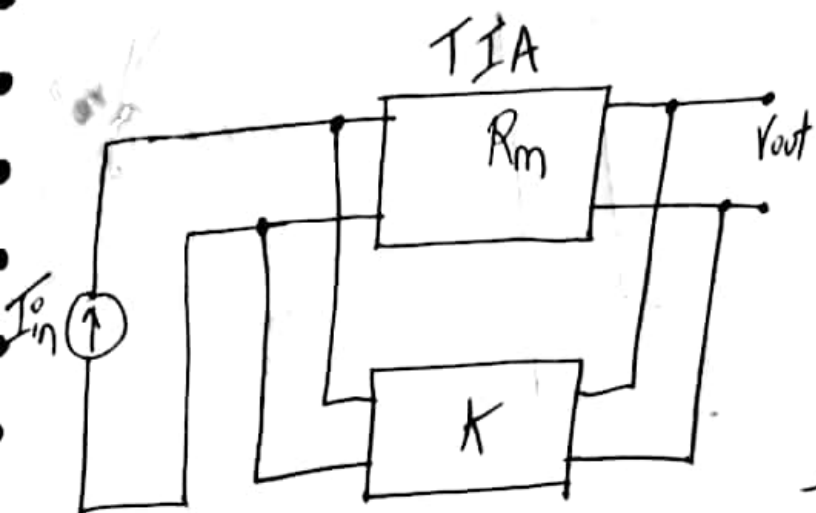

→ Closed-loop Gain
 $(R_{mf}) = \frac{R_m}{1 + KR_m}$

→ Closed-loop Input impedance $(R_{if}) = \frac{R_{in}}{1 + KR_m}$


→ Closed-loop output impedance $(R_{of}) = \frac{R_{out}}{1 + KR_m}$

- Senses a voltage at the o/p
- returns a current at the I/p

INDERJIT SINGH

Analysis of Current-Voltage feedback topology:- (current-series)

11/3/20

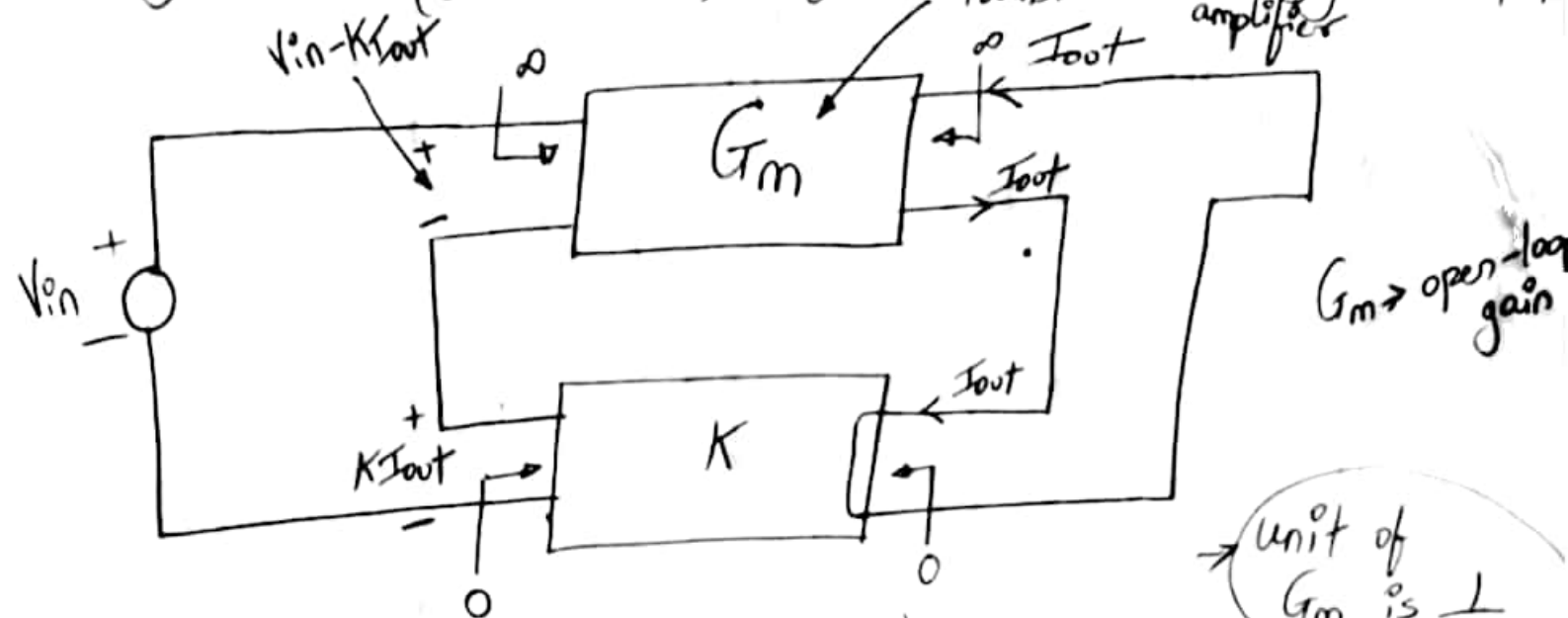

• Closed-loop gain: $\left(\frac{I_{out}}{V_{in}} = ? \right)$

$$(V_{in} - K I_{out}) G_m = I_{out}$$

$$V_{in} G_m = K G_m I_{out} + I_{out}$$


$$V_{in} G_m = I_{out} (1 + K G_m)$$

$$\Rightarrow \boxed{\frac{I_{out}}{V_{in}} = \frac{G_m}{1 + K G_m}} = G_{mf} \rightarrow \text{closed-loop gain}$$

→ Gain with flb reduces by a factor of $(1 + K G_m)$

INDERJIT SINGH

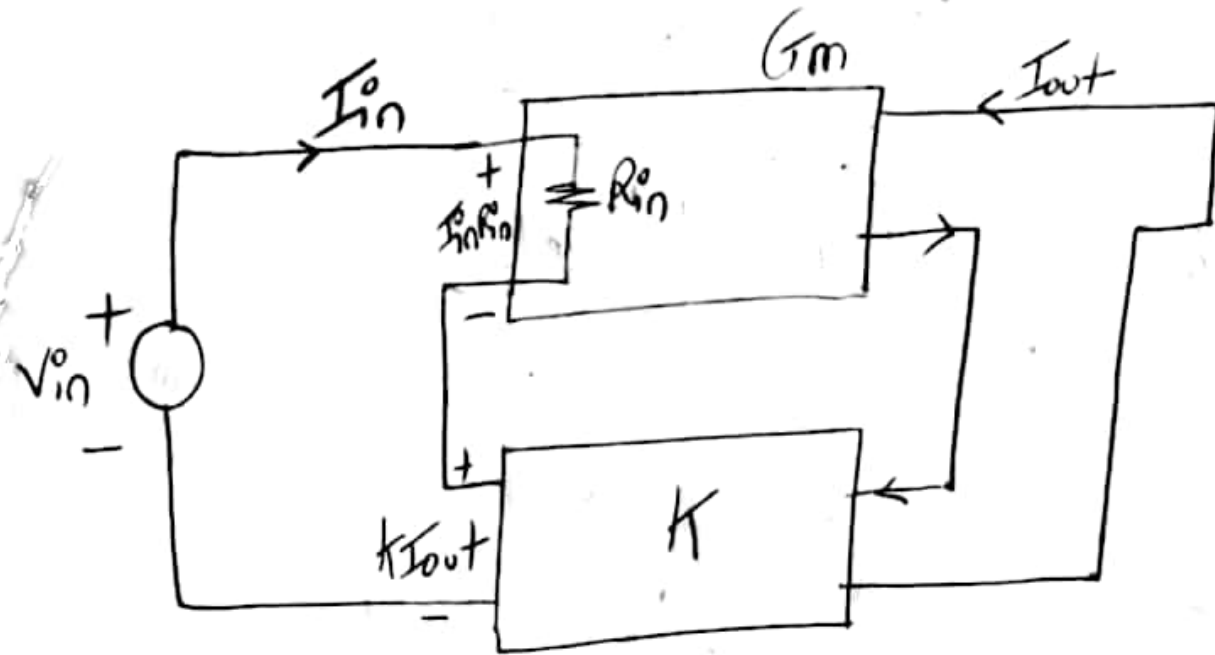Closed-loop Input Impedance :- ($\frac{V_{in}^o}{I_{in}^o} = ?$)



$(I_{in}^o R_{in}) G_m K \Rightarrow$ voltage at o/p of f/b ~w.

KVL at i/p side,



$$V_{in}^o - I_{in}^o R_{in} G_m K = I_{in}^o R_{in}$$

$$V_{in}^o = I_{in}^o R_{in} (1 + G_m K)$$

$$\Rightarrow \boxed{\frac{V_{in}^o}{I_{in}^o} = R_{in} (1 + G_m K)} \quad \xrightarrow{\text{closed-loop i/p impedance}}$$

~~how closed loop~~ i/p impd has gone up by a factor of $(1 + K G_m)$

Closed-loop O/P impedance :

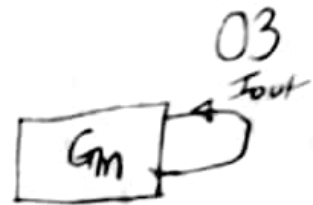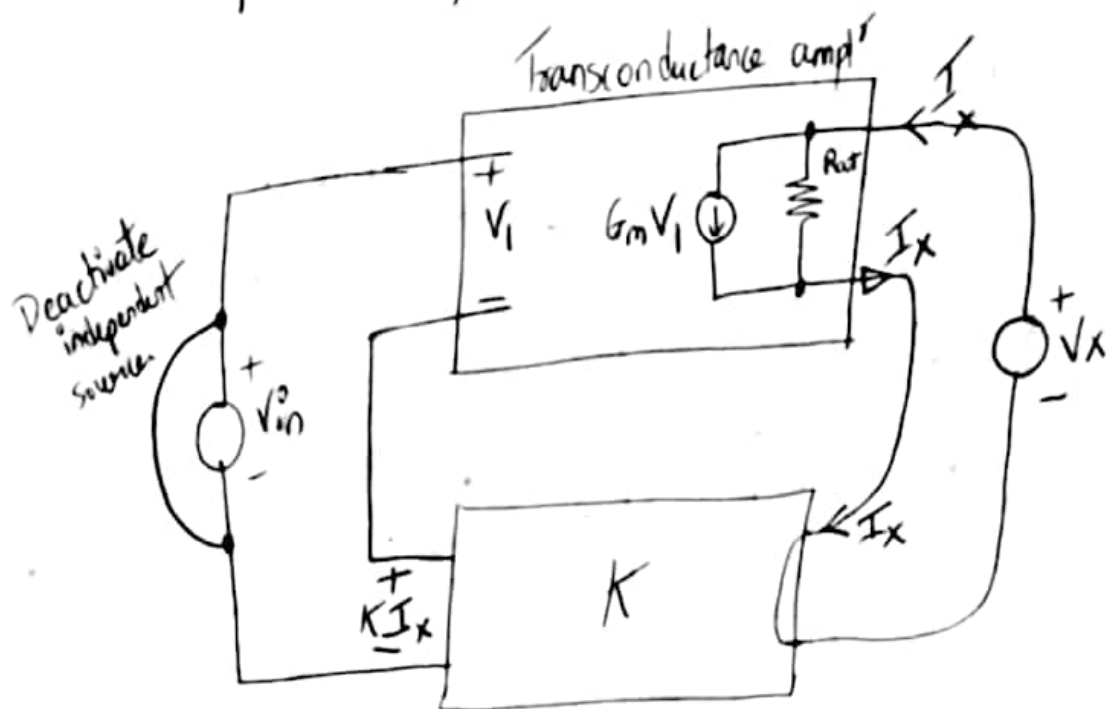

- How to measure o/p impedance when there a current at the o/p?
- Cut the o/p loop, place a vtg source &

$$V_1 = -K I_x$$

→ KCL at O/P loop ,

$$-K I_x G_m + \frac{V_x}{R_{out}} = I_x$$

$$\frac{V_x}{R_{out}} = I_x (1 + K G_m)$$


$$\Rightarrow \boxed{\frac{V_x}{I_x} = R_{out} (1 + K G_m)}$$

→ R_{outf} → Closed-loop o/p impedance

→ The above ckt wants to deliver a current (ie wants to become a good current source, so $R_{outf} \uparrow$)

means the above ckt has become a good current source.

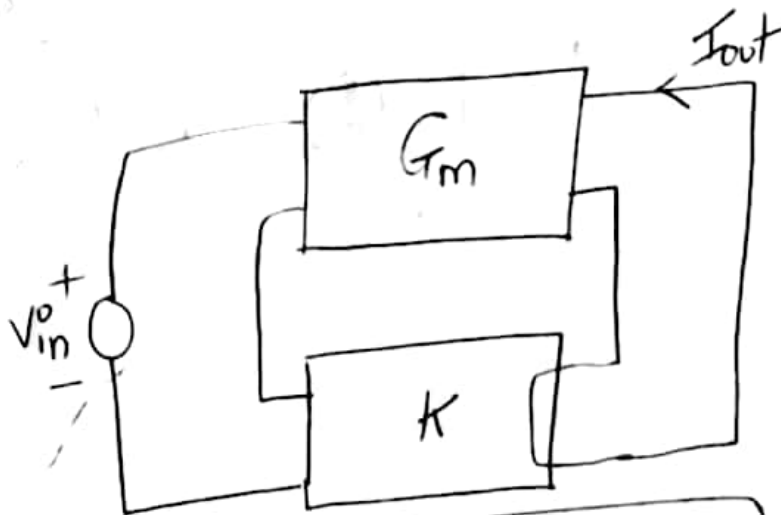Summary:- Current - Voltage feedback topology:-



→ Closed loop gain $G_{mf} = \frac{G_m}{1 + K G_m}$


→ Closed loop I/p impedance $R_{in f} = R_{in}(1 + K G_m)$

- senses a current at o/p
- returns a voltage at I/p

→ Closed-loop O/p impedance $R_{out f} = R_{out}(1 + K G_m)$

Analysis of Current-current feedback topology: -

12/3

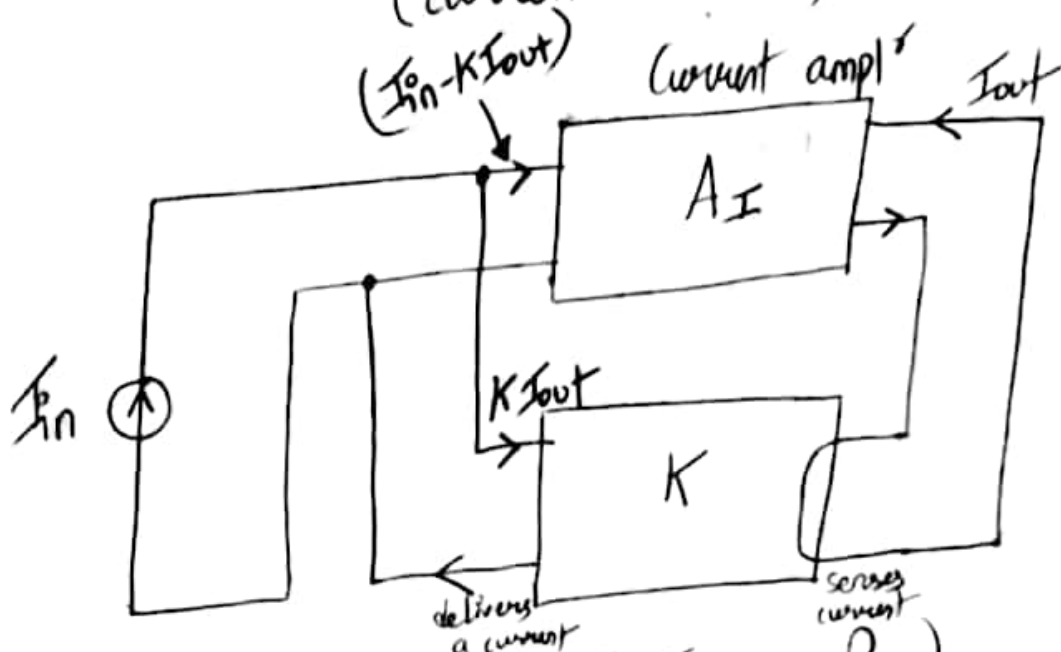

$A_I \rightarrow$ open loop gain

Closed-loop gain: $\left(\frac{I_{out}}{I_{in}} = ? \right)$

unit of A_I : unitless

$$(I_{in} - K I_{out}) A_I = I_{out}$$

$$\text{i.e. } I_{in} A_I = A_I K I_{out} + I_{out}$$


$$\text{i.e. } I_{in} A_I = I_{out} (1 + K A_I)$$

$$\Rightarrow \boxed{\frac{I_{out}}{I_{in}} = \frac{A_I}{1 + K A_I}} \rightarrow A_{If} \rightarrow \text{closed-loop gain}$$

→ Gain with -ve flb reduces by a factor of $(1 + K A_I)$

INDERJIT SINGH

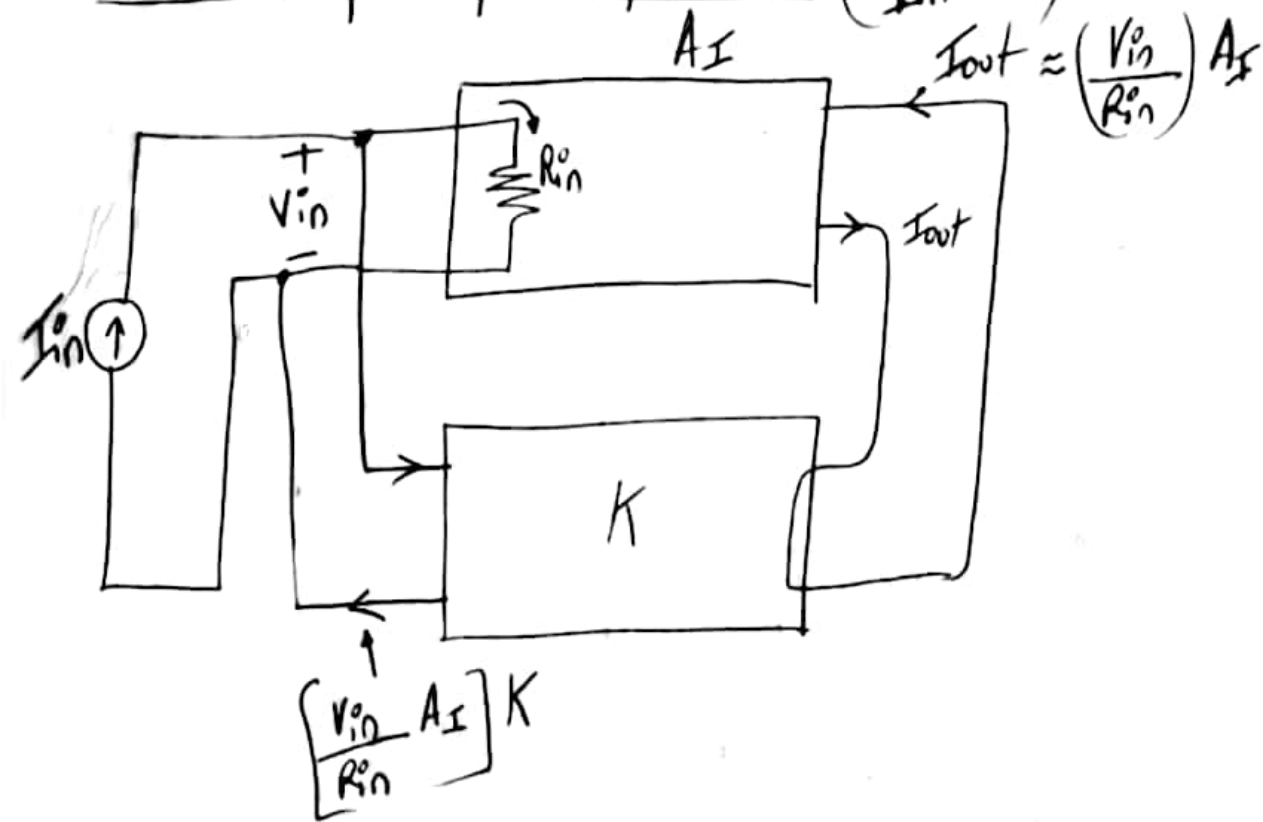Closed-loop Input impedance:- $\left(\frac{V_{in}}{I_{in}} = ?\right)$



$$\rightarrow \left[I_{in} - \left(\frac{V_{in}}{R_{in}} A_I K \right) \right] R_{in} = V_{in}$$

$$\text{ie } I_{in} R_{in} - V_{in} A_I K = V_{in}$$

$$\text{ie } I_{in} R_{in} = V_{in} (1 + K A_I)$$


$$\Rightarrow \frac{V_{in}}{I_{in}} = \frac{R_{in}}{1 + K A_I}$$

$\rightarrow R_{in}^f \rightarrow$ Closed-loop I/P impedance

Closed-loop Output Impedance :- $\left(\frac{V_x}{I_x} = ? \right)$

03

Deactivate it
ie o.c I_{in}

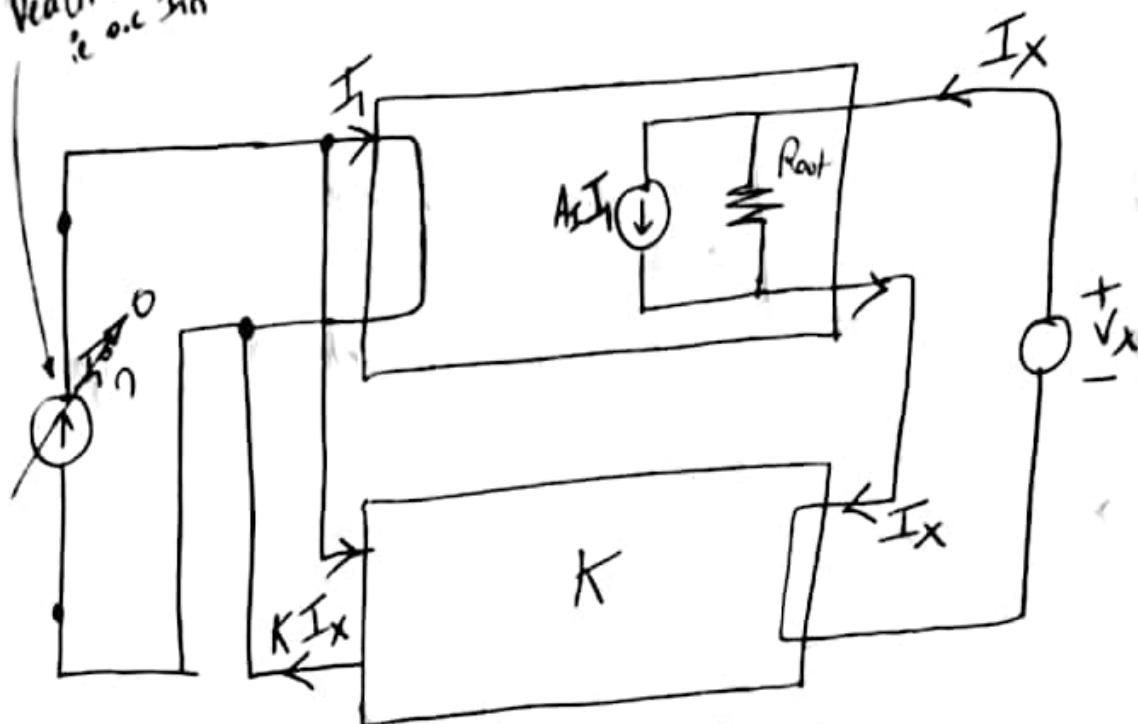

- Cut the o/p wire & insert a test source
- Deactivate all independent source ie $I_{in} = 0$
- Find $\frac{V_x}{I_x} = ?$

$$I_1 = -K I_x \quad \text{--- (KCL)}$$

$$\text{ie } A I_1 = -K I_x A$$

KCL at o/p loop,

$$-K I_x A + \frac{V_x}{R_{out}} = I_x$$

INDERJIT SINGH


$$\text{ie } \frac{V_x}{R_{out}} = I_x (1 + K A)$$

$$\text{ie } \boxed{\frac{V_x}{I_x} = R_{out} (1 + K A)} \quad \text{--- } R_{out} \rightarrow \text{Closed-loop O/p impedance.}$$

INDERJIT SINGH

Summary:-

Current-Current feedback topology:-

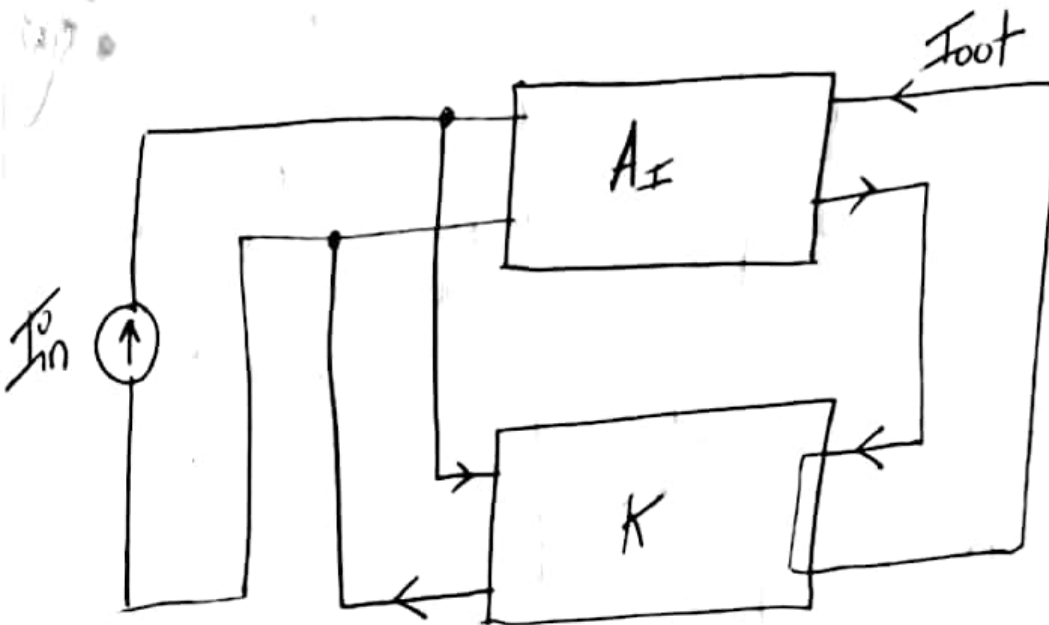

→ senses current at o/p

→ returns a current at I/P

→ Closed-loop gain: $A_{If} = \frac{A_I}{1 + KA_I}$ 4/8

→ Closed-loop i/p impedance: $R_{if} = \frac{R_{in}}{1 + KA_I}$

→ Closed-loop o/p impedance: $R_{outf} = R_{out} (1 + KA_I)$

INDRIT SINGH

Feedback Topologies	Sense (Sampling) mechanism	Return (Mixing) mechanism	Amplifiers used	Closed loop gain	Closed loop I/P impedance $R_{in f}$	Closed loop o/p impedance $R_{out f}$
1. Voltage-voltage (shunt-series) (Voltage-series)	sensing a voltage at the o/p in parallel	returning a voltage at the i/p in series	Voltage amplifiers	$A_{vf} = \frac{A_v}{1+K A_v}$	$R_{in} (1+K A_v)$	$\frac{R_{out}}{(1+K A_v)}$
2. Voltage-current (shunt-shunt) (Voltage-shunt)	sensing a voltage at the o/p in parallel	returning a current at the i/p in parallel	Trans-impedance amplifiers	$R_{mf} = \frac{R_m}{1+K R_m}$	$\frac{R_{in}}{1+K R_m}$	$\frac{R_{out}}{1+K R_m}$
3. Current-voltage (series-series) (Current-series)	sensing a current at the i/p in series	returning a voltage at the i/p in series	Trans-conductance amplifiers	$G_{mf} = \frac{G_m}{1+K G_m}$	$R_{in} (1+K G_m)$	$R_{out} (1+K G_m)$
4. Current-current (series-shunt) (Current-shunt)	sensing a current at the o/p in series	returning a current at the i/p in parallel	Current amplifiers	$A_{if} = \frac{A_i}{1+K A_i}$	$\frac{R_{in}}{(1+K A_i)}$	$R_{out} (1+K A_i)$