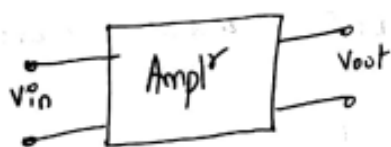


Basics of BJT amplifier

BJT amplifiers

Understanding concepts of amplification with reference to input/output characteristics

✓ Amplifier requirements:-




- 1) Gain should be high
eg voltage gain of a voltage amplifier \rightarrow high
- 2) I/P impedance
- 3) O/P impedance
- 4) Linearity (O/P should be linear w.r.t I/P)

• BJT as a device should amplify \rightarrow small time-varying signals.

\rightarrow This condition must be satisfied for BJT amplifiers to be Linear

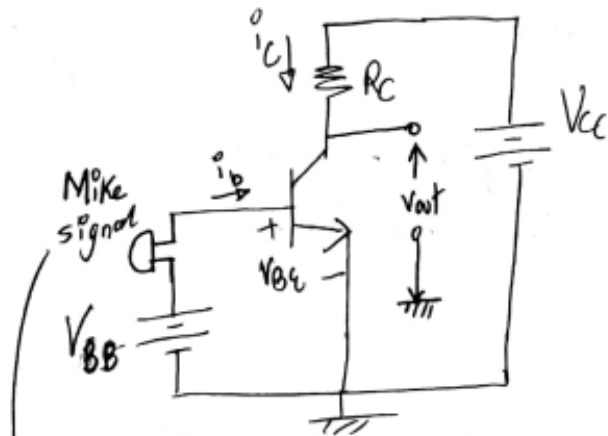• Next, we need to superimpose small AC sig with DC?
Why DC biasing is required \rightarrow so that BJT wakes up & works in proper mode i.e. active region
 \rightarrow so that it is used as amplifier





It adds a small-time varying 1/P V_{in} ($V_{mike} \propto V_{msinot}$)

→ BJT act as : voltage-dependent current source

→ "converts" a voltage to a current
 (V_{BE}) or V_{be}


(I_C) — DC quantity

i_c — AC quantity

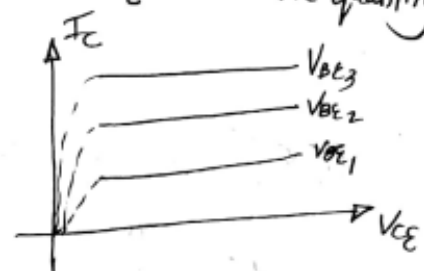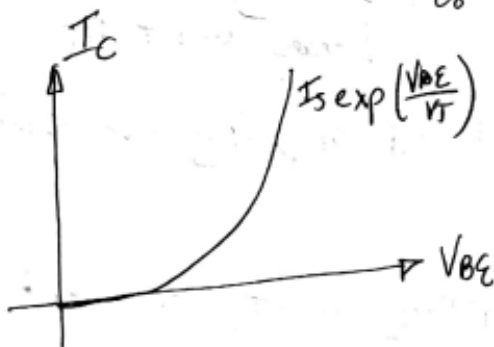


Biasing: Provide proper voltage (V_{BE}) & current (I_C) so that the transistor can amplify (in the absence of signals)

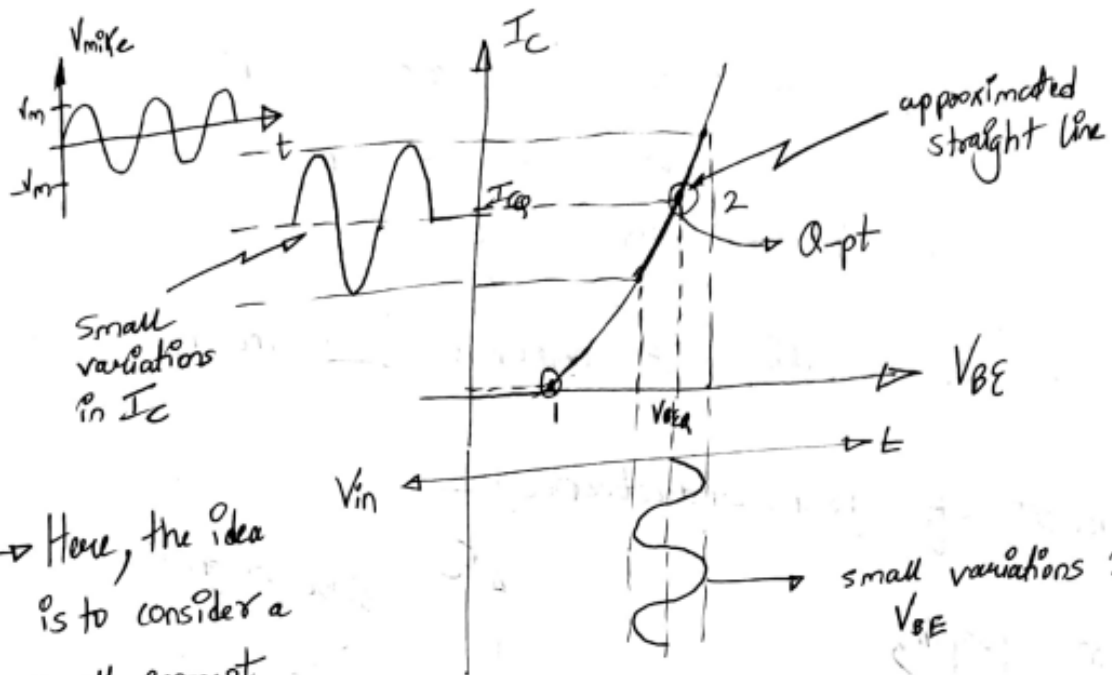Operating point : The bias values chosen for V_{BE} , I_C , V_{CE} , ... etc.



→ Here, the idea is to consider a small segment of exponential curve to be Linear straight line

Combining transfer curve & time response

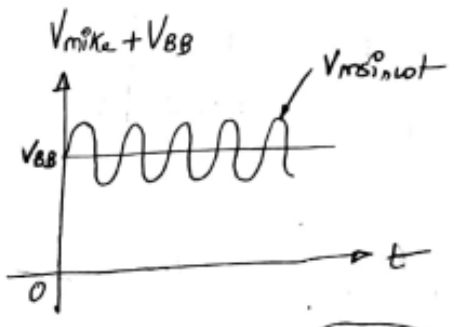

So our s/g limit should be within this linear segment

→ Hence, called as small s/g

I_S - reverse satn current
eg $10^{-15} A$

Observations:-

- 1) At point A, in absence of s/g, variations in collector current are very small ($\sim I_S$) i.e BJT is not biased & will not work in active region
- 2) At point B, BJT is biased in active region, since it has sufficient value of I_C & V_{BE}

3) A bjt can acts as voltage-dependent current source \rightarrow since I_C changes in response to its base-emitter voltage.

4) The operating point determine how the bjt responds.


• Concept of transconductance :-

From graph,

$$g_m = \left. \frac{dI_C}{dV_{BE}} \right|_{Qpt}$$

slope of
 I_C vs V_{BE}
characteristics

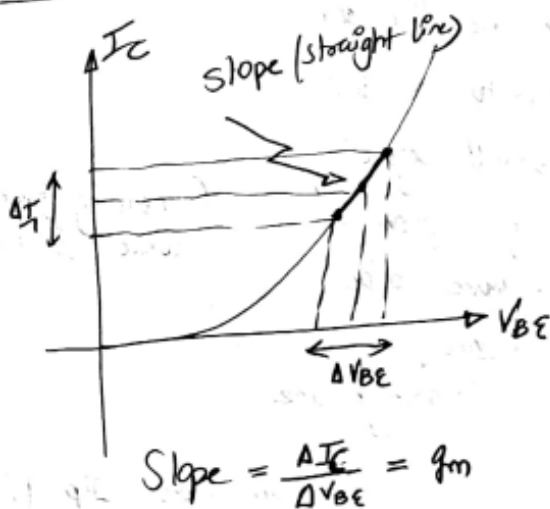unit: $\frac{1}{\Omega}$ or $\frac{mA}{V}$



$$g_m = \frac{dI_C}{dV_{BE}}$$

$$= \frac{d}{dV_{BE}} \left(I_S \exp \frac{V_{BE}}{V_T} \right)$$

$$= \frac{I_S}{V_T} \exp \frac{V_{BE}}{V_T}$$

$$g_m = \frac{I_C}{V_T}$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$\Delta I_C = \Delta V_{BE} g_m$$

Small
changes
in I_C

small
changes
in V_{BE}

slope \rightarrow a constant


It suggest that base-to emitter voltage controls the collector current in a BJT

($V_T = 26mV$ @ $27^\circ C$)

$$g_m = \frac{I_{CQ}}{V_T}$$

05

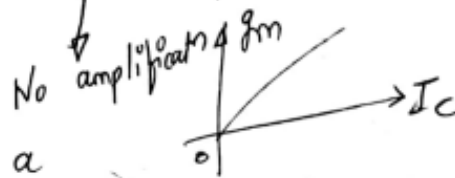1) With no bias $\Rightarrow I_C = 0 \Rightarrow g_m = 0$




2) For amplification, we need a certain $g_m \Rightarrow$ certain $I_{CQ} \rightarrow$ certain V_{BE} .

Small-signal operation:-

\hookrightarrow The signal coming into the ckt is "small"
 \rightarrow The signal perturbs the bias (operating) point by only a small amount.
 \hookrightarrow comparable to V_T value.

Small-sig parameter (r_{π}) :-

Consider I/P characteristics of

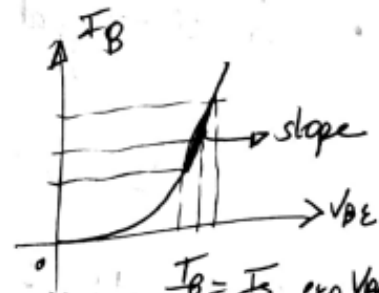

by

$$r_{\pi} = \frac{1}{\text{slope}} = \frac{\Delta I_B}{\Delta V_{BE}} \Big|_{V_{CE} = \text{constant}}$$



$$\therefore \frac{dI_B}{dV_{BE}} = \frac{d}{dV_{BE}} \left(\frac{I_S}{\beta} \exp \frac{V_{BE}}{V_T} \right) = \frac{I_S}{\beta \times V_T} \exp \left(\frac{V_{BE}}{V_T} \right)$$

$$\therefore \frac{dI_B}{dV_{BE}} = \frac{I_B}{V_T} \therefore \boxed{\frac{dV_{BE}}{dI_B} = r_{\pi} = \frac{I_{BQ}}{V_T}}$$

• Small-sig hybrid- π model of BJT

06

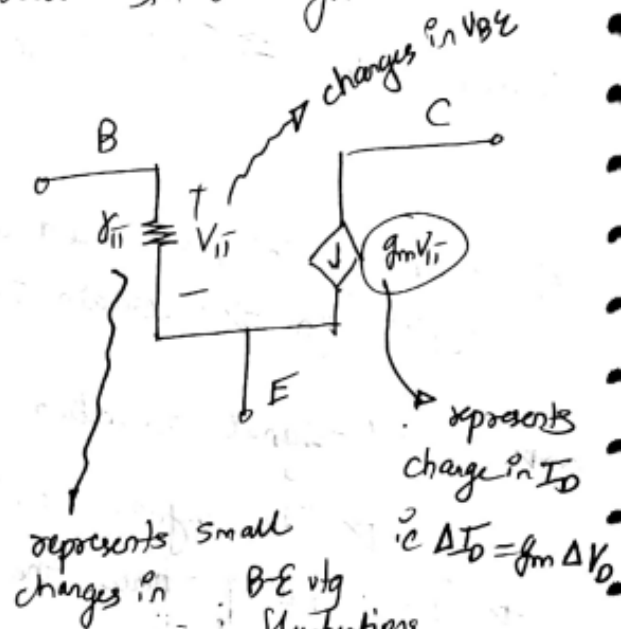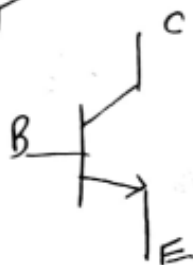Now, we are ready to draw Small-signal model of BJT




• Small-Signal model \Rightarrow (represents only, time-varying quantities)


\searrow represent only changes in parameters

• Early effect (Small-sig o/p resistance/impedance) (so DR r_o)

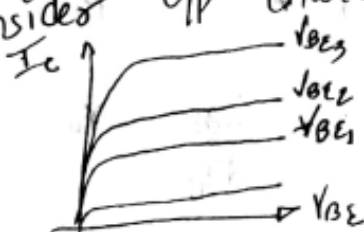
let's consider o/p characteristics of BJT



We think, I_c remains constant

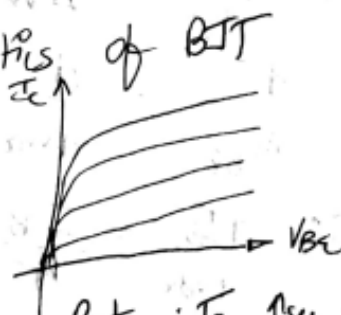

But, I_c rises slightly with v_{ce}

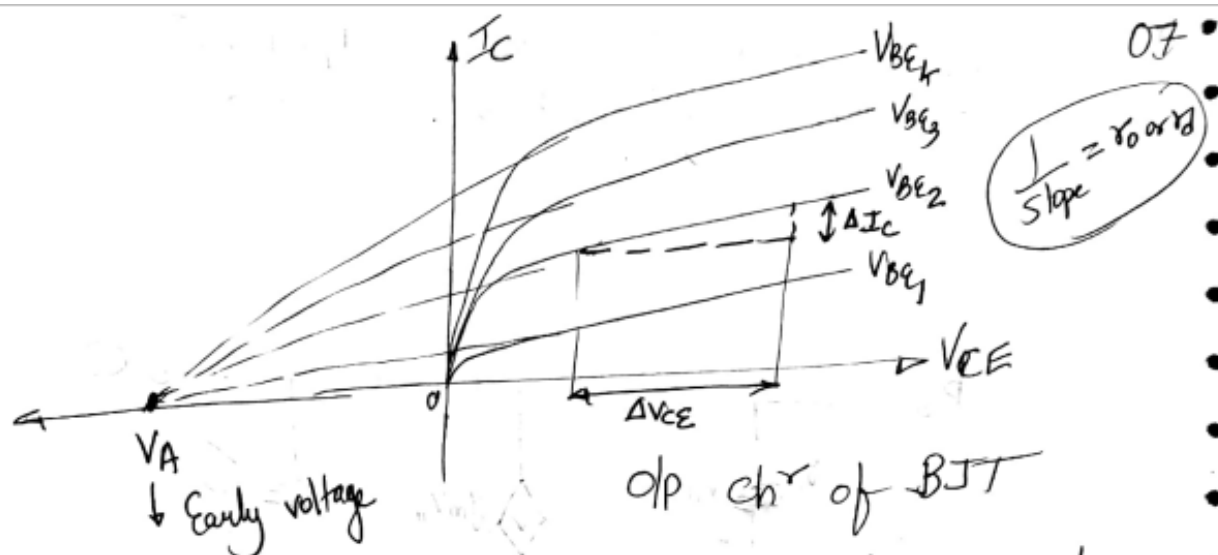

- In above graph, if we extrapolate I_C curve to -ve axis of V_{CE} , these family of curves meet at a point called "Early voltage" V_A .

- In reality, I_C rises slightly with V_{CE} due to early effect.

$$I_C = \left(I_S \exp \frac{V_{BE}}{V_T} \right) \left(1 + \frac{V_{CE}}{V_A} \right) \quad V_A: \text{Early voltage}$$

$$\text{Slope} = \frac{dI_C}{dV_{CE}} = \left(\frac{I_S}{V_A} \exp \frac{V_{BE}}{V_T} \right) \left(1 + \frac{V_{CE}}{V_A} \right)$$

$$\text{ie } \frac{dI_C}{dV_{CE}} = \frac{I_{CQ}}{V_A}$$

$$\text{ie } r_o = r_d = \frac{dV_{CE}}{dI_C} = \frac{V_A}{I_{CQ}}$$

$$\text{ie } r_o = r_d = \frac{V_A}{I_{CQ}}$$


• We need to include in small-sig model.

r_o ,

Small-sig op resistance of a BJT biased in forward active region.

Complete small signal model of npn BJT including early effect is given below

08

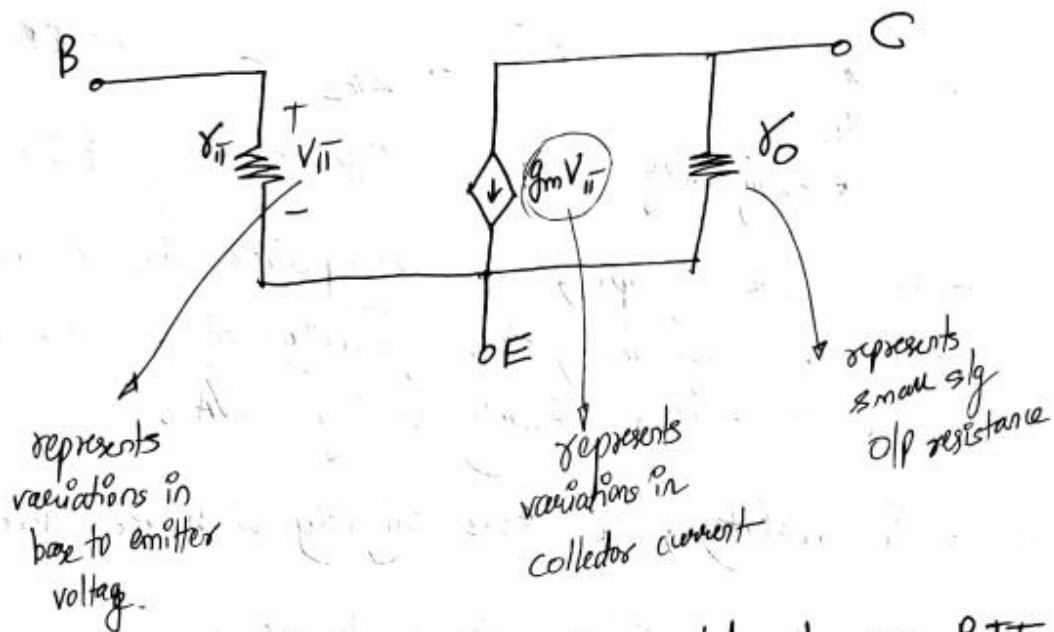

Small-signal hybrid- π model of npn BJT

→ Small-signal parameters :-

1.
$$r_{\pi} = \frac{\beta}{g_m} \quad \Omega$$

2.
$$g_m = \frac{I_{CQ}}{V_T} \quad \frac{mA}{V}$$


3.
$$r_o = \frac{V_A}{I_{CQ}} \quad k\Omega$$

Common emitter amplifier with internal resistance R_{sig}

✓ AC Analysis of BJT amplifiers:-

09


1. Common emitter amplifier:-

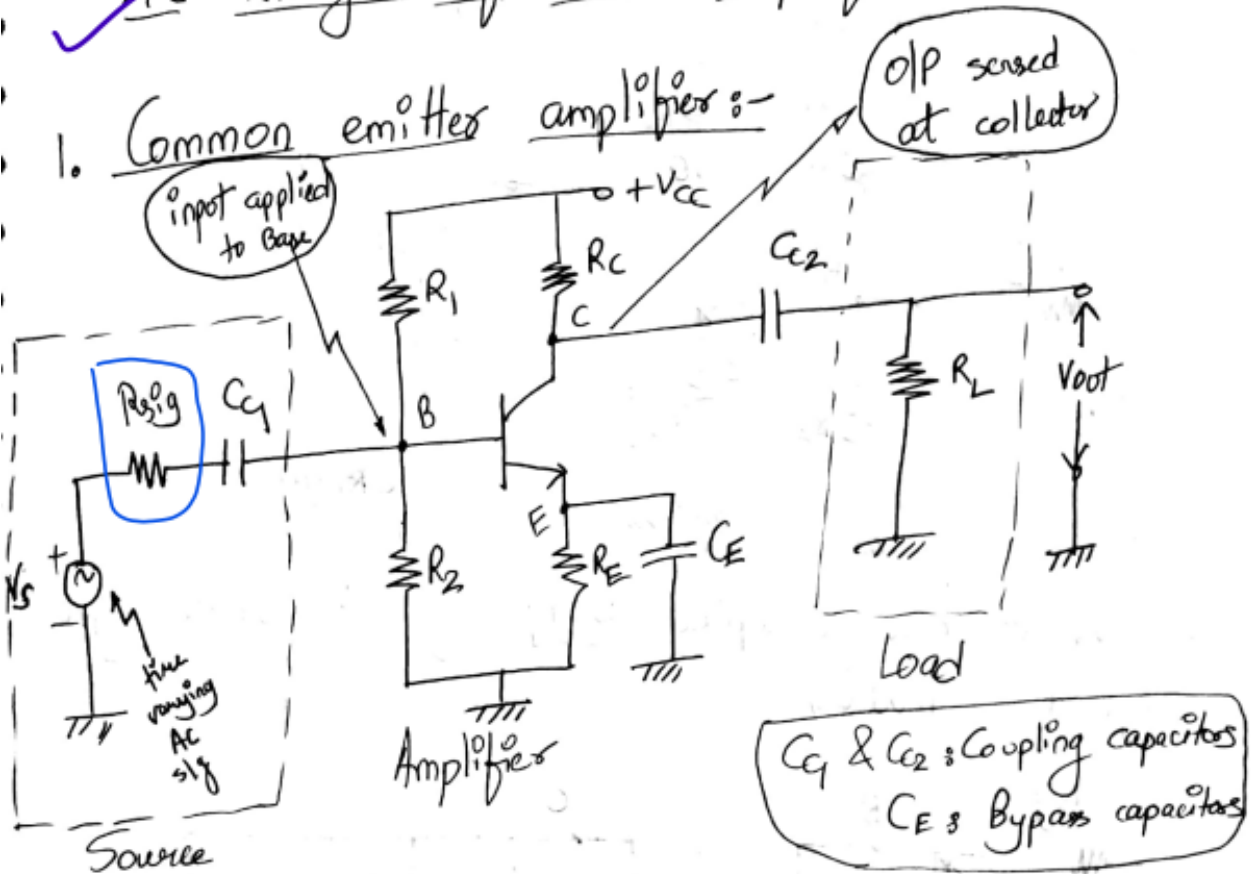


Observations:

1. In CE amplifier, IP signal is applied to the "base" terminal and o/p is sensed at the "Collector" terminal.
2. For AC analysis, all the capacitors are replaced by a short circuit \rightarrow as the capacitive impedances ($X_C = \frac{1}{2\pi f C}$) are very low at mid-frequencies.
3. DC supply is also replaced by a short circuit for small signal (AC) analysis.

→ AC equivalent circuit is,

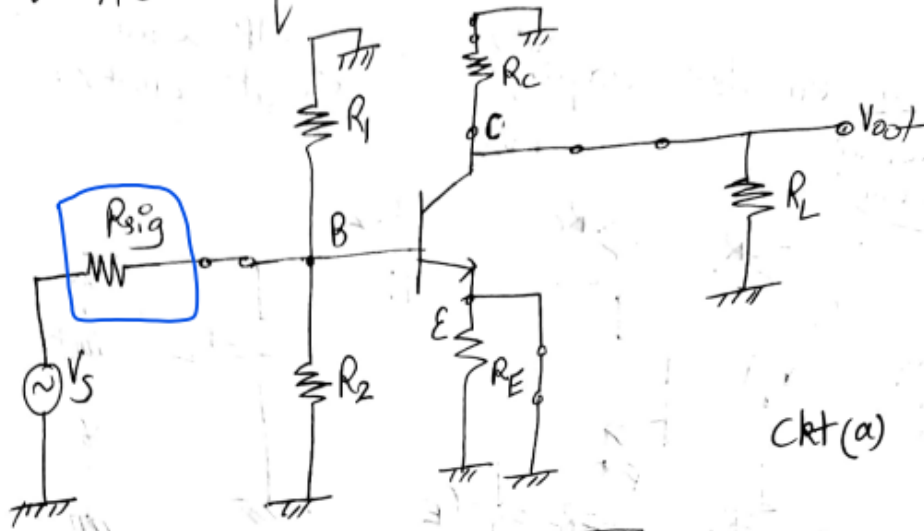

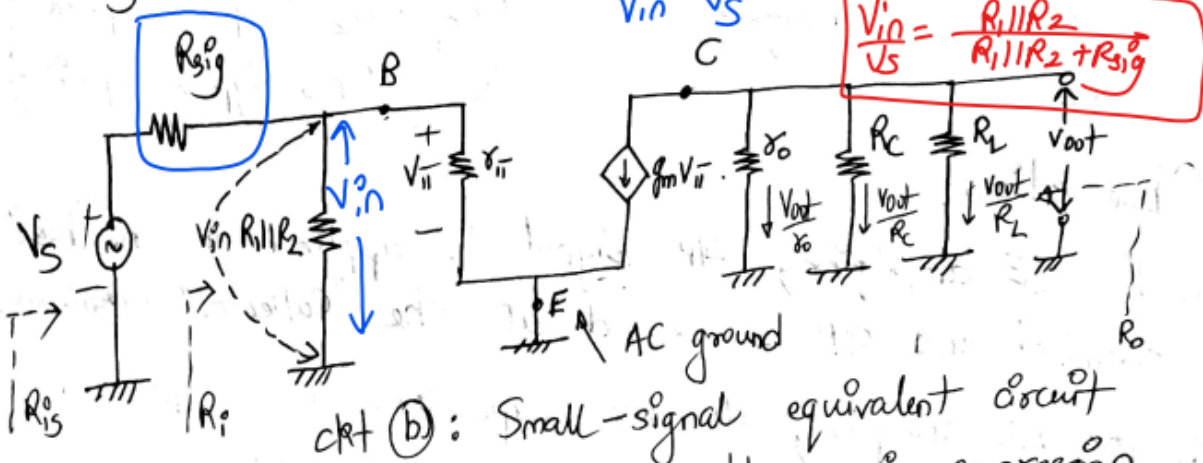→ Now, we have to replace BJT by its small-signal hybrid- π model, $A_v = \frac{V_{out}}{V_{in}} \frac{V_{in}}{V_s}$



Analysis:

1) To find A_v : voltage gain expression

• From ckt b, $V_{in} = V_{\pi}$

KCL at Collector terminal,

11

$$g_m V_{\pi} + \frac{V_{out}}{r_o} + \frac{V_{out}}{R_C} + \frac{V_{out}}{R_L} = 0$$

$$g_m V_{in} = -V_{out} \left(\frac{1}{r_o} + \frac{1}{R_C} + \frac{1}{R_L} \right)$$

$$\rightarrow \boxed{A_v = \frac{V_{out}}{V_{in}} = -g_m (r_o \parallel R_C \parallel R_L)}$$

small-sig voltage gain
of amplifier

-ve sign indicates that
I/P & o/p are out-of phase

$$\text{Now, } A_{v_s} = \frac{V_{out}}{V_s} = \frac{V_{out}}{V_{in}} \times \frac{V_{in}}{V_s} = A_v \times \frac{V_{in}}{V_s}$$

$$\text{From ckt (b), } A_{v_s} = A_v \frac{V_{in}}{V_s}$$

$$\rightarrow \boxed{\frac{V_{in}}{V_s} = \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{sig}}}$$



--- by V.D.R

$$\text{ie } \boxed{A_{v_s} = A_v \times \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{sig}}}$$

2) Input impedance/resistance (Z_i/R_i):

12

From ckt (b),

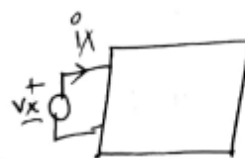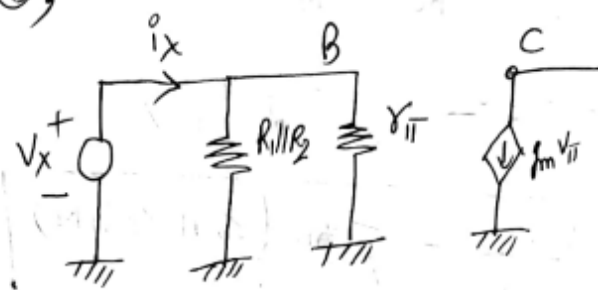


Since, B-C junction is reverse-biased & open-ckt, no current flows from B to C in ckt above,

∴ Current i_x flows into $(R_1 || R_2)$ branch & r_{π} branch

$$\frac{V_x}{i_x} = R_1 || R_2 || r_{\pi}$$

$$R_i = R_1 || R_2 || r_{\pi}$$

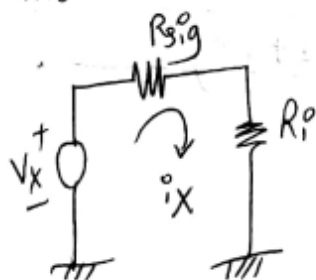Now, if we include source resistance R_{sig} , we have



$$R_{is} = \frac{V_x}{i_x} = R_{sig} + R_i$$

$$R_{is} = R_{sig} + R_1 || R_2 || r_{\pi}$$



3. o/p impedance/resistance: (Z_o/R_o)

For o/p resistance calculation,
we short-ckt i/p source.

i.e. $V_{in} = 0$ i.e. $V_s = 0$

i.e. Since $V_{in} = V_{ii} \Rightarrow V_{ii} = 0$

Referring ckt (B), we get:

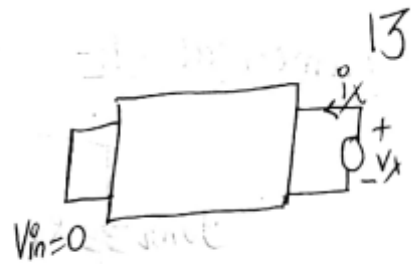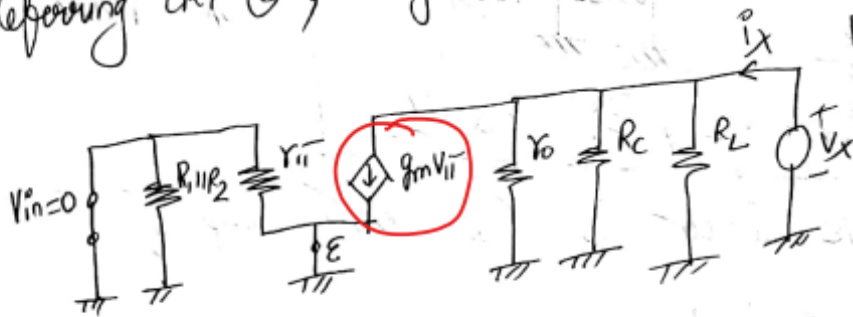


$$g_m V_{ii} = 0$$

It means that
a current source
being zero

it is replaced
by open-ckt

Above ckt reduces to

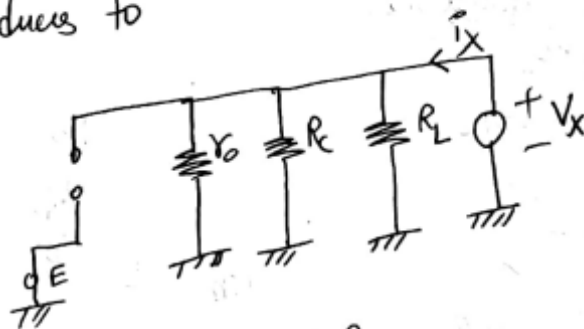

$$\text{i.e. } \frac{V_x}{I_x} = r_o \parallel R_c \parallel R_L$$

$$\text{i.e. } \boxed{R_o = r_o \parallel R_c \parallel R_L}$$