

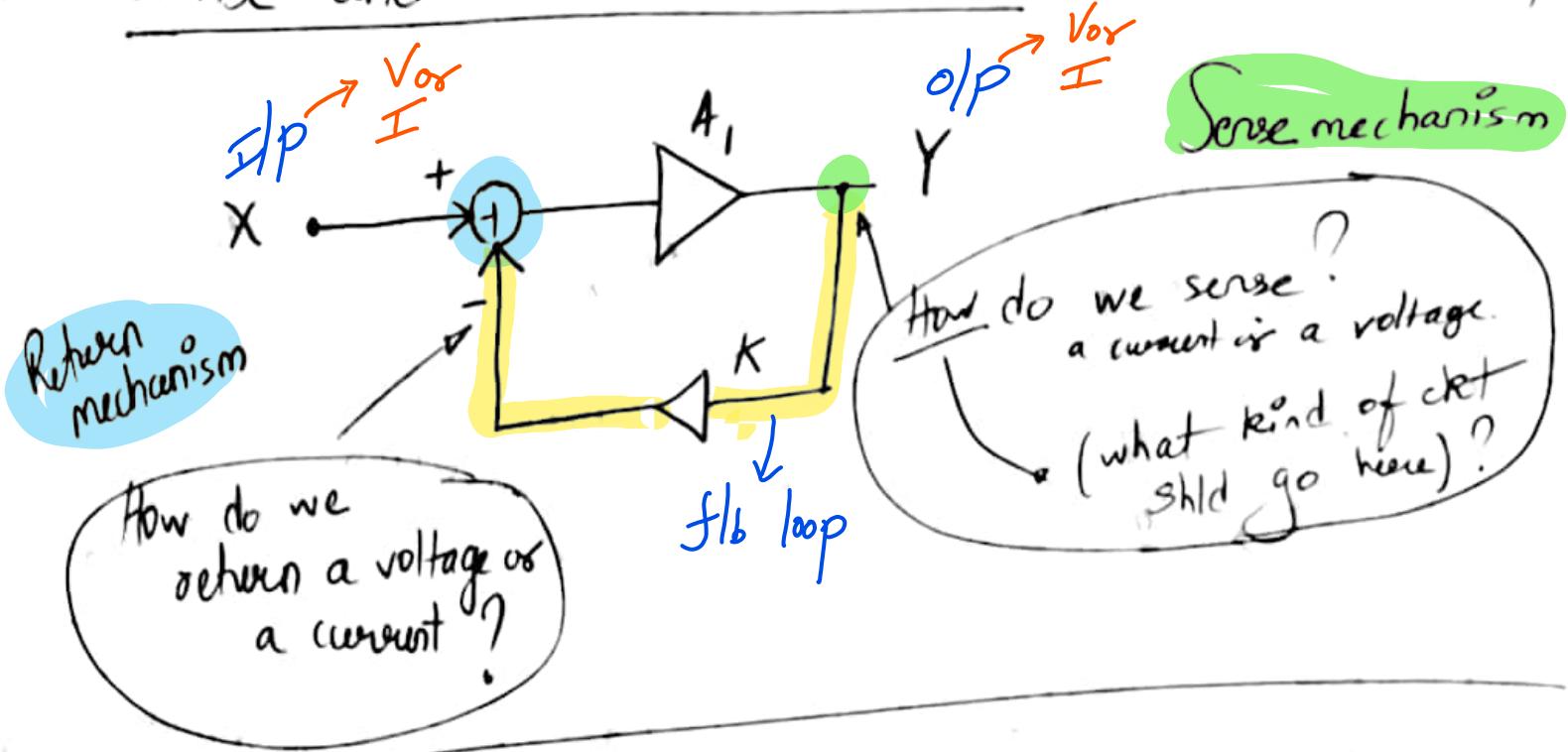


7. Sense and Return Mechanisms:-

07



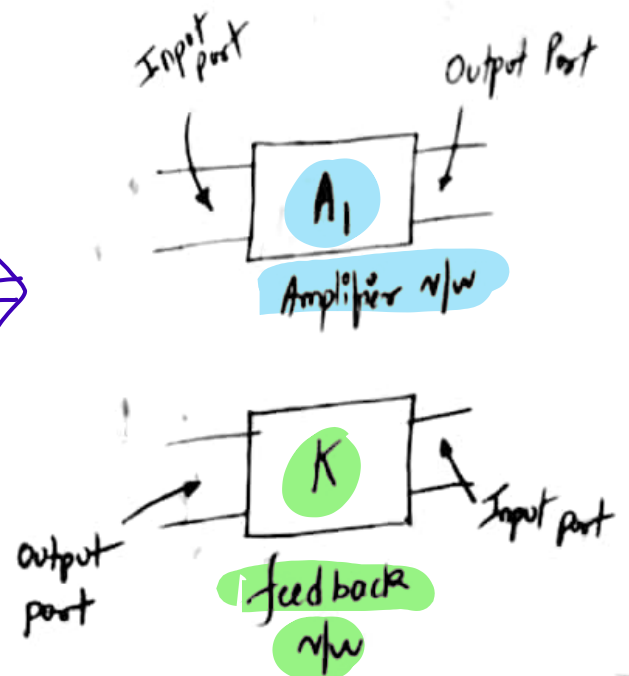


Alternative Feedback Model:-

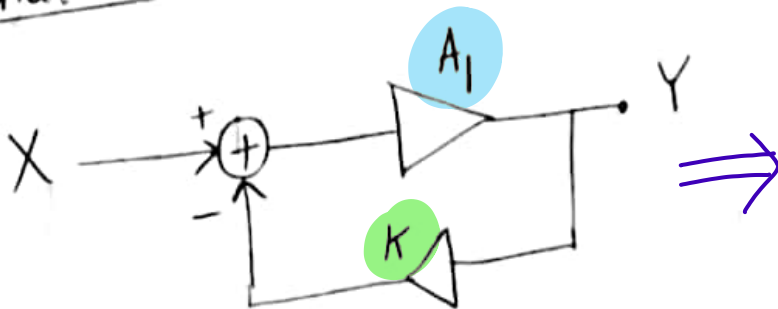

Return mechanisms:

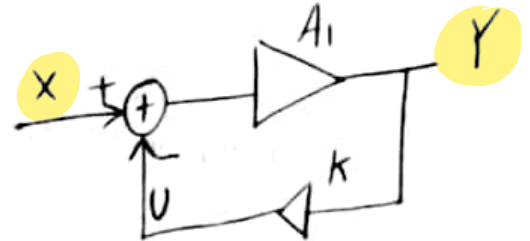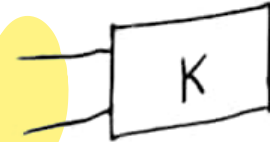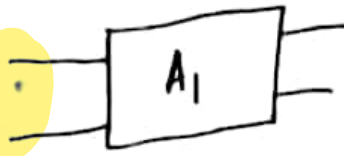How to subtract two voltages or two currents?




→ X & Y can be a voltage or a current


→ X & U should have same dimension

Current

Voltage


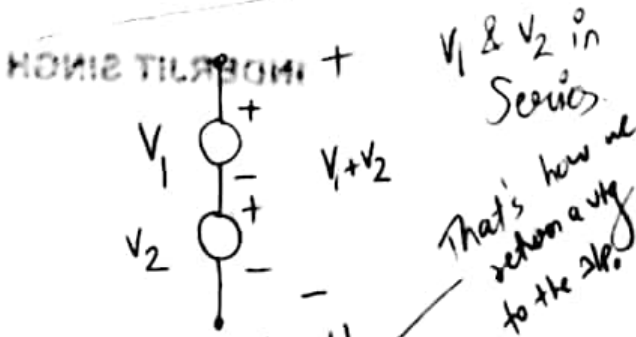


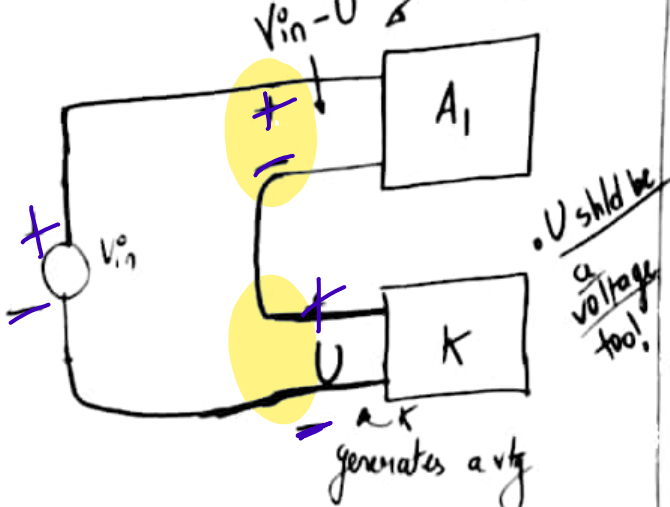V_1 & V_2 in Series
That's how we return a voltage to the i/p.



→ That's how we built a subtractor at the i/p of a system.

I_1 & I_2 in Parallel

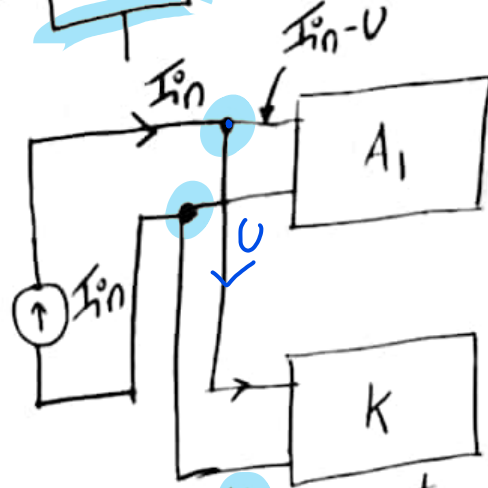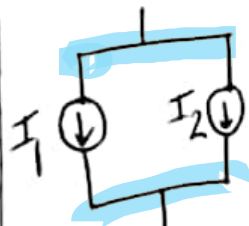


• U is a current

→ That's how we return a current to the i/p.

INDERJIT SINGH


Review of Sense and Return mechanisms:-

voltage

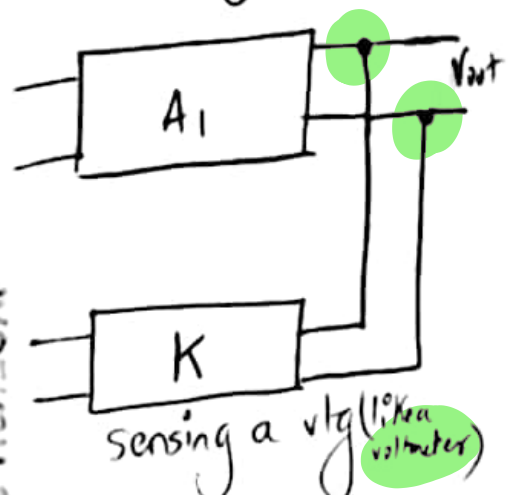


voltage

current

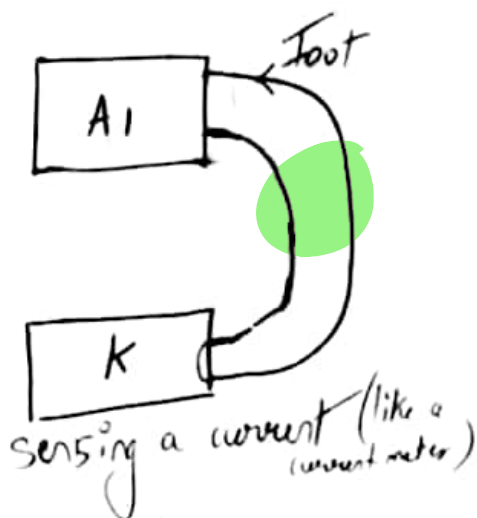


current

Sense mechanism (Sampling)

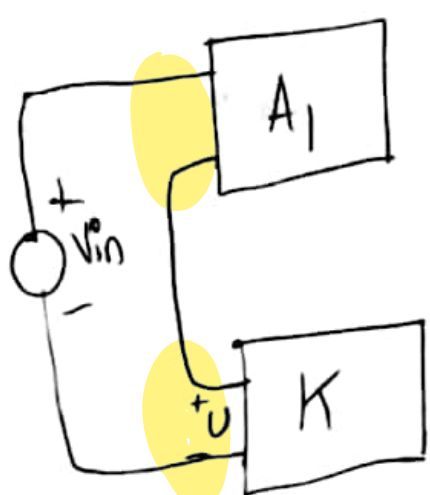



add two vts: Put them in series

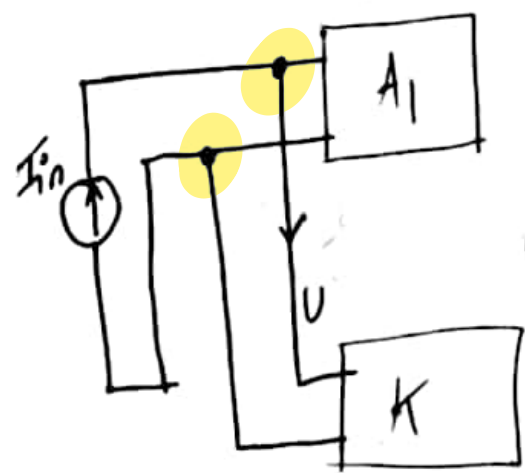

add two currents. Put them in parallel

Return mechanism (Mixing)

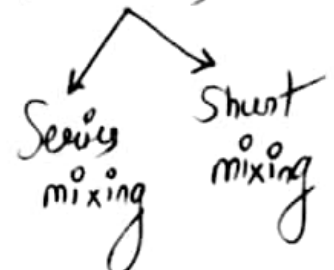

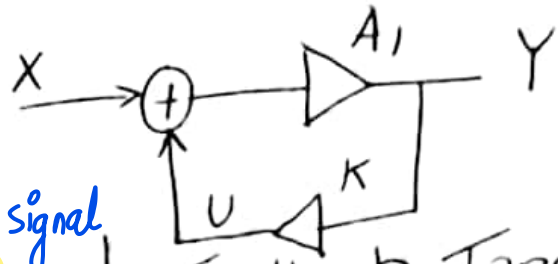

X ^{I/p}	Y ^{o/p}	U ^{flb signal}	Feedback Topology
V	V	V	① Voltage-Voltage Feedback <small>what we sense at the o/p output what we shunt to o/p input</small>
I	V	I	② (shunt-series feedback) ③ <u>Voltage-Series feedback</u> Voltage-current feedback (shunt-shunt feedback) <u>Voltage-shunt feedback</u>
V	I	V	(current-voltage feedback) (series-series feedback) <u>Current-series feedback</u>
I	I	I	(current-current feedback) (series-shunt feedback) <u>Current-shunt feedback</u>

→ Why 4 flb Topologies?


Negative flb gives us interesting & different features for these 4 flb topologies.

INDERJIT SINGH


Objective: To find the closed-loop gain and the closed-loop input & o/p impedances.

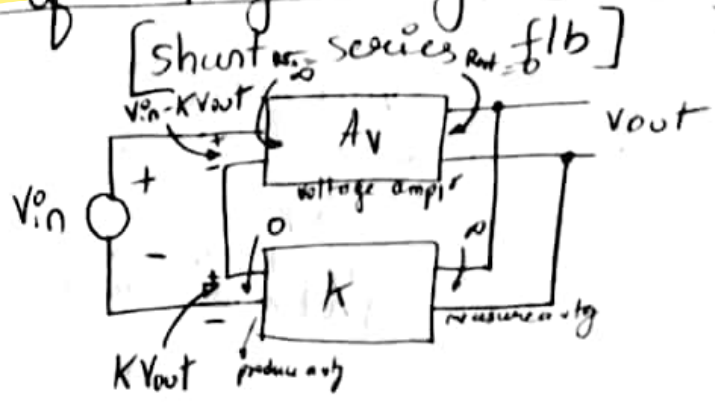V. important *Ring* *A_f* *R_{out}*

Analysis of Voltage-Voltage feedback: (Voltage-series) topology



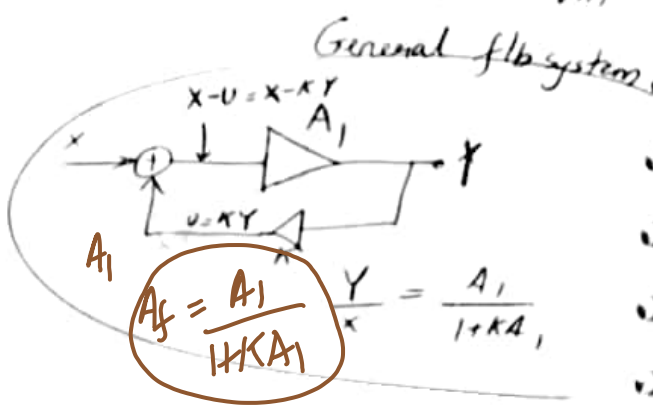
open loop gain = A_v
closed loop gain = $\frac{V_{out}}{V_{in}}$



$V_{out} = A_v (V_{in} - K V_{out})$
 $V_{out} + A_v K V_{out} = A_v V_{in}$
 $V_{out} (1 + K A_v) = A_v V_{in}$

$A_{vf} \rightarrow \frac{V_{out}}{V_{in}} = \frac{A_v}{1 + K A_v} \rightarrow$ closed-loop gain

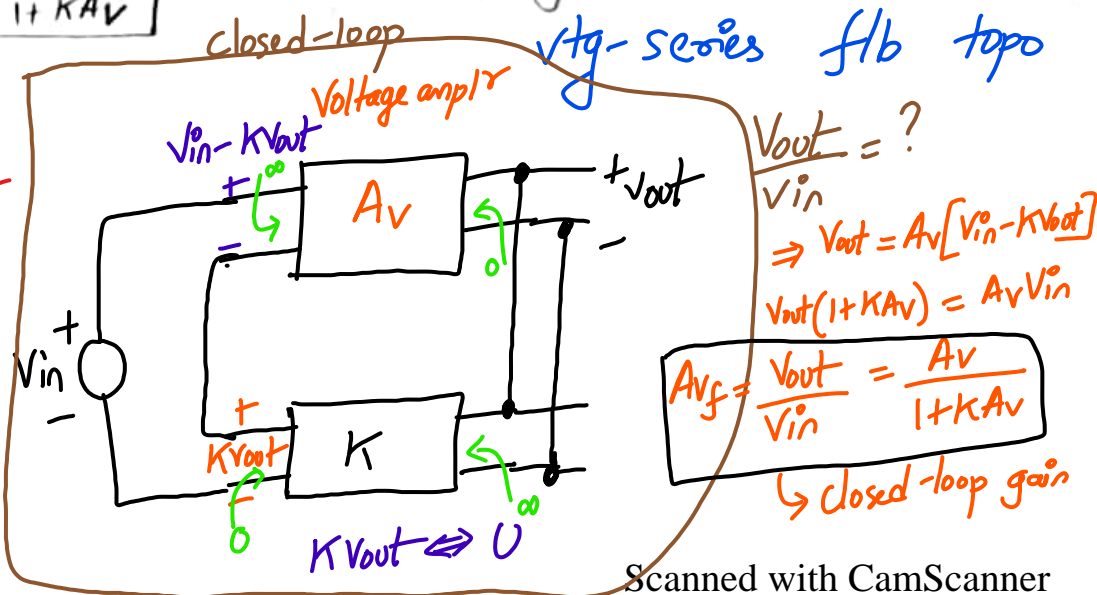$V_{in} \rightarrow [A_v] \rightarrow V_{out}$
open-loop gain
 $A_v = \frac{V_{out}}{V_{in}}$



$\frac{V_{out}}{V_{in}} = ?$
 $\Rightarrow V_{out} = A_v [V_{in} - K V_{out}]$
 $V_{out} (1 + K A_v) = A_v V_{in}$
 $A_{vf} = \frac{V_{out}}{V_{in}} = \frac{A_v}{1 + K A_v}$
closed-loop gain