


# Need and Principle of DSBSC

**Conventional AM (DSBFC) requires more bandwidth.**


**In DSBFC wave more power is consumed in carrier. It does not carry any information.**

**Sideband carries same information.**


# Single Sideband systems

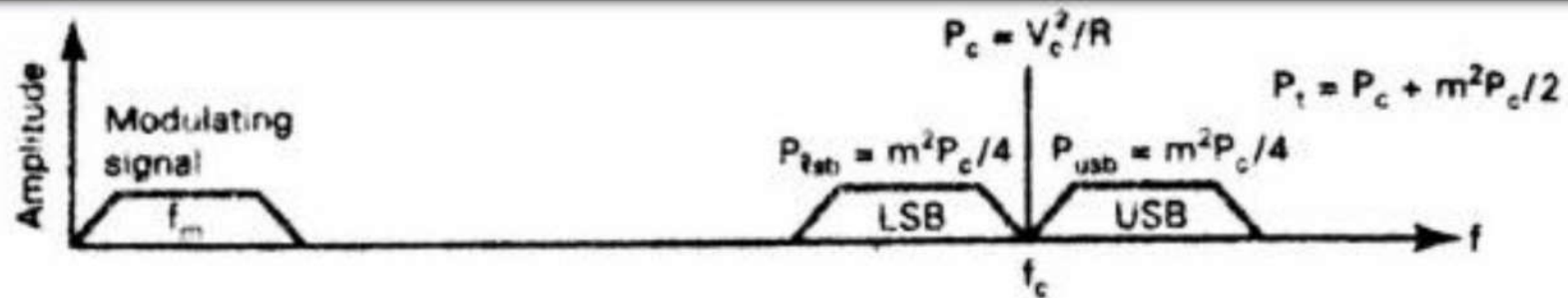

(a)

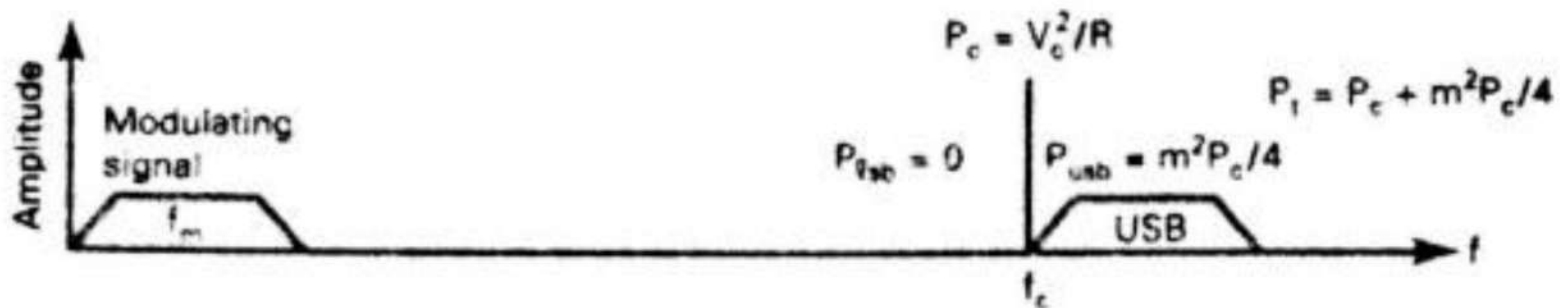


(b)

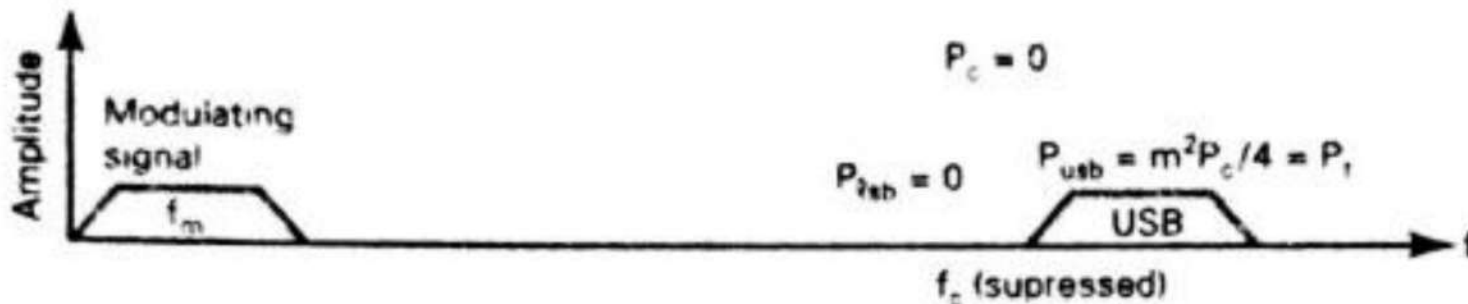


(c)


# Single Sideband systems

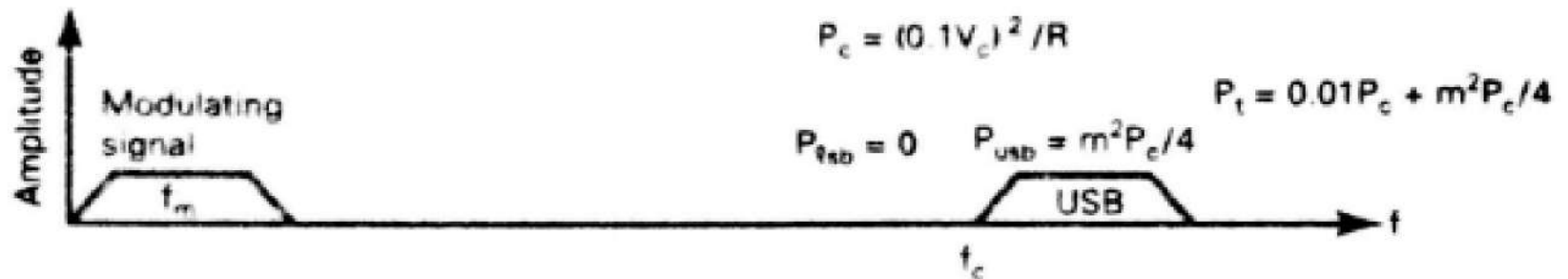

(d)

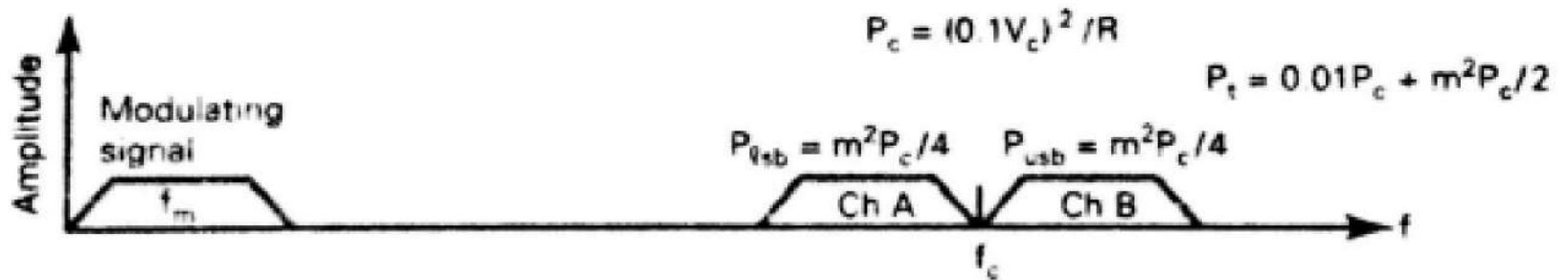


(e)

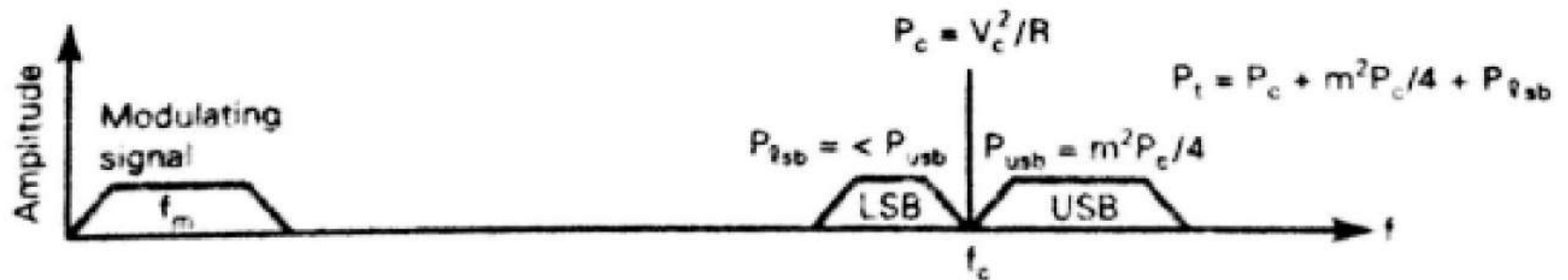


(f)



# DSBSC Wave

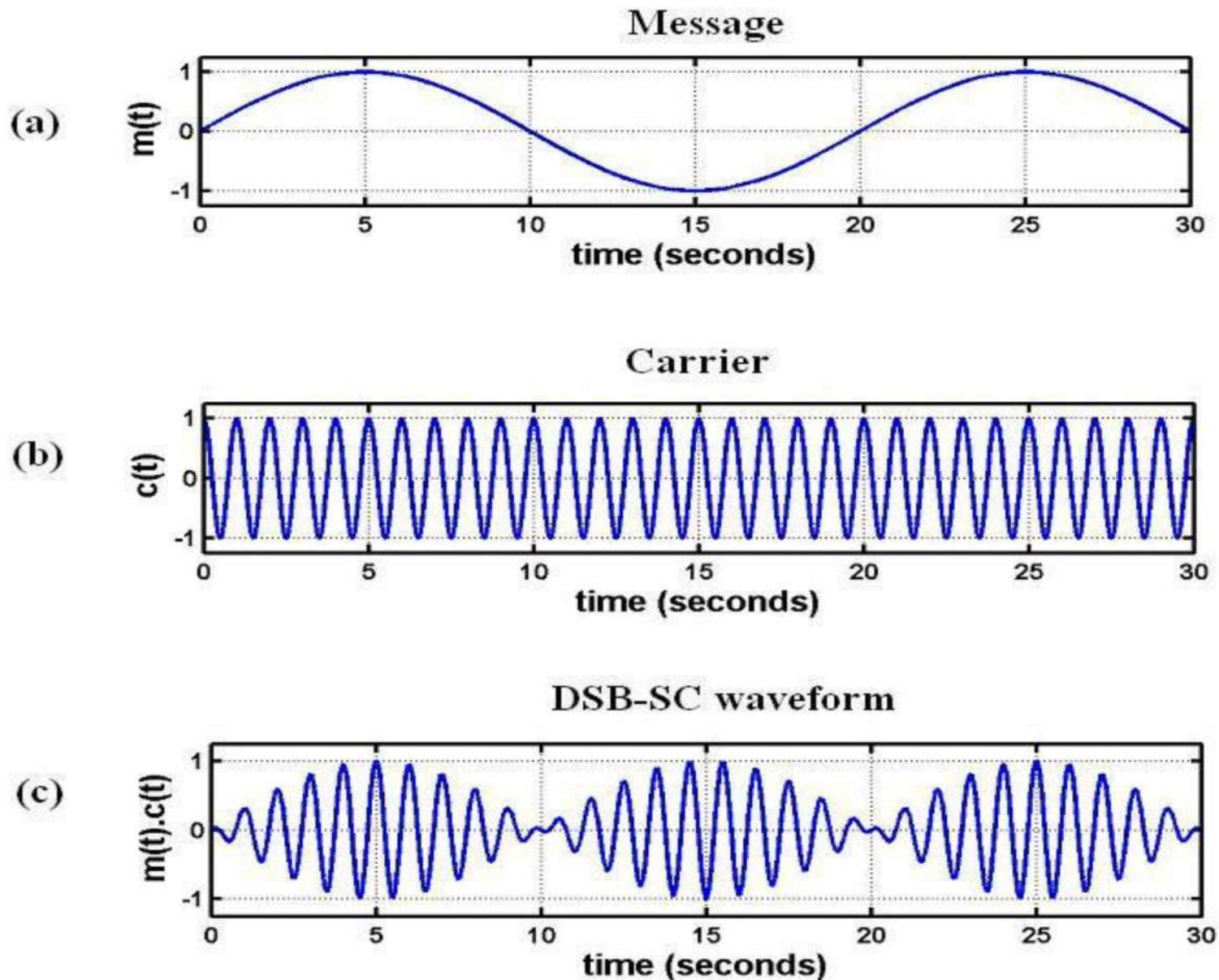


# SSBFC Wave

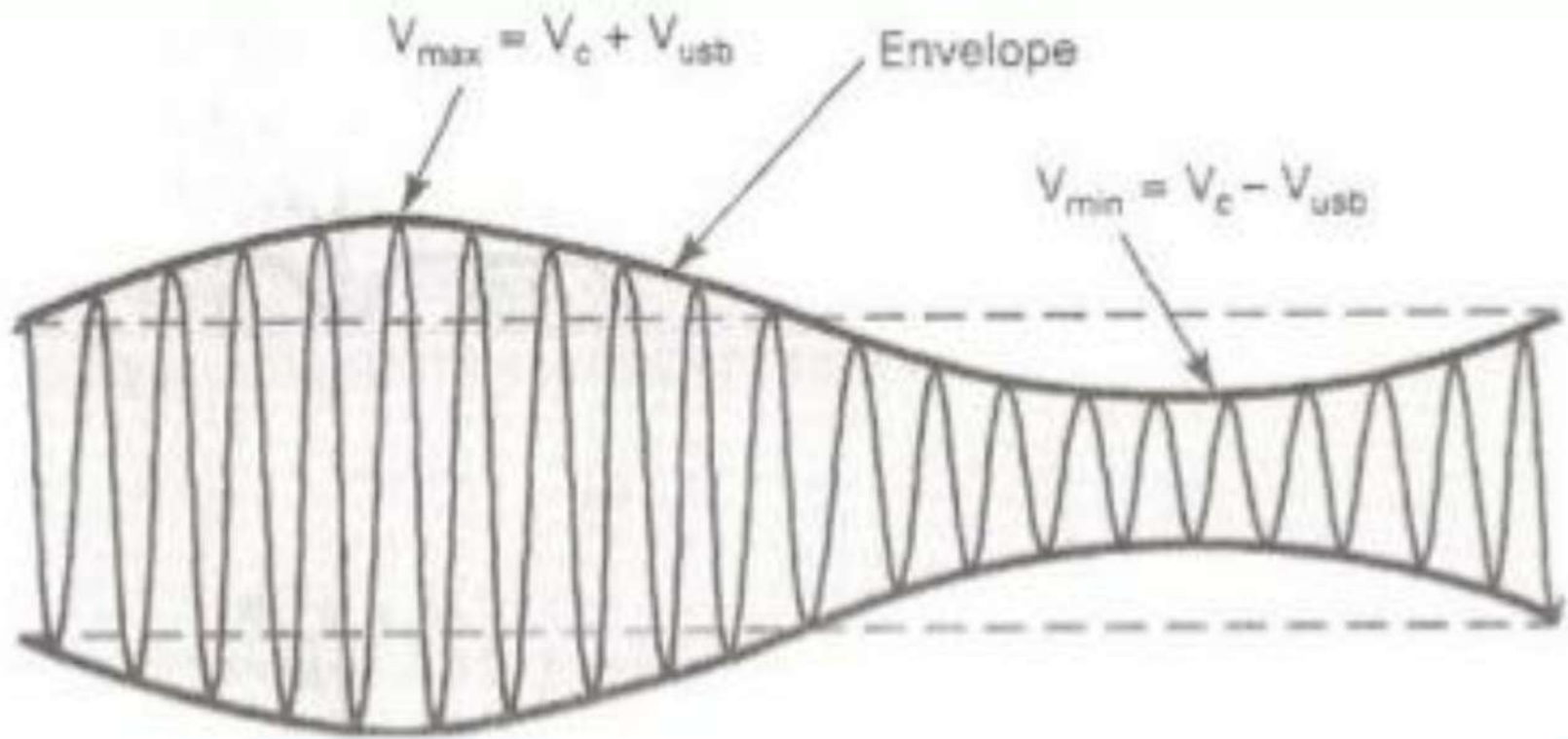


# SSBSC Wave

$$V_p = V_{usf}$$

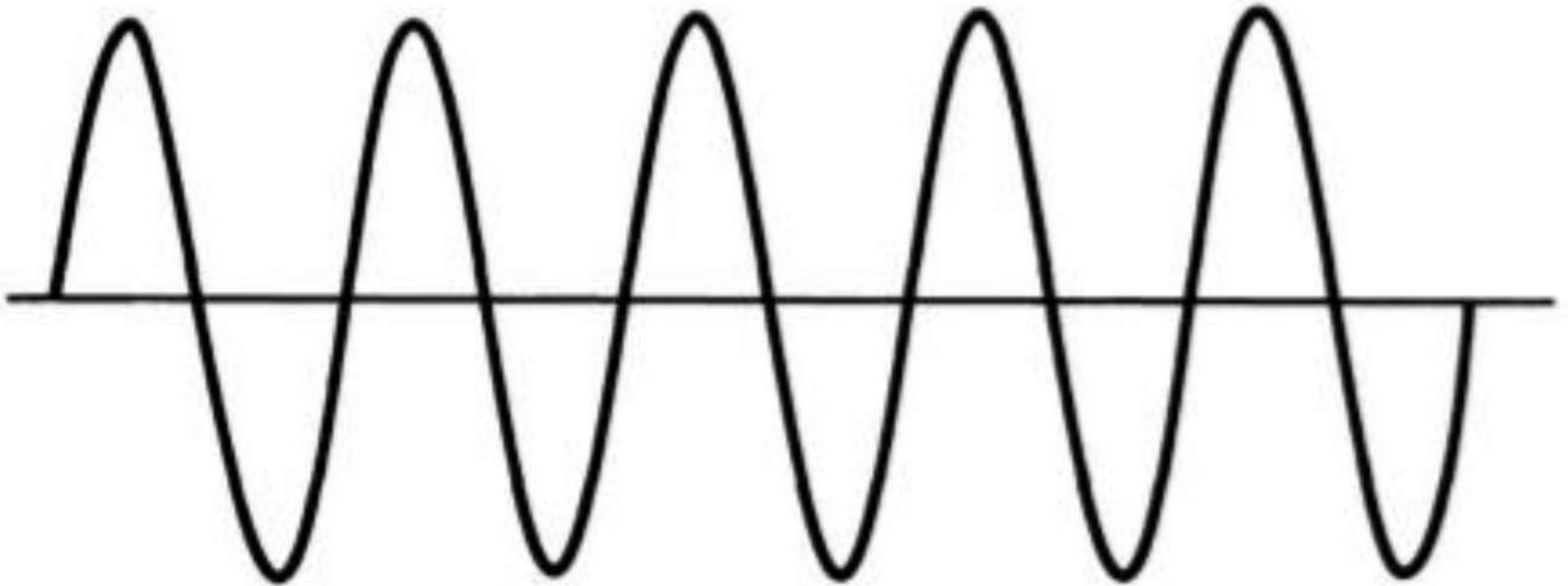

# Basic Principle of DSBSC wave

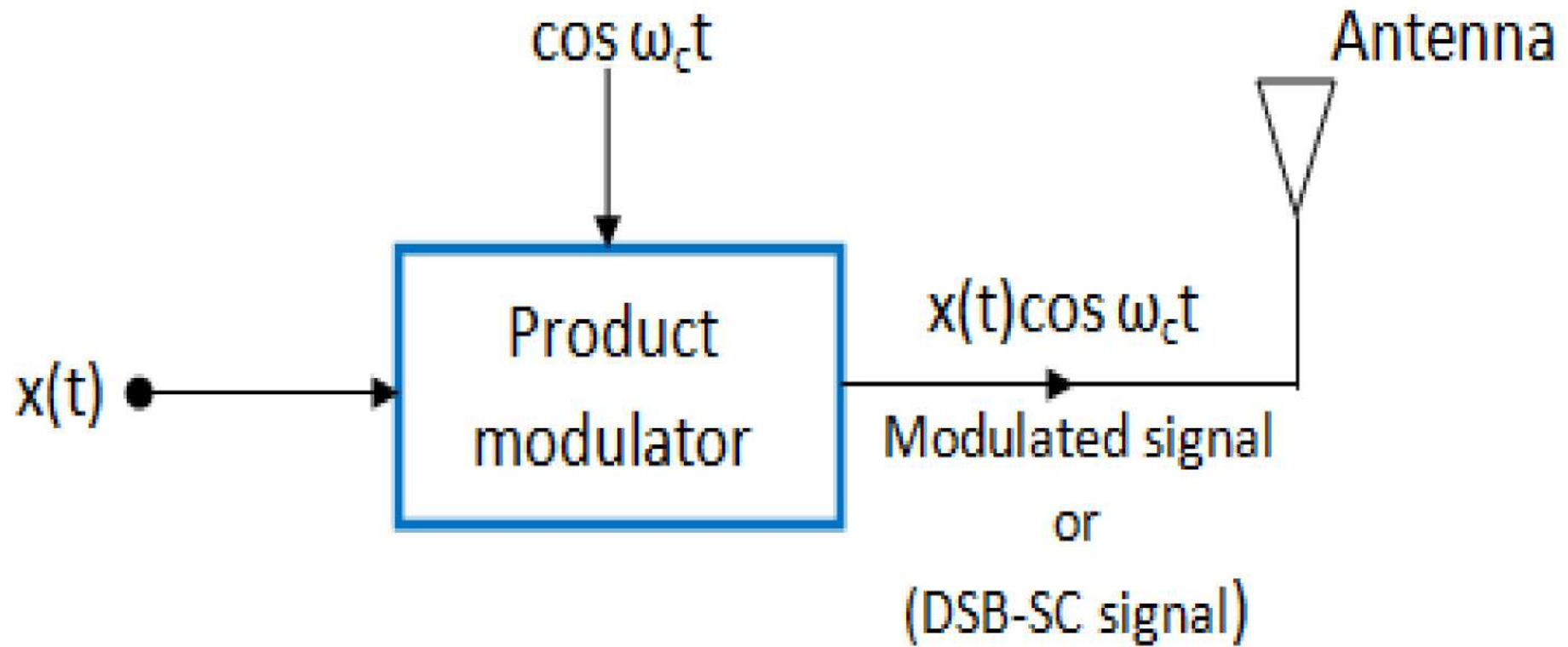

$$x(t) \cos \omega_c(t) \leftrightarrow \frac{1}{2} [X(\omega - \omega_c) + X(\omega + \omega_c)]$$



# Basic Principle of DSBSC wave

$$V_{am}(t) = [(1 + m \sin(2\pi f_m t))][V_c \sin(2\pi f_c t)]$$


- **If constant component is removed from the modulating signal then,**

$$V_{am}(t) = [m \sin(2\pi f_m t)][V_c \sin(2\pi f_c t)]$$



$$V_{am}(t) = \frac{mV_c}{2} \cos[2\pi(f_c - f_m)t] - \frac{mV_c}{2} \cos[2\pi(f_c + f_m)t]$$





# DSBSC Generation- Ring Modulator

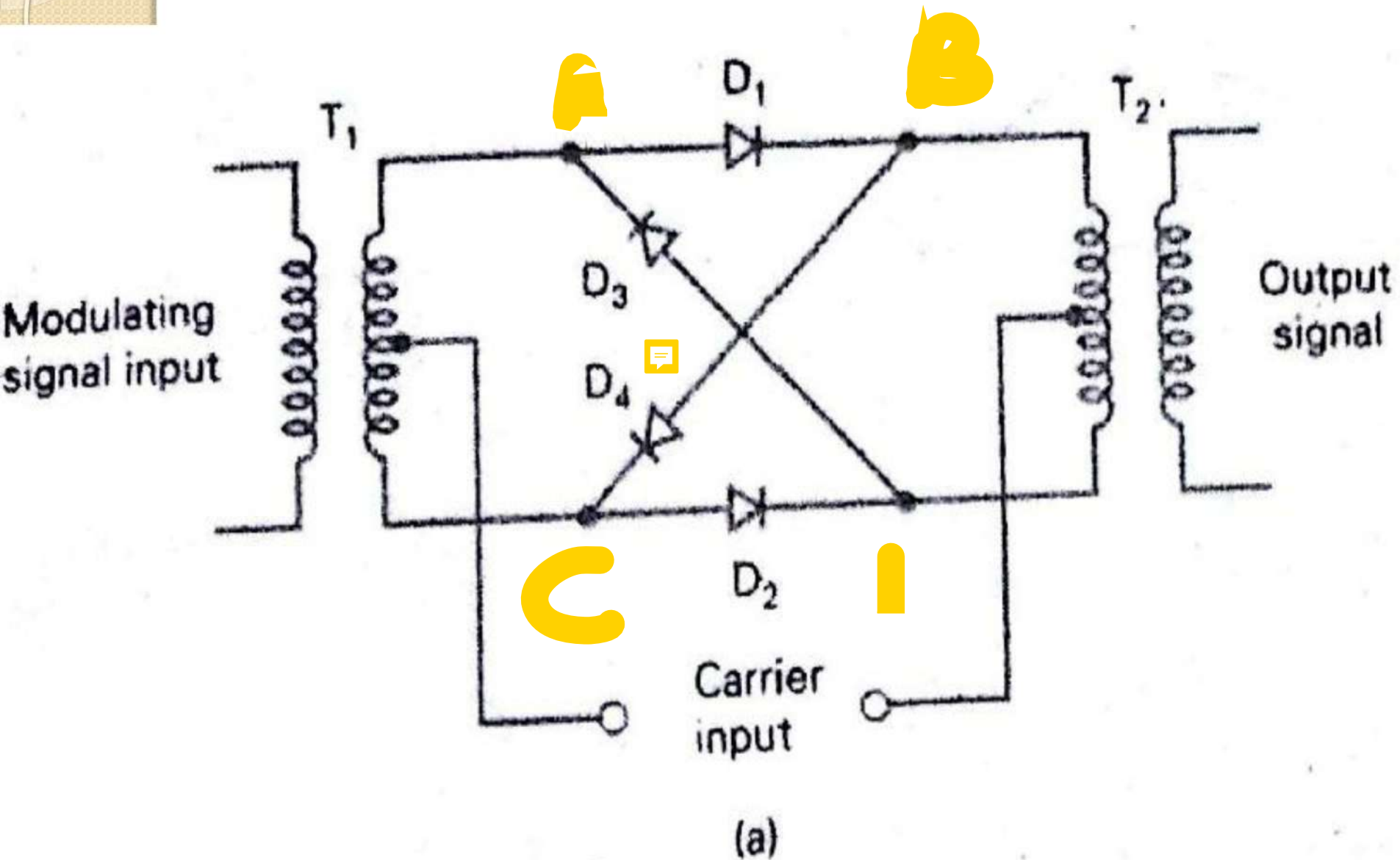


# DSBSC Generation- Ring Modulator

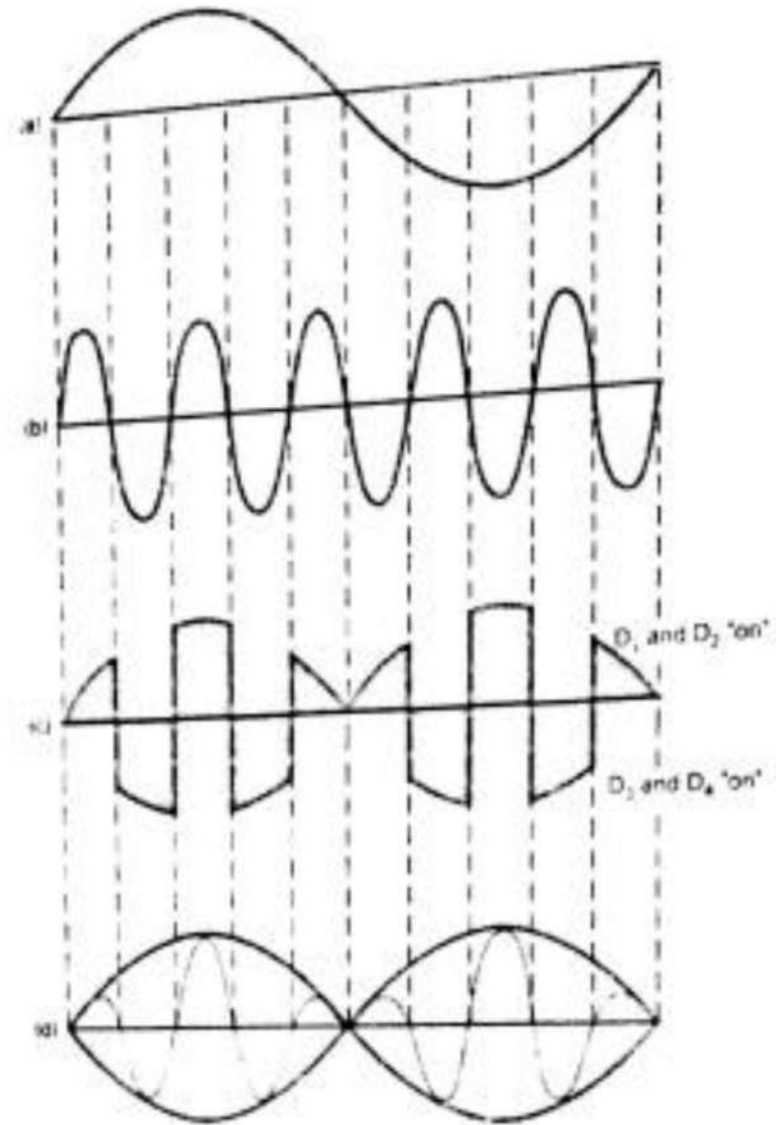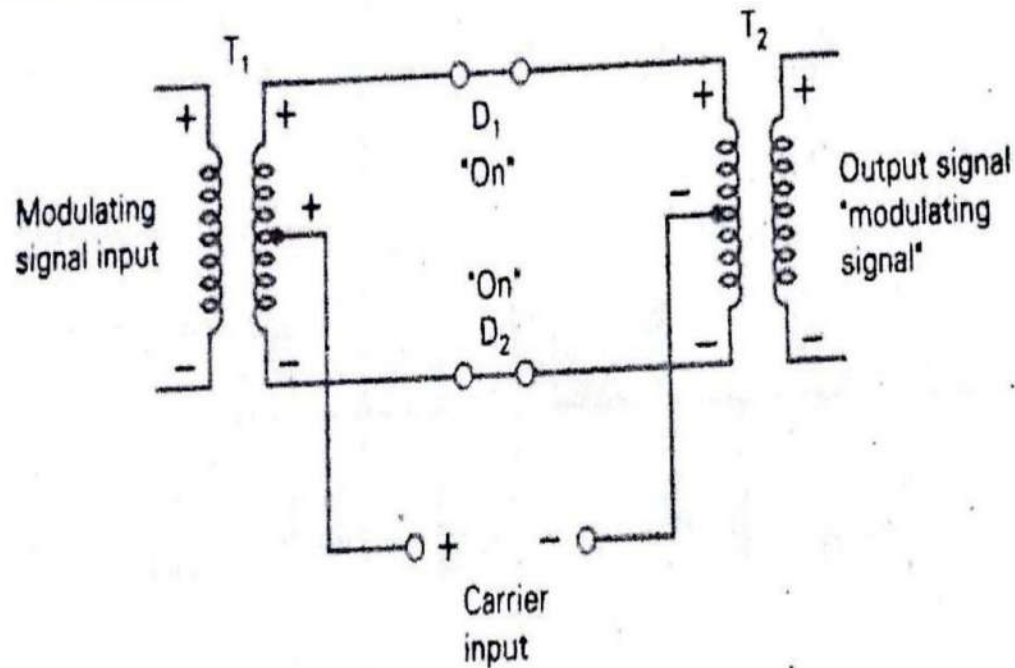

# DSBSC Generation- Ring Modulator

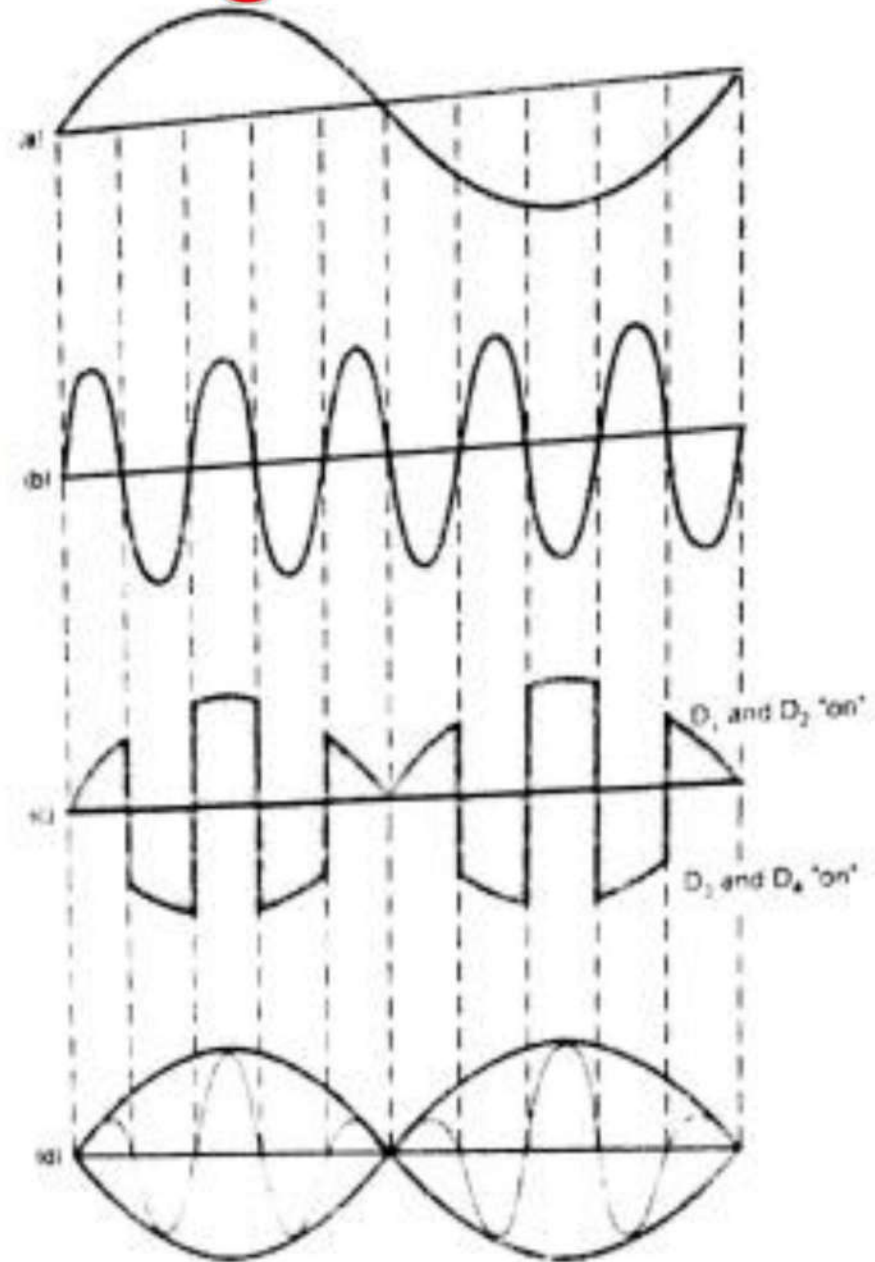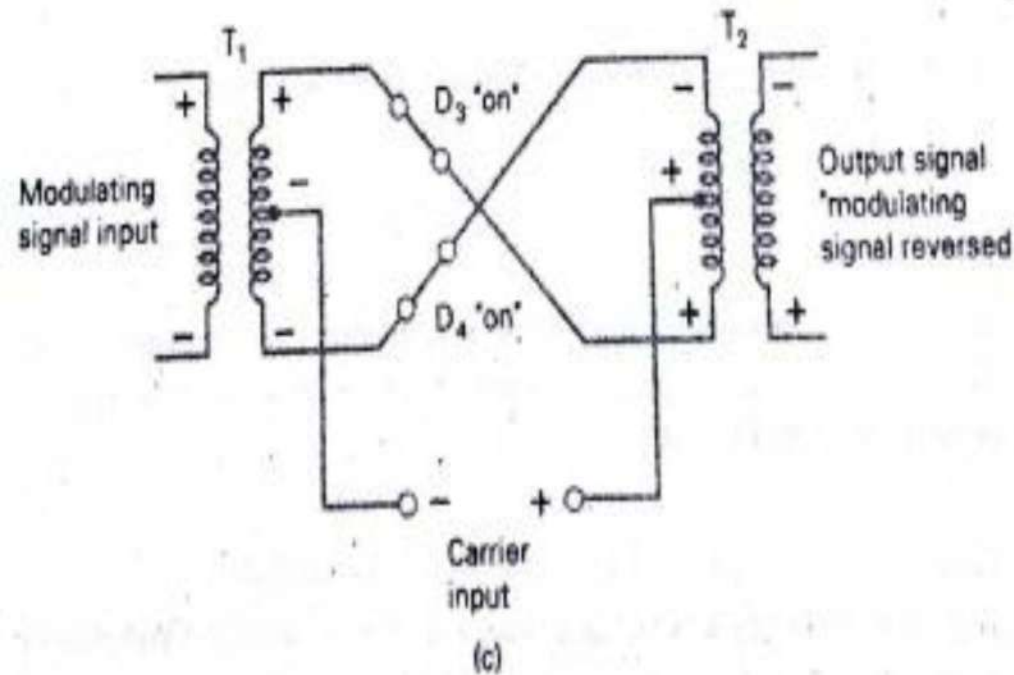


# DSBSC Generation- Balanced Modulator

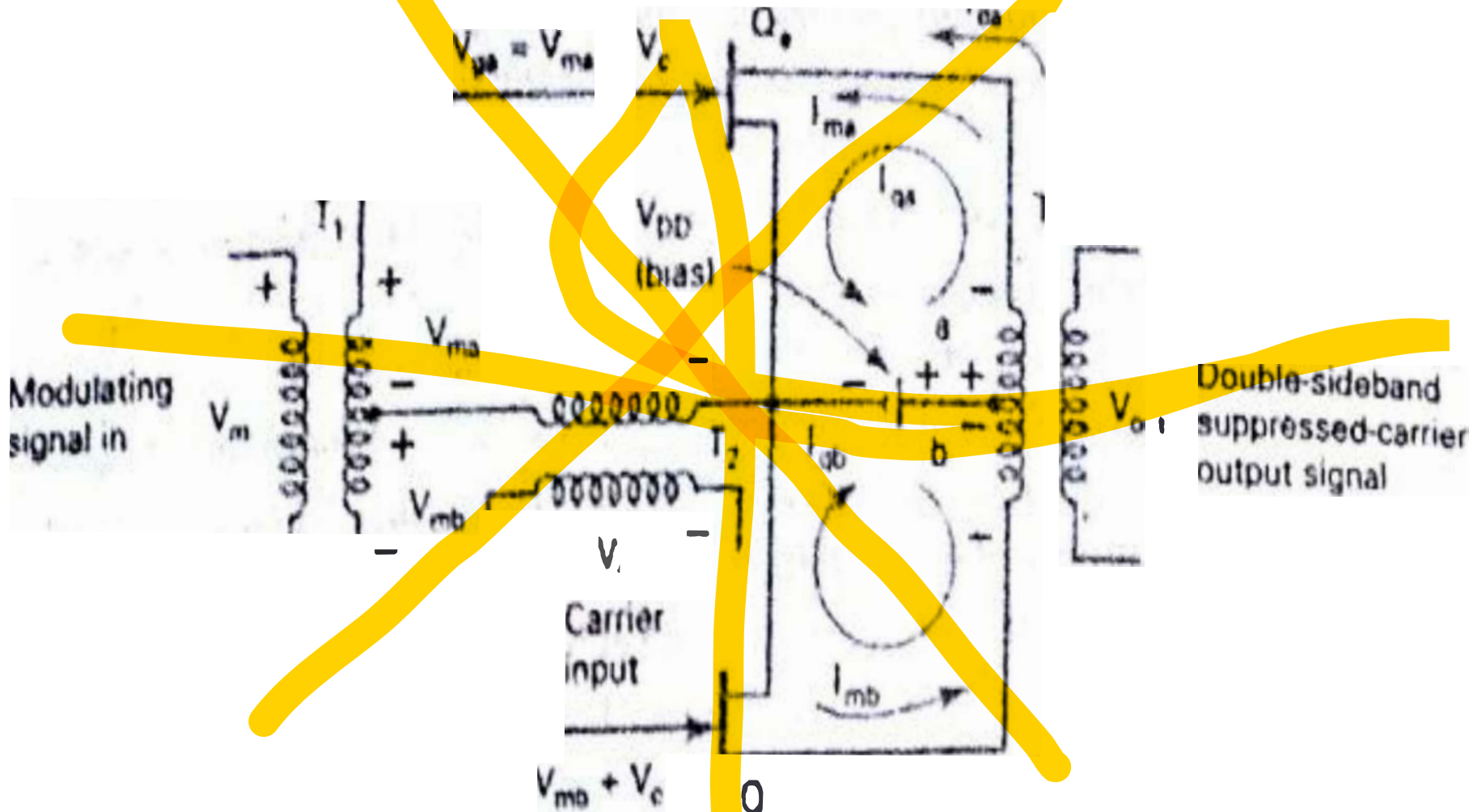



# DSBSC Generation- Balanced Modulator

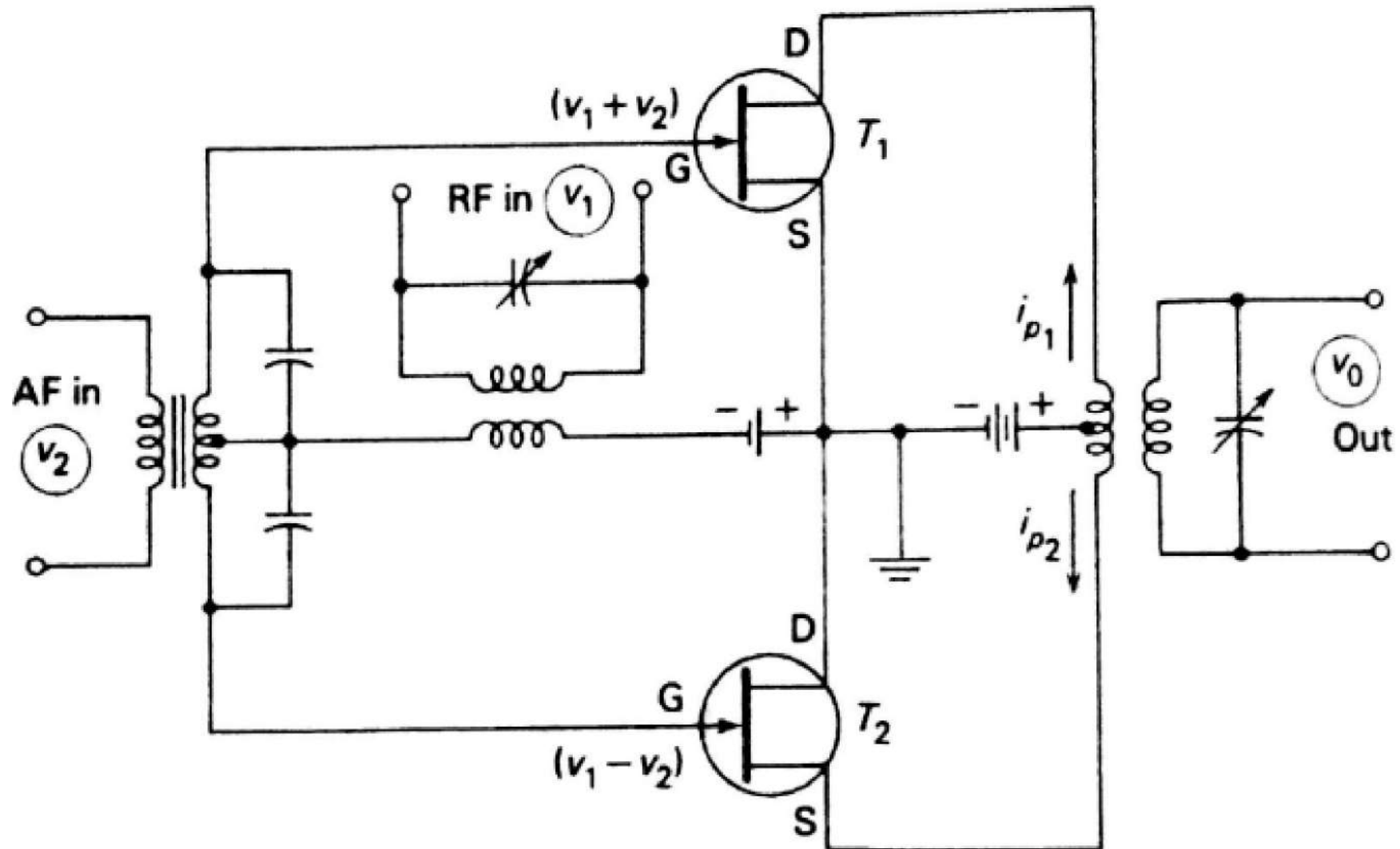

# DSBSC Generation- Balanced Modulator

$$\begin{aligned} i_{d_1} &= a + b(v_1 + v_2) + c(v_1 + v_2)^2 \\ &= a + bv_1 + bv_2 + cv_1^2 + cv_2^2 + 2cv_1v_2. \end{aligned} \quad (4-9)$$

$$\begin{aligned} i_{d_2} &= a + b(v_1 - v_2) + c(v_1 - v_2)^2 \\ &= a + bv_1 - bv_2 + cv_1^2 + cv_2^2 - 2cv_1v_2 \end{aligned} \quad (4-10)$$

As previously indicated, the primary current is given by the difference between the individual drain currents. Thus

$$i_1 = i_{d_1} - i_{d_2} = 2bv_2 + 4cv_1v_2 \quad (4-11)$$

# DSBSC Generation- Balanced Modulator

We may now represent the carrier voltage  $v_1$  by  $v_c \sin \omega_c t$  and the modulating voltage  $v_2$  by  $V_m \sin \omega_m t$ . Substituting these into Equation (4-11) gives

$$\begin{aligned} i_1 &= 2bV_m \sin \omega_m t + 4cV_m V_c \sin \omega_c t \sin \omega_m t \\ &= 2bV_m \sin \omega_m t + 4cV_m V_c \frac{1}{2} [\cos (\omega_c - \omega_m)t - \cos (\omega_c + \omega_m)t] \end{aligned} \quad (4-12)$$


The output voltage  $v_0$  is proportional to this primary current. Let the constant of proportionality be  $\alpha$ . Then

$$\begin{aligned} v_0 &= \alpha i_1 \\ &= 2\alpha b V_m \sin \omega_m t + 2\alpha c V_m V_c [\cos (\omega_c - \omega_m)t - \cos (\omega_c + \omega_m)t] \end{aligned}$$

Simplifying, we let  $P = 2\alpha b V_m$  and  $Q = 2\alpha c V_m V_c$ . Then

$$v_0 = \underbrace{P \sin \omega_m t}_{\text{Modulation frequency}} + \underbrace{Q \cos (\omega_c - \omega_m)t}_{\text{Lower sideband}} - \underbrace{Q \cos (\omega_c + \omega_m)t}_{\text{Upper sideband}} \quad (4-13)$$

# DSBSC Detection (Demodulation)

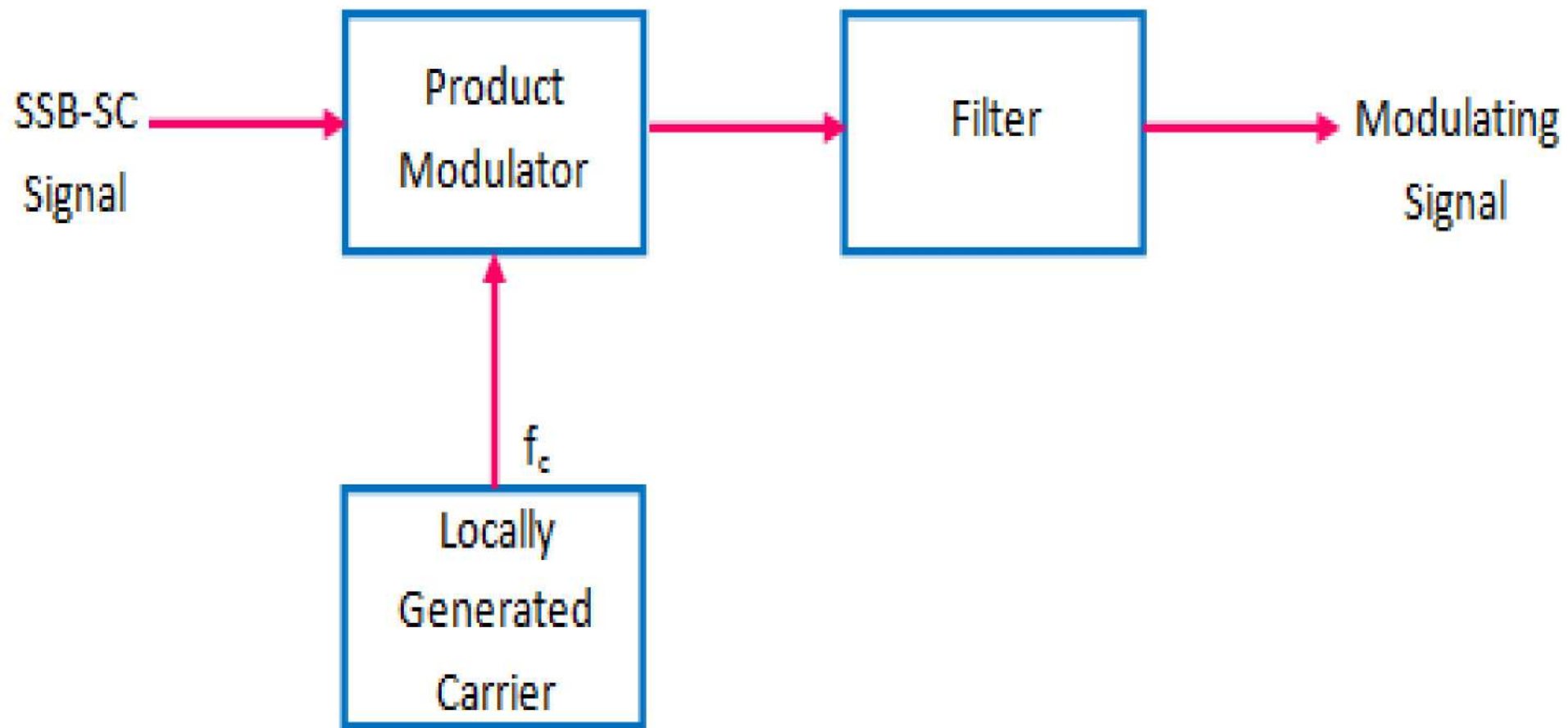



# Mathematical Analysis

Let the output of the local oscillator be given by,

$$c'(t) = \cos(2\pi f_c t + \phi) \quad \dots(3.92)$$

Thus its amplitude is 1 (unity), frequency is  $f_c$  and the phase difference is arbitrary equal to  $\phi$ . This phase difference has been measured with respect to the original carrier  $c(t)$  at the DSB-SC generator. Therefore, the output of the product modulator is given by,

$$m(t) = s(t) \cdot c'(t) \quad \dots(3.93)$$

$$s(t) = \text{DSB-SC input} = x(t) \cdot E_c \cos(2\pi f_c t)$$

and

$$c'(t) = \text{Local carrier} = \cos(2\pi f_c t + \phi)$$

or

$$m(t) = x(t) \cdot E_c \cos(2\pi f_c t) \cos(2\pi f_c t + \phi)$$

Therefore,

$$m(t) = x(t) \cdot E_c \cos(2\pi f_c t + \phi) \cos(2\pi f_c t) \quad \dots(3.94)$$

$$\text{But, } \cos A \cos B = \frac{1}{2} [\cos(A+B) + \cos(A-B)]$$

$$\text{Hence, } \cos(2\pi f_c t + \phi) \cos(2\pi f_c t) = \frac{1}{2} [\cos(2\pi f_c t + \phi + 2\pi f_c t) + \cos \phi] = \frac{1}{2} [\cos(4\pi f_c t + \phi) + \cos \phi]$$

# Mathematical Analysis

Thus,


$$m(t) = \frac{1}{2} x(t) E_c [\cos(4\pi f_c t + \phi) + \cos \phi]$$

Therefore,

$$m(t) = \underbrace{\frac{1}{2} E_c \cos \phi x(t)}_{\text{Scaled version of message signal } x(t)} + \underbrace{\frac{1}{2} x(t) E_c \cos(4\pi f_c t + \phi)}_{\text{Unwanted term}}$$

$$v_o(t) = \frac{1}{2} E_c \cos \phi x(t)$$
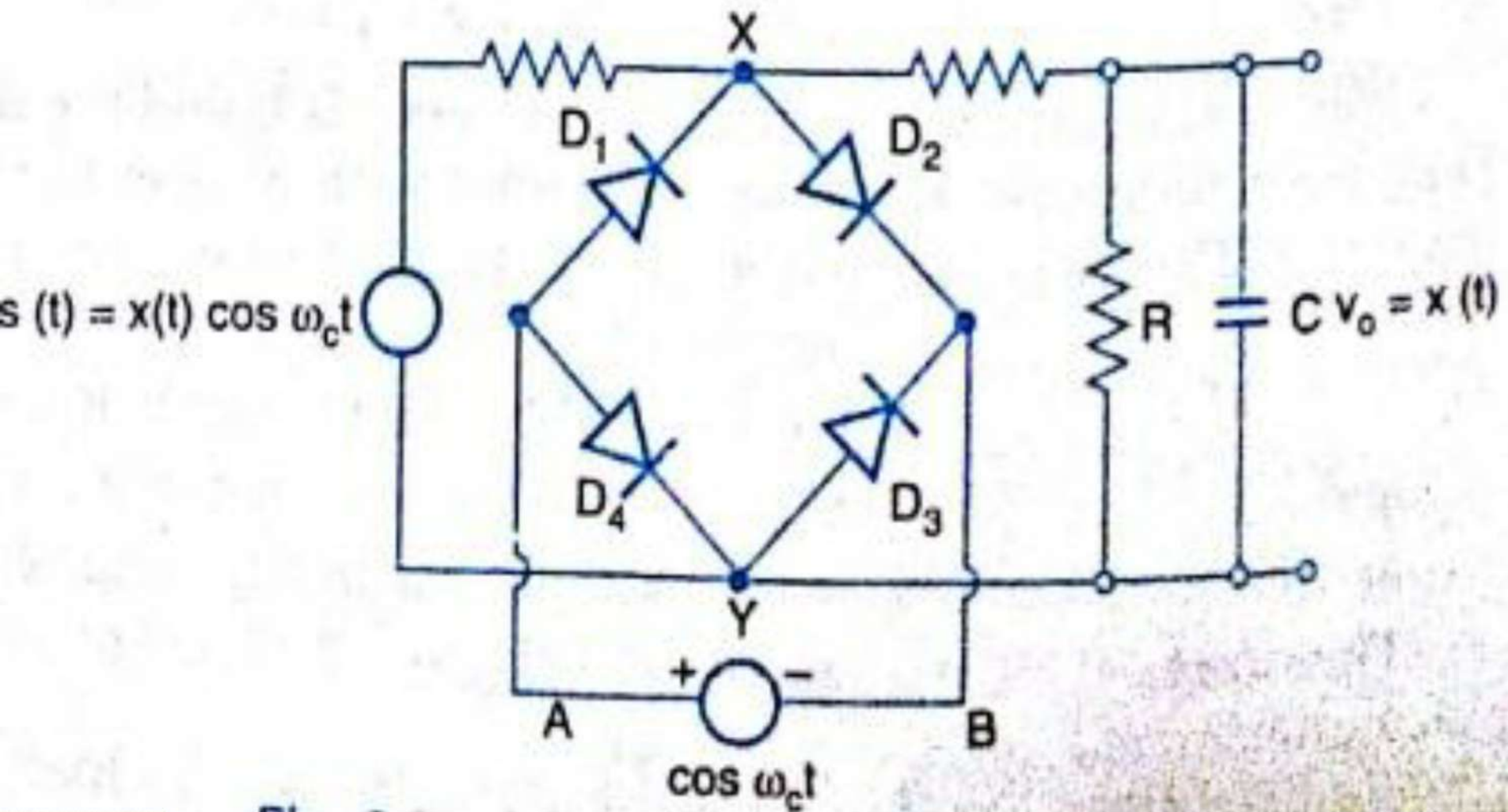
# DSBSC Demodulation by switching (chopper) demodulator





# DSBSC Demodulation by switching (chopper) demodulator

Thus,

$$v_o(t) = s(t) \times \cos \omega_c t$$

or

$$v_o(t) = x(t) \cos \omega_c t \times \cos \omega_c t = x(t) \cos^2 \omega_c t \quad \dots(3.97)$$

or

$$v_o(t) = x(t) \left[ \frac{1 + \cos 2\omega_c t}{2} \right]$$

Therefore,

$$v_o(t) = \frac{x(t)}{2} + \frac{1}{2} \cos(2\omega_c t) \quad \dots(3.98)$$

Taking the Fourier Transform of this expression, we get the spectrum of  $V_o$  as under:

$$F[v_o(t)] = V_o(f) = \frac{1}{2} X(f) + \frac{1}{2} [\delta(f - 2f_c) + \delta(f + 2f_c)]$$



# DSBSC Demodulation by switching (chopper) demodulator

