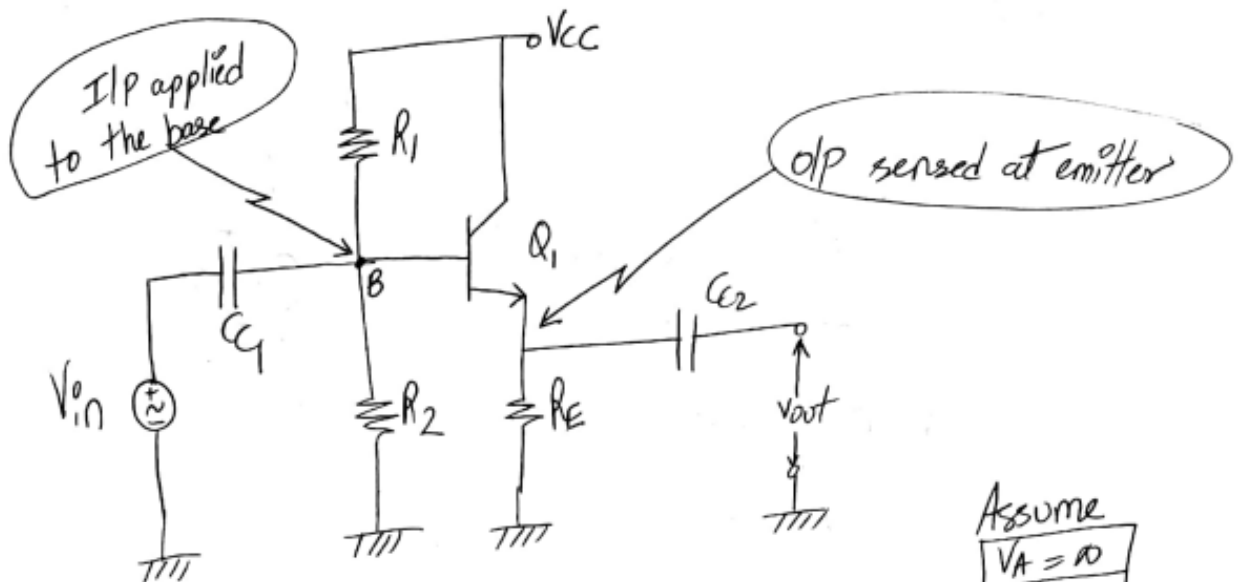


Common Collector BJT amplifier


32

* Common-collector amplifier (npn BJT)
(Emitter follower)



Assume
 $V_A = \infty$
 $r_{e0} = \infty$

Small-signal voltage gain: A_v

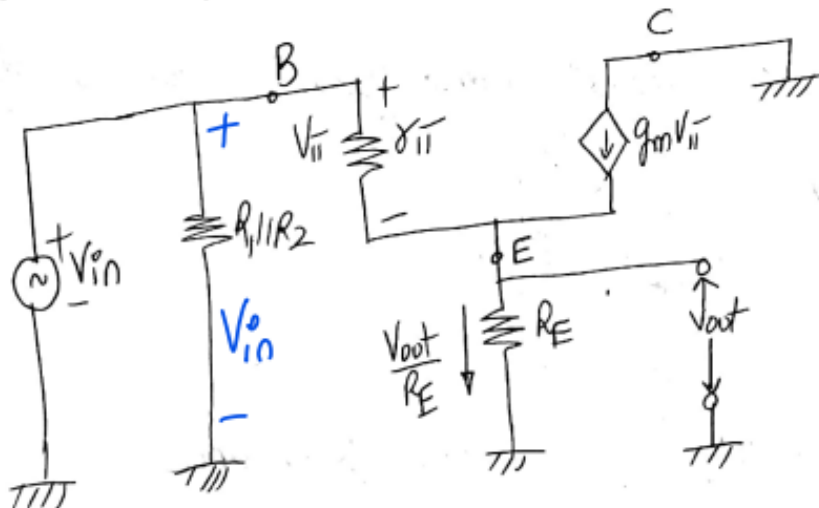

ckt(c): Small-signal equivalent ckt of CC amplifier

From ckt(c), apply KVL to B-E loop,

$$V_{in} = V_{ii} + V_{out} \quad \text{ie} \quad \boxed{V_{ii} = V_{in} - V_{out}} \quad \text{--- (1)}$$

KCL at 'E' node, gives

$$\frac{V_{ii}}{r_{ii}} + g_m V_{ii} = \frac{V_{out}}{R_E}$$

$$\frac{V_{in} - V_{out}}{r_{ii}} + g_m (V_{in} - V_{out}) = \frac{V_{out}}{R_E} \quad (\text{From ①})$$

$$\frac{V_{in}}{r_{ii}} + g_m V_{in} = \frac{V_{out}}{R_E} + g_m V_{out} + \frac{V_{out}}{r_{ii}}$$

$$V_{in} \left(\frac{1}{r_{ii}} + g_m \right) = V_{out} \left[\frac{r_{ii} + g_m r_{ii} R_E + R_E}{r_{ii} R_E} \right]$$

$$V_{in} \left(\frac{1 + g_m r_{ii}}{r_{ii}} \right) = V_{out} \left[\frac{r_{ii} + g_m r_{ii} R_E + R_E}{r_{ii} R_E} \right]$$

But, $g_m r_{ii} = \beta$

$$r_{ii} = \frac{\beta}{g_m}$$

$$V_{in} (1 + \beta) = V_{out} \left[\frac{r_{ii} + (1 + \beta) R_E}{R_E} \right]$$

$$\boxed{\frac{V_{out}}{V_{in}} = \frac{R_E (1 + \beta)}{r_{ii} + (1 + \beta) R_E}}$$

\div & \times Nr & Dr by $(1 + \beta)$

$$\frac{V_{out}}{V_{in}} = \frac{R_E}{\frac{r_{ii}}{(1 + \beta)} + R_E}$$

$$\frac{r_{ii}}{1 + \beta} \approx \frac{r_{ii}}{\beta} = \frac{1}{g_m}$$

$$\text{i.e. } \frac{V_{out}}{V_{in}} \approx \frac{R_E}{\frac{1}{g_m} + R_E} = A_v$$

$$A_v = \frac{R_E}{\frac{1}{g_m} + R_E}$$

→ CC amplifier

let's verbalize the gain formula,

$$A_v = \frac{\text{Resistance tied betn emitter \& ac ground}}{\frac{1}{g_m} + \text{resistance tied betn emitter \& ac gnd}}$$

$$A_v = \frac{g_m R_E}{1 + g_m R_E}$$

is always very close to 1, but always less than unity

i.e. $A_v \leq 1$ for a CC amplifier or emitter follower


→ There is no phase difference betn the i/p & o/p signals in an emitter follower.

→ In this amplifier, i/p signal changes in the base follows the changes in the emitter. Hence, the name of circuit is "emitter follower".

ILP impedance: $Z_i^o(R_{in})$

35

Redrawing ckt(c),

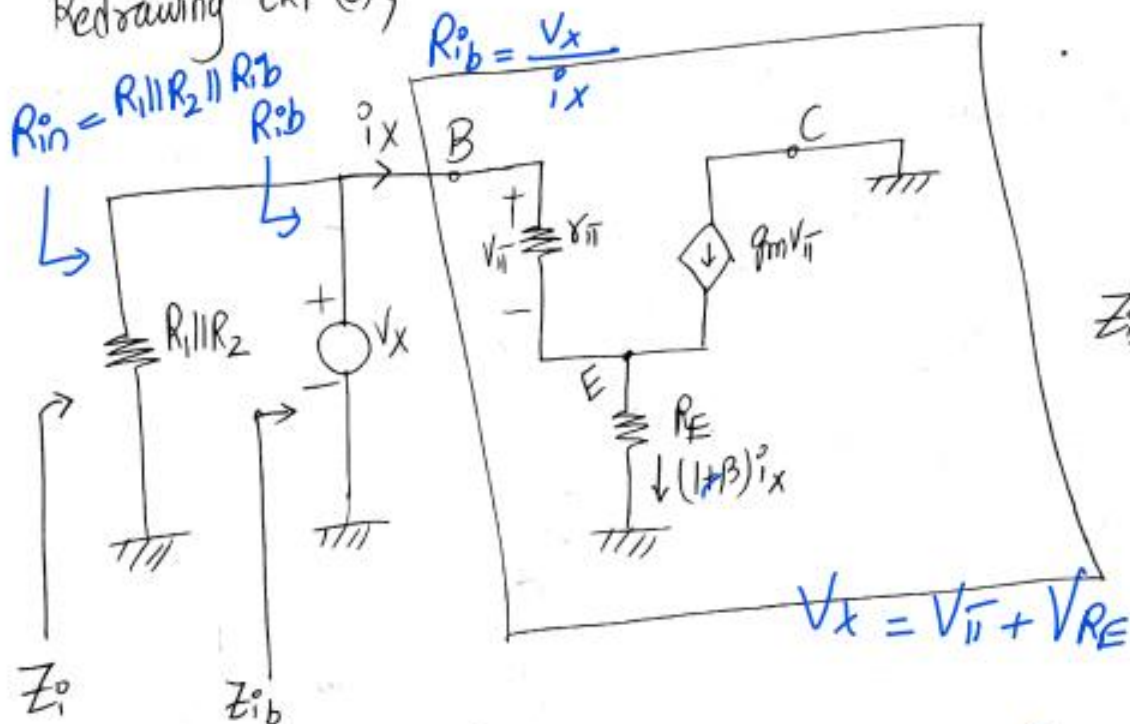

From ckt, $V_{\pi} = i_x r_{\pi}$ ✓

$$i_E = (1+\beta)i_B$$

$$\text{i.e. } g_m V_{\pi} = g_m i_x r_{\pi}$$

Current through 'B' is i_x

Current through 'E' is $(1+\beta)i_x$

KVL at B-E loop, gives

$$V_x = V_{\pi} + \text{voltage drop across } R_E$$

$$V_x = i_x r_{\pi} + (1+\beta) i_x R_E$$

$$\text{so } Z_{ib} = \frac{V_x}{i_x} = r_{\pi} + (1+\beta) R_E$$

$$R_{in} = R_1 \parallel R_2 \parallel R_{i_b}$$

$$Z_o = R_1 \parallel R_2 \parallel [r_{ii} + (1+\beta)R_E]$$

R_{in} or Z_i

"high"



high i/p impedance
in CC amplifier

" r_{ii} "

36

* Output impedance: Z_o (Root)

Redrawing ckt(c) with $V_{in}=0$

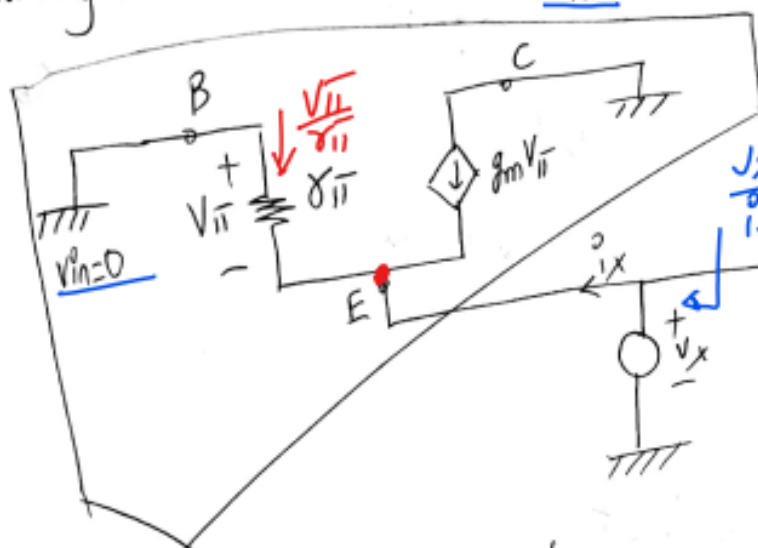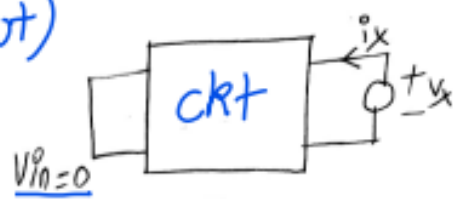

$$\frac{v_x}{i_x} = R_o'$$

$$R_{out} = R_o' \parallel R_E$$

From above ckt, $V_{ii} = -V_x$

KCL at 'E' node gives,

$$\frac{V_{ii}}{r_{ii}} + g_m V_{ii} + i_x = 0$$

$$-\frac{V_x}{r_{ii}} - g_m V_x = -i_x$$

$$V_x \left(\frac{1}{r_{ii}} + g_m \right) = i_x$$

$$i_x^o = V_x \left(\frac{g_m r_{ii} + 1}{r_{ii}} \right)$$

$$g_m r_{ii} = \beta$$

$$i_x^o = V_x \left(\frac{1 + \beta}{r_{ii}} \right)$$

$$1 + \beta \approx \beta$$

$$i_x^o = V_x \left(\frac{\beta}{r_{ii}} \right)$$

$$\frac{\beta}{r_{ii}} = g_m$$

$$i_x^o = V_x g_m$$

$$\frac{V_x}{i_x^o} = \frac{1}{g_m}$$

$$R_{out} = \frac{1}{g_m} \parallel R_E$$


$$\therefore Z_o = R_E \parallel \frac{1}{g_m}$$

Low output impedance

$A_v \approx 1$
 $R_{in} \approx \text{high}$
 $R_{out} \approx \text{low}$

Application of CC amplifier :-

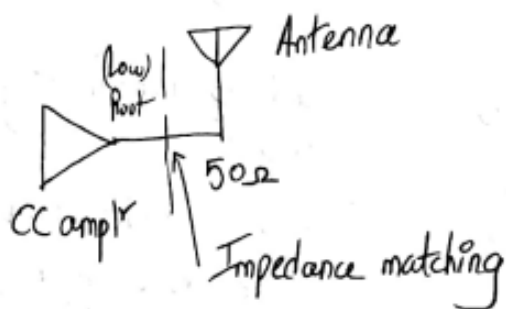- It is used as a buffer betn amplr and o/p stage
- It is used to drive a low impedance antenna or speaker



Comparison of CE, CB, CC amplifier

38

# Comparison of CE, CB and CC amplifiers			
	Common-emitter	Common-base	Common-collector
1. Circuit			
2. I/P applied to	Base terminal	Emitter terminal	Base terminal
3. o/p sensed at	Collector terminal	Collector terminal	Emitter terminal
4. Voltage gain	$A_v = -g_m R_C$ High	$A_v = g_m R_C$ High	$A_v = \frac{g_m R_E}{1 + g_m R_E} \approx 1$ Low
5. I/P impedance	$Z_i = R_1 \parallel R_2 \parallel r_{\pi}$ medium	$Z_i = \frac{1}{g_m} \parallel R_E$ Low	$Z_i = R_1 \parallel R_2 \parallel [r_{\pi} + (1 + \beta) R_E]$ v. high
6. o/p impedance	$Z_o = R_C$ medium	$Z_o = R_C$ medium	$Z_o = \frac{1}{g_m} \parallel R_E$ Low
7. Phase of o/p signal	Out: of Phase with i/p signal	In phase with i/p signal	In phase with i/p signal
8. Application	Common used as inverting voltage amplifiers	1) used as non-inverting amplifier 2) used as a ckt which can be driven by a low impedance source	1) used as a <u>voltage buffer</u> 2) used to <u>drive a low impedance load</u> (eg antenna or speaker)