

AEC 33.2 21/4/22

• Properties of Negative feedback: -

$$\frac{Y}{X} = \frac{A_1}{1 + KA_1} \approx \frac{1}{K} \text{ if } KA_1 \gg 1$$


① Gain Desensitization $\Rightarrow \frac{Y}{X}$ is less sensitive to temperature, supply, etc than A_1 is.

2) Bandwidth Extension: Greater BW for closed-loop system


05

3) Modification of Input and output impedances.

4) Higher Linearity {eg

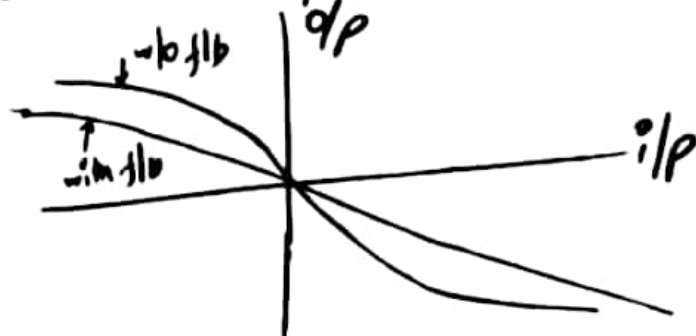





④ Higher Linearity : Diffamp.

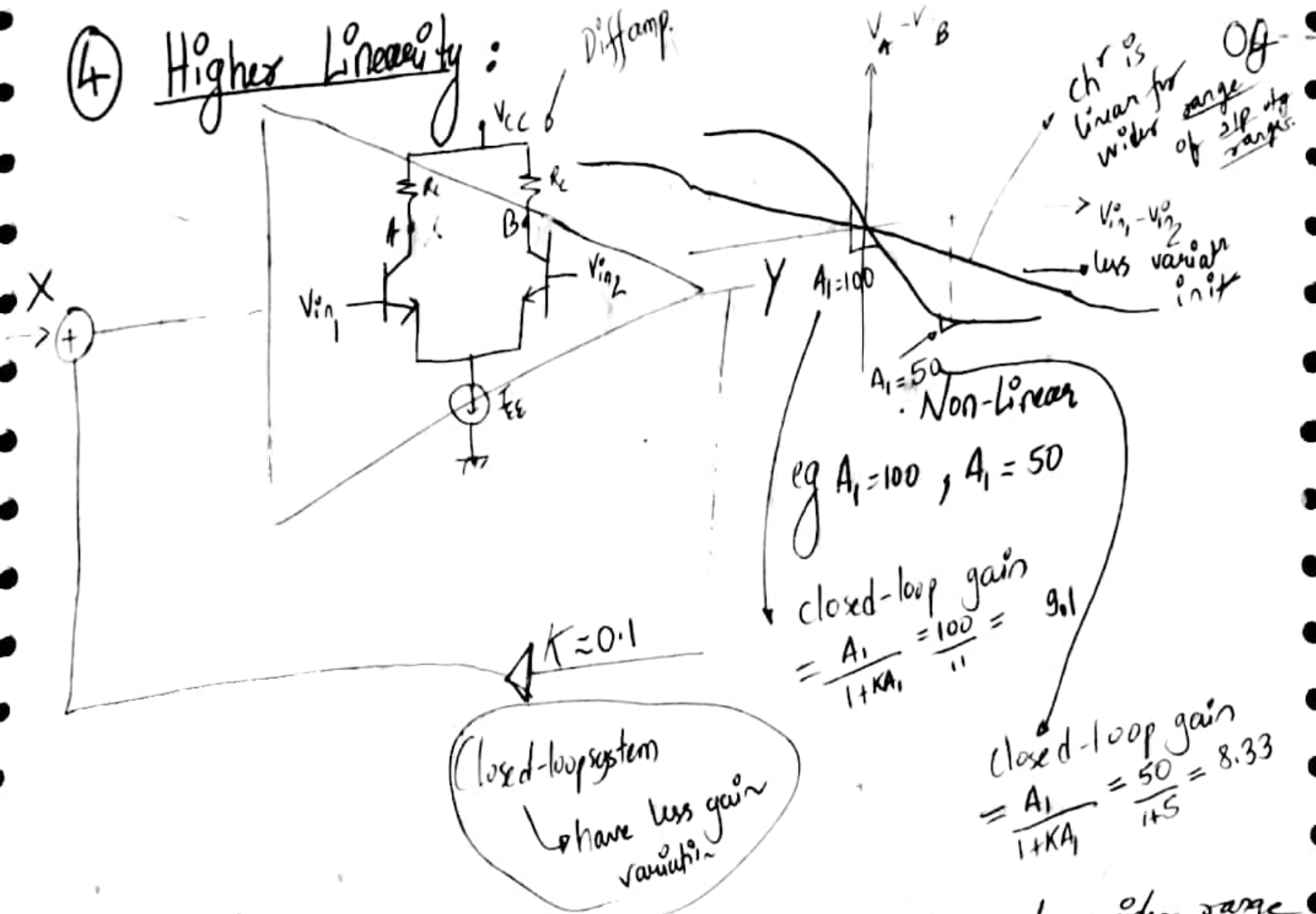


→ Higher Linearity means that characteristics is linear for wider range of ΔP voltages.

• A Few Quick Notes

a) Ideal vs Real sources

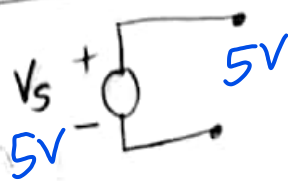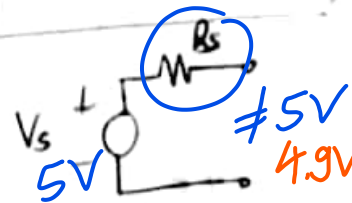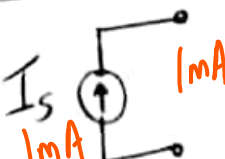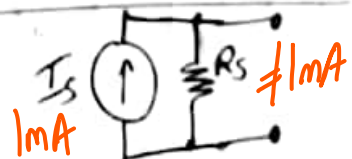	Ideal	Real (Internal resistance)	
Voltage source (const, variable, dependent or indep)			<p>For a good voltage source, R_s is <u>small</u></p>
Current source			<p>For a good current source, R_s is <u>high</u></p>

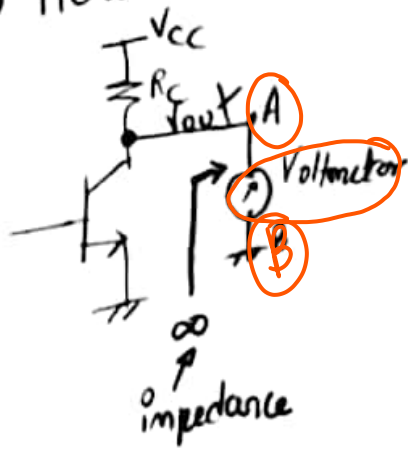b) How do we measure a voltage or a current?




~ Voltmeter should measure the voltage without disturbing or loading the circuit (w/o changing the gain of the ckt)

~ That is possible \rightarrow only if the impedance of the voltmeter is infinite.

~ So, this circuit doesn't feel that we connected something betn A & B

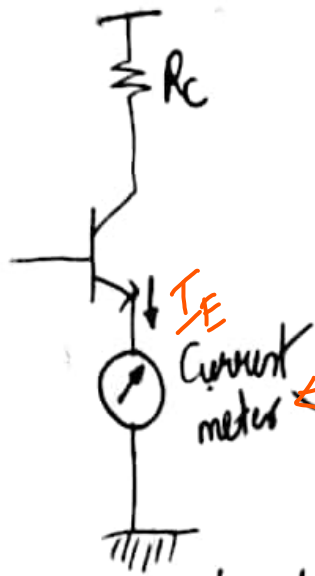~ So, an ideal voltmeter has an infinite impedance.
So any device or ckt that is suppose to measure voltage must have an ∞ i/p impedance.
high in practise.



→ We don't want to insert a 02 disturb the ckt while inserting the current meter.

impedance should be low


Any device or ckt wants to measure current or sense a current must have low impedance.

Review of topics:-

- Properties of Feedback:





- "Good" Voltage and Current sources:-

- Sensing Voltages and currents:-

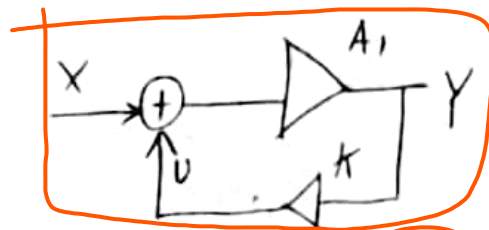

$$\frac{Y}{X} = \frac{A_1}{1 + KA_1} \approx \frac{1}{K}$$

$\rightarrow A_f$

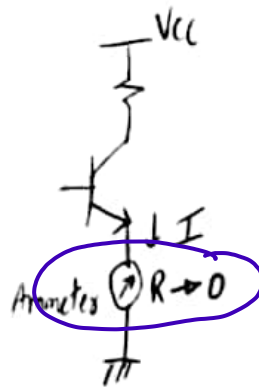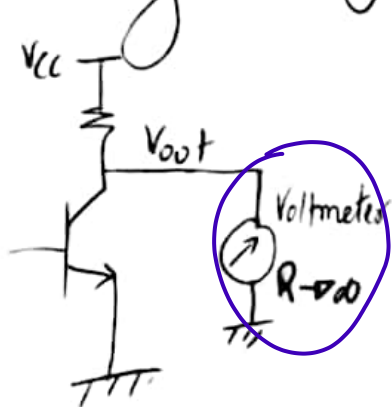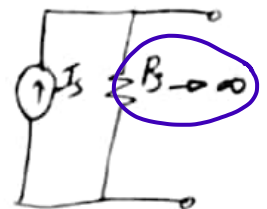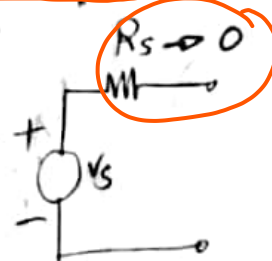


ANDESH SINGH

Types of Amplifiers:-

$V_{in} \rightarrow V_{out} \rightarrow A_v$


1. Voltage amplifiers:-

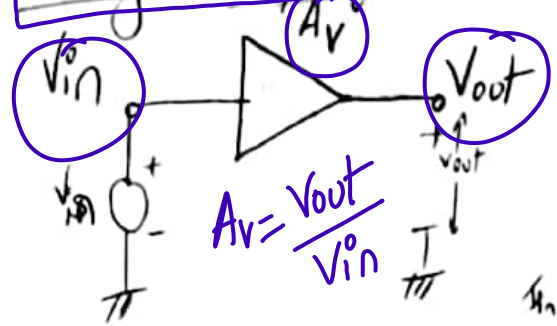

eg CE stage, cascode amplr, CB amplr are voltage amplr


→ A_v : voltage gain

$$A_v = \frac{V_{out}}{V_{in}}$$

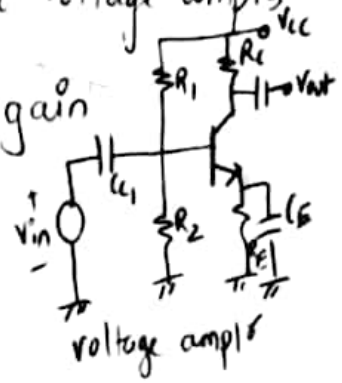

voltage amplr

2. Transimpedance amplifiers:-

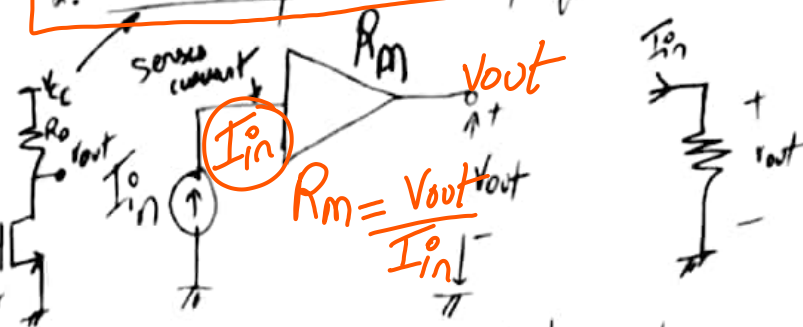


eg. Most of the cameras that captures images, in it a sensor has a current for every pixel & that current has to flow through a amplr like above

2. Optical communication:-


→ $\text{Gain} = \frac{V_{out}}{I_{in}} = R_m \frac{\text{Unit}}{\Omega}$

3. Transconductance Amplifiers:-

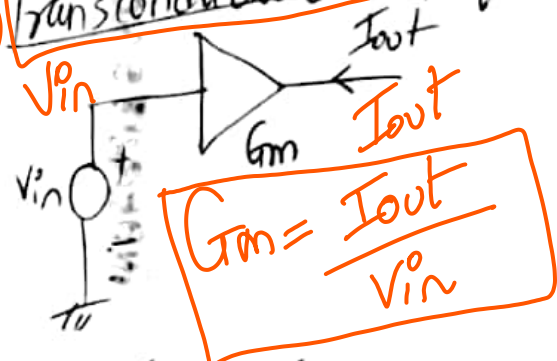


$$\text{Gain} = \frac{I_{out}}{V_{in}} = G_m$$

Unit:- $\left(\frac{1}{\Omega}\right)$

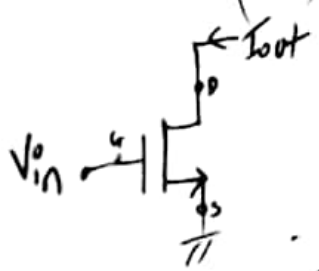


4. Current Amplifiers

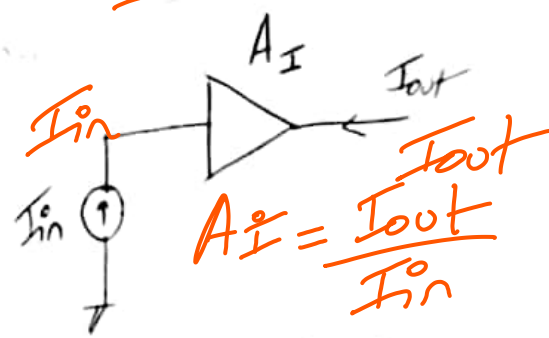

→ A_I : current gain


$$A_I = \frac{I_{out}}{I_{in}}$$

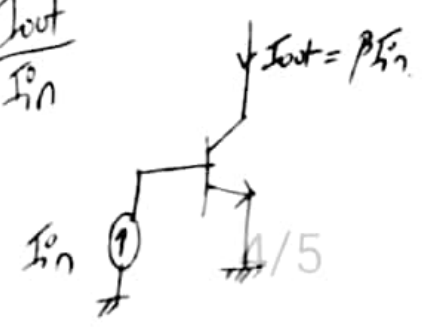

Input and Output Impedances of Four Amp. Topologies:-


03

1. Voltage ampl^r:-

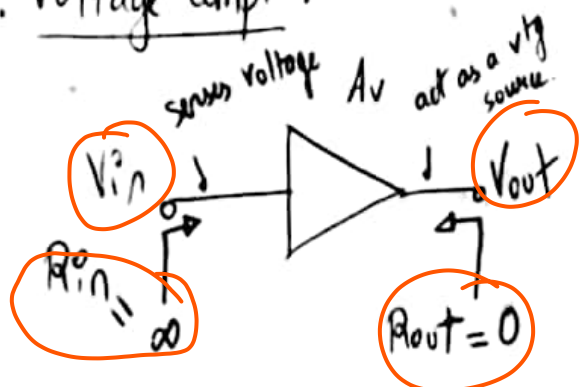


→ V. Ampl^r interface easily with outside world if $R_{in} = \infty$ (ie it doesn't load the preceding ckt) and $R_{out} = 0$ (ie it drive any load)


3. Transconductance ampl^r:-

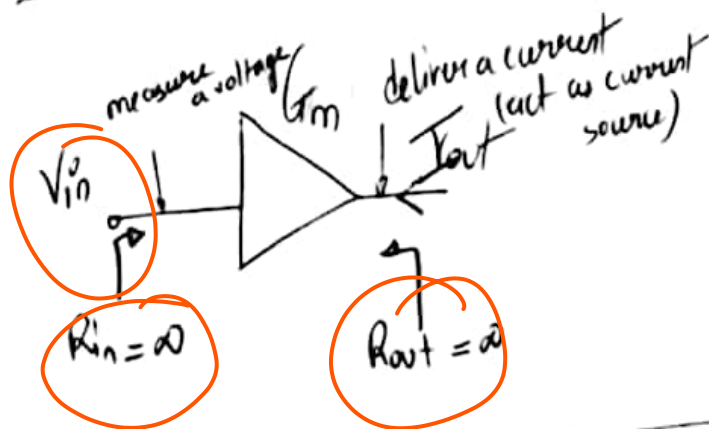

2. Transimpedance ampl^r:-

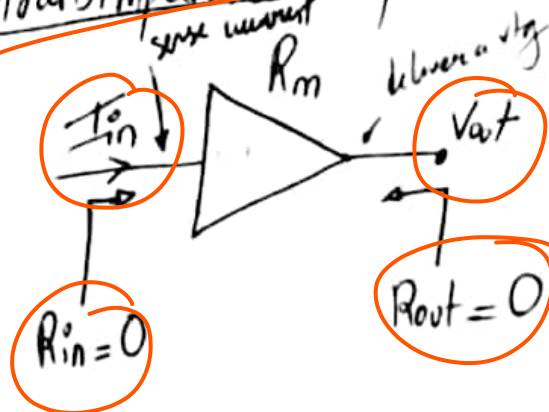


4. Current ampl^r:-

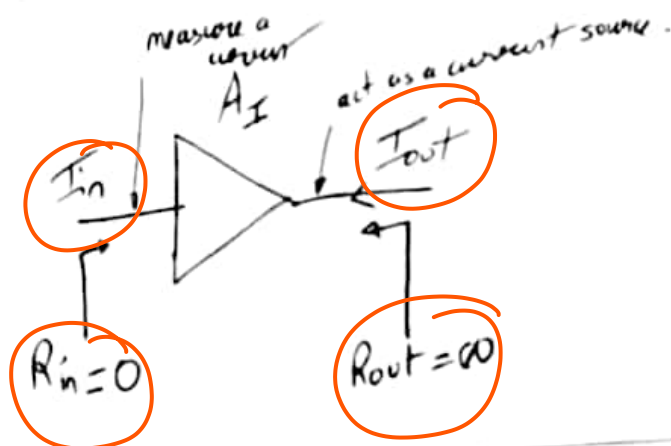



INDERJIT SINGH

Models of Power Amplifier Topologies:

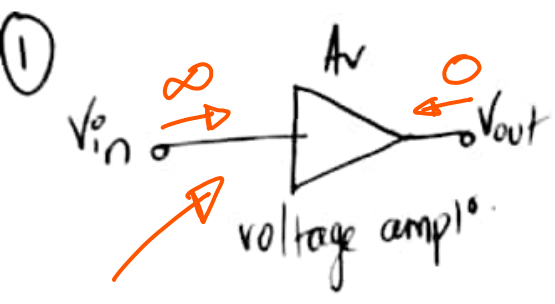


→ This ckt generates a vty V_{out} at the o/p equal to $A_v \times V_{in}$. That's a dependent vty source.


$V_{out} = A_v V_{in}$

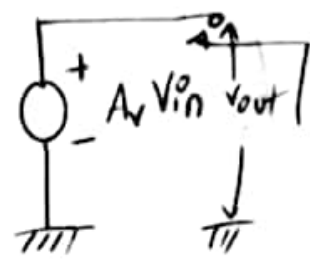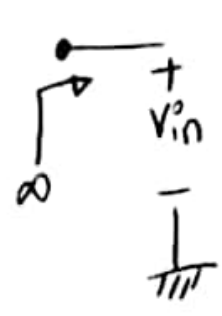



Ideal case model

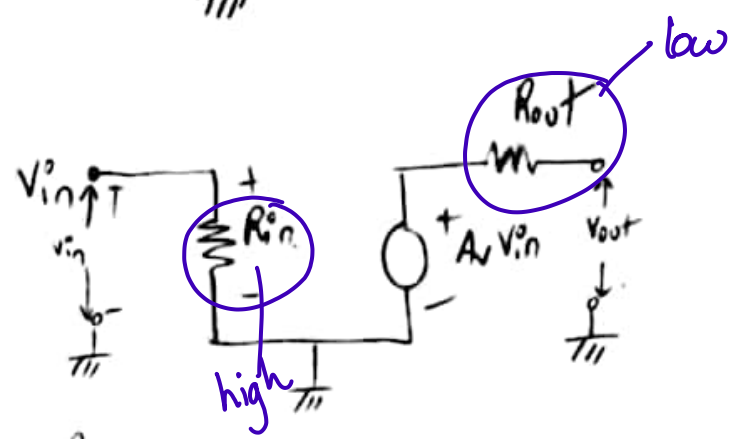


model of Actual voltage amplr

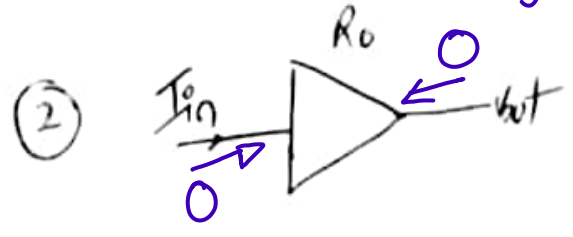

Transimpedance amplr

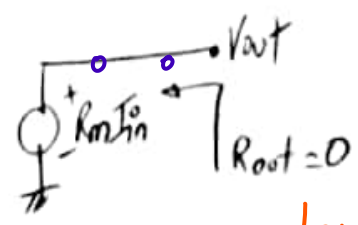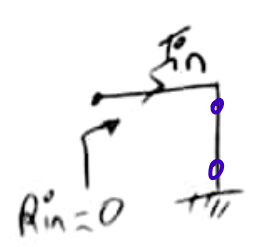


Ideal model


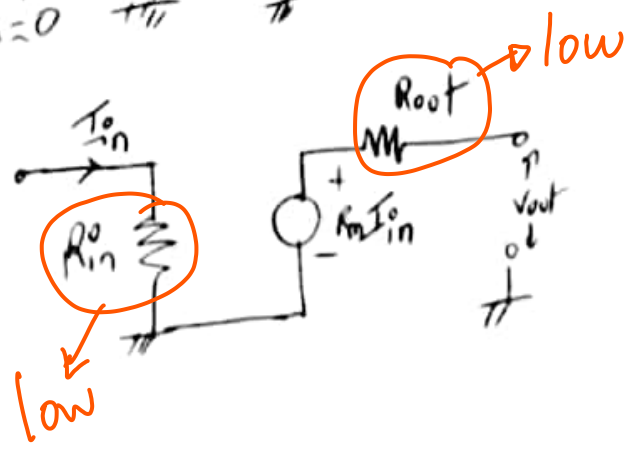


Actual model

INDERJIT SINGH

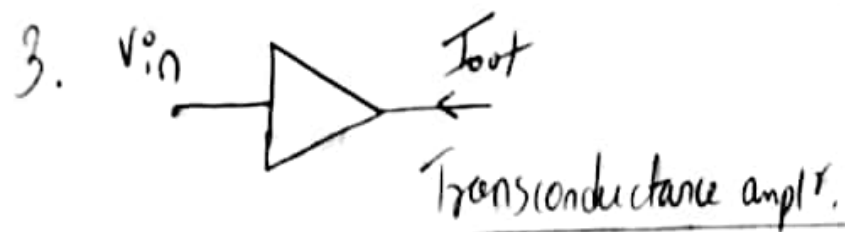

Ideal model

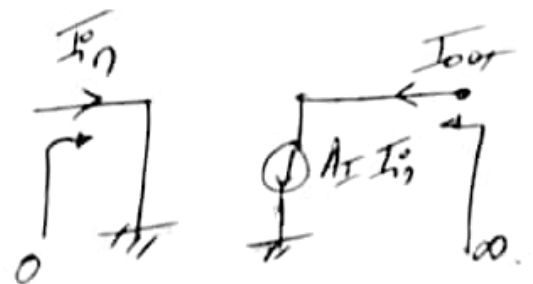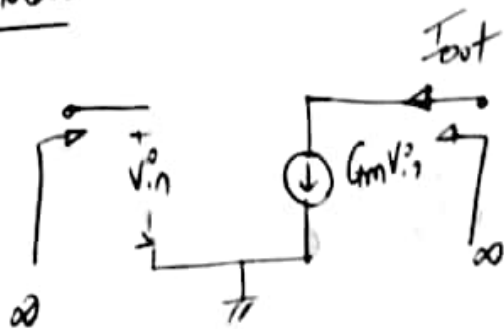

Actual model

