

A chain coiled up near the edge of a smooth table starts to fall over the edge. The velocity v when a length x has fallen is given by $xv \frac{dv}{dx} + v^2 = gx$. Solve the Differential equation to express v in terms of x .

$$\frac{dy}{dx} + P(x)y = Q(x)$$

$$\frac{dv}{dx} + P(x)v = Q(x)$$

$$xv \frac{dv}{dx} + v^2 = gx$$

$$v \frac{dv}{dx} + \frac{v^2}{x} = g$$

$$\text{put } v^2 = y$$

$$\Rightarrow 2v \frac{dv}{dx} = \frac{dy}{dx}$$

$$\frac{1}{2} \frac{dy}{dx} + \frac{y}{x} = g \Rightarrow \frac{dy}{dx} + \frac{2y}{x} = 2g$$

$$P = \frac{2}{x} \quad Q = 2g$$

Soln's:

$$y e^{\int P dx} = \int e^{\int P dx} Q dx + C \quad \text{--- (1)}$$

$$e^{\int P dx} = e^{\int \frac{2}{x} dx} = e^{2 \log x} = e^{\log x^2} = x^2$$

Soln's from (1)

$$y x^2 = \int x^2 2g dx + C$$

$$v^2 x^2 = 2g \frac{x^3}{3} + C$$

$$v^2 = \frac{2gx}{3} + \frac{C}{x^2}$$



In a circuit containing inductance L , resistance R , and voltage E , the current i is given by

$L \frac{di}{dt} + Ri = E$. Find the current i at time t if at $t = 0$, $i = 0$ and L, R, E are constants.

$$L \frac{di}{dt} + Ri = E$$

$$\frac{di}{dt} + \frac{R}{L} i = \frac{E}{L}$$

$$P = \frac{R}{L}$$

$$Q = \frac{E}{L}$$

Ans is $i e^{\int P dt} = \int e^{\int P dt} Q dt + C$

$$i e^{\frac{R}{L}t} = \int e^{\frac{R}{L}t} \frac{E}{L} dt + C$$

$$i e^{\frac{R}{L}t} = \int e^{\frac{R}{L}t} \frac{E}{L} dt + C$$

$$= \frac{E}{L} \frac{e^{\frac{R}{L}t}}{\frac{R}{L}} + C = \frac{E}{R} e^{\frac{R}{L}t} + C$$

$$i = \frac{E}{R} + C e^{-\frac{R}{L}t} \quad \text{--- (1)}$$

given at $t=0$ $i=0$

$$0 = \frac{E}{R} + C e^0 \Rightarrow C = -\frac{E}{R}$$

from (1) $i = \frac{E}{R} - \frac{E}{R} e^{-\frac{R}{L}t} = \frac{E}{R} (1 - e^{-\frac{R}{L}t})$.

$$y e^{\int P dx}$$

$$\frac{dy}{dx} + P(x)y = Q(x)$$

$$y = i$$

$$x = t$$

$$\frac{di}{dt} + P(t)i = Q(t)$$

In a circuit containing inductance L resistance R and voltage E , the current i is given by
 $E = Ri + L \frac{di}{dt}$. If $L = 640H$, $R = 250 \Omega$ and $E = 500\text{volts}$ and $i = 0$ when $t = 0$, find the
 time that elapses before the current reaches 90% of its maximum value.

$$L \frac{di}{dt} + Ri = E$$

$$\frac{di}{dt} + \frac{R}{L} i = \frac{E}{L}$$

from earlier problem soln is

$$i = \frac{E}{R} (1 - e^{-R/L t}) \quad \text{--- (1)}$$

Consider max. value of current is I which we'll get at $t \rightarrow \infty$

i.e. here $i = I$ at $t \rightarrow \infty$

$$\text{from (1)} \quad I = \frac{E}{R} (1 - e^{-\infty}) \quad e^{-\infty} = \frac{1}{e^{\infty}} = 0$$

$$I = \frac{E}{R}$$

given $i = 90\%$ of I (max value of current).

$$= \frac{90}{100} I = \frac{9}{10} \frac{E}{R}$$

$$\text{from (1)} \quad i = \frac{E}{R} (1 - e^{-R/L t})$$

$$\frac{9}{10} \frac{E}{R} = \frac{E}{R} (1 - e^{-R/L t})$$

$$e^{-R/L t} = 1 - \frac{9}{10} = \frac{1}{10}$$

$$\frac{1}{e^{R/L t}} = \frac{1}{10} \Rightarrow e^{R/L t} = 10$$

$$\frac{R}{L} t = \ln(10)$$

$$t = \frac{L}{R} \ln(10) = \frac{640}{250} \ln(10)$$

$$= 5.89 \text{ sec.}$$

The charge q on the plate of a condenser of capacity C charged through a resistance R by the steady voltage V satisfies the differential equation $R \frac{dq}{dt} + \frac{q}{C} = V$. If $q = 0$ at $t = 0$, show that $q = CV(1 - e^{-t/RC})$. Find also the current flowing into the plate.

$$\frac{dq}{dt} + P(t)q = Q(t)$$

$$R \frac{dq}{dt} + \frac{q}{C} = V$$

$$\frac{dq}{dt} + \frac{1}{RC} q = \frac{V}{R}$$

$$P = \frac{1}{RC} \quad Q = \frac{V}{R}$$

$$q e^{\int P dt} = \int e^{\int P dt} Q dt + C \quad \text{--- (1)}$$

$$e^{\int P dt} = e^{\int \frac{1}{RC} dt} = e^{\frac{t}{RC}}$$

from (1)

$$q e^{t/RC} = \int e^{t/RC} \frac{V}{R} dt + C_1$$

$$= \frac{V}{R} \frac{e^{t/RC}}{1/RC} + C_1$$

$$q e^{t/RC} = \frac{V}{R} \times RC e^{t/RC} + C_1$$

$$q = VC + C_1 e^{-t/RC}$$

$$\text{at } t=0 \quad q=0$$

$$0 = VC + C_1 \Rightarrow C_1 = -VC$$

$$q = VC - VC e^{-t/RC}$$

$$= VC(1 - e^{-t/RC})$$

$$i = \frac{dq}{dt} = VC \left(0 - e^{-t/RC} \left(-\frac{1}{RC} \right) \right)$$

$$= VC \frac{e^{-t/RC}}{RC} = \frac{V}{R} e^{-t/RC}$$