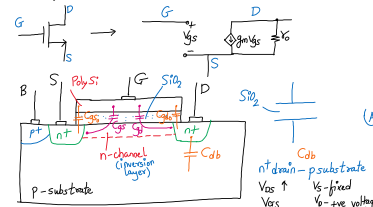


\* High frequency model of MOSFET:





$$X_C = \frac{1}{2\pi f C}$$


$f \uparrow \rightarrow X_C \downarrow$

$C_{gs}$  &  $C_{gd}$ : Inter-electrode/Parasitic capacitance ( $\sim pF$ )  
 $C_{gs}$  &  $C_{gd}$ : Overlap capacitance ( $\sim pF$ )  
 $C_{db}$ : Drain to substrate junction capacitance ( $\sim pF$ )

$$C = \frac{qA}{dV}$$

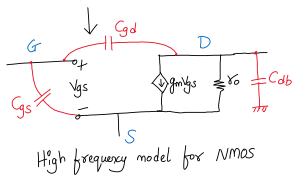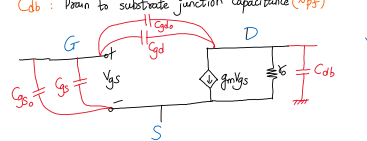


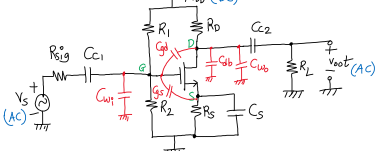\* High-frequency response of MOSFET amplifier:



$C_{C1}, C_{C2}, C_S$ : Externally connected capacitors ( $\mu F$ )  
 $C_{gs}, C_{gd}, C_{db}, C_{wi}, C_{wo}$ : Inter-electrode capacitance  
 Parasitic capacitance  
 Stray capacitance


\* Miller theorem (Miller effect):

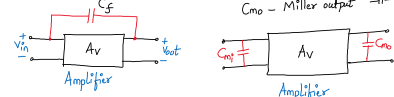

$$C_{mi} = (1 - A_v) C_f$$

$$C_{mo} = (1 + \frac{1}{A_v}) C_f$$

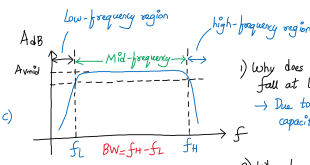
$f \rightarrow v \rightarrow \text{high}$   
 $X_C = \frac{1}{2\pi f C}$   
 $f \uparrow \rightarrow X_C \downarrow$



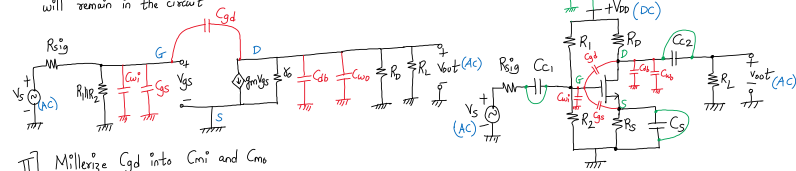
1) Why does the gain of amplifier fall at low frequency?  
 → Due to externally connected capacitor ( $C_{C1}, C_{C2}, C_S$ )  
 $(f_{LC1}, f_{LC2}, f_{LS})$   
 2) Why does the gain of amplifier fall at high frequency?  
 → Due to parasitic or stray capacitors ( $C_{gs}, C_{gd}, C_{db}, C_{wi}, C_{wo}$ )  
 $(f_{Hi}, f_{Ho})$

I] High-frequency equivalent circuit:

For high frequency, connected capacitors ( $C_{C1}, C_{C2}, C_S$ ) are behaving as short-circuit, but all stray (parasitic) capacitors will remain in the circuit



II] Millerize Cgd into Cmi and Cmo

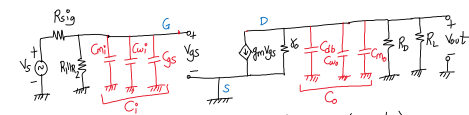


$$C_{mi} = C_{gd} (1 - A_v)$$

$$C_{mo} = C_{gd} (1 + \frac{1}{A_v})$$



$$C_i = C_{mi} + C_{wi} + C_{gs}$$

$$C_o = C_{db} + C_{wo} + C_{mo}$$

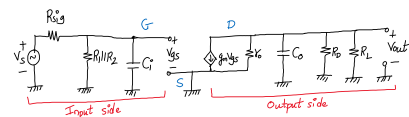

III] Input side circuit ( $f_{Hi}$ )

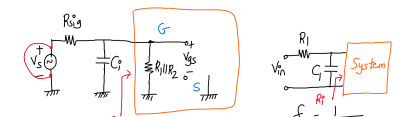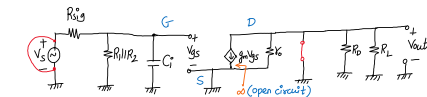Short circuit  $C_o$  &  $V_S$  and consider  $C_i$



$$R_T = R_{S1} \parallel R_2$$



$$R_{eq} = R_{S1} \parallel R_1 \parallel R_2$$

$$f_{Hi} = \frac{1}{2\pi R_{eq} C_i}$$

where,  $C_i = C_{mi} + C_{wi} + C_{gs}$   
 $C_{mi} = C_{gd} (1 - A_v)$

IV] Output side circuit ( $f_{Ho}$ )

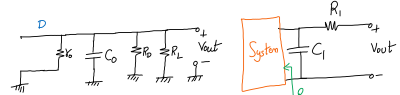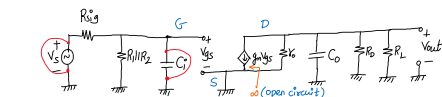Short circuit  $C_i$  &  $V_S$  and consider  $C_o$



$$R_{eq} = R_o \parallel R_L \parallel R_{S1}$$

$$f_{Ho} = \frac{1}{2\pi R_{eq} C_o}$$

where,  $C_o = C_{mo} + C_{wo} + C_{db}$   
 $C_{mo} = C_{gd} (1 + \frac{1}{A_v})$

V] Estimation of  $f_H$ :

$$f_H = \min(f_{Hi}, f_{Ho}) \rightarrow \text{Higher cut-off frequency of the amplifier}$$