

Introduction to feedback: General feedback system

21/2/0

Today's lecture

- Introduction to feedback
- General feedback system
- "Closed-loop" Transfer Function

- Feedback has been around since ages - human^{as long as} have been around.

Simple exercise:- (Eg of negative flb)

- Close your eyes and try to touch your finger tips
- I can't, why?
- Becoz, we have broken a flb loop consisting of our eyes that monitors the movement of our fingers to make sure that the finger tip touch.
- The notion of having a loop that regulates & monitors movements & actions is very powerful.

Examples of Negative feedback:

Our Eyes



Pupil shrinks
when we go to a
bright room.

The eye is smart enough to adjust the size of the pupil to make sure that the amount of light that enters our eye & hits the retina in the back is controlled.

Our Ears:



That's a -ve f/b system.

If you go to a concert that has very loud music, & we stay there for 1 or 2 hours & then when you leave the concert & you go to a quiet area: You feel like your ears are a little deaf / you are little hard of hearing. Why?


~ If music is so loud, our ear has a mechanism to adjust the threshold of hearing (so that loud music does not damage our ear), so when you leave the concert, that mechanism is still keeping the threshold at that point, so you feel a little hard of hearing & it takes some time for the

ear to go back to where it was.

03

That's a -ve f/b system:- That tries to adjust the volume (level of sound) that enters your ear. -ve f/b \rightarrow Stabilizing

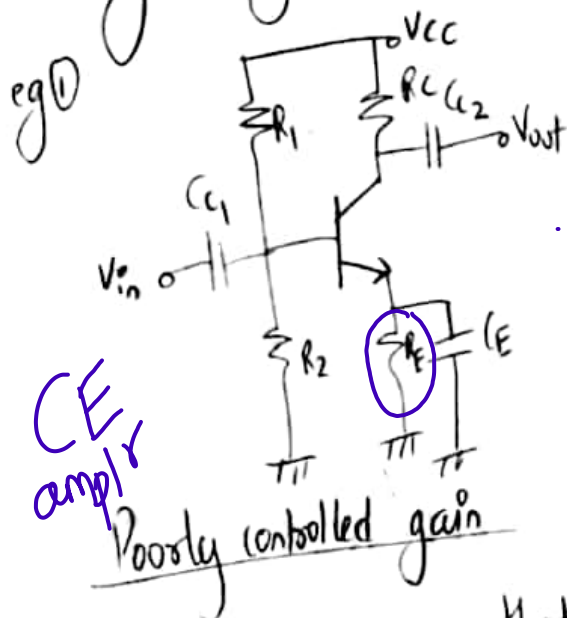• Why negative feedback? ----- used in ckt's? (what am I trying to achieve?)



$$A_v = -150 \text{ (with CE)}$$

$$A_v = -g_m R_C$$

gain is not that accurate

If an application requires a gain of $A_v = -4.00$ to such precision.


A_v can vary:

- Resistor: whether discrete or in a chip has some variability
- ~ from Temperature it changes
- ~ from sample to sample it changes

• There is no way, that this $A_v = -g_m R_C$ gain will give us that amount

-ve \rightarrow Reduces gain f/b but makes it more

(are going down the road. stable)

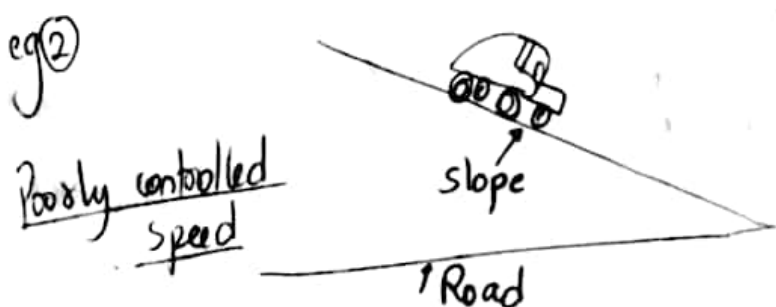

• Without feedback, we have "untamed" and "poorly-controlled" circuits and systems.



If we just let the car go by itself, the speed of car will keep rising, there is no way to control the speed. (The Slope wants to accelerate the car) - i.e speed keeps rising.

• So, without any f/b present, we have no control over the car.

INDERJIT SINGH



Purpose of negative feedback is to in eq (1) tightly controlled gain (A_v) and in eq (2) is to make sure that the speed of the car ^{achieve} some amount that you want (under control).

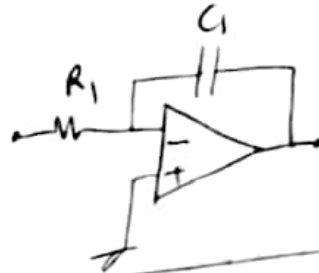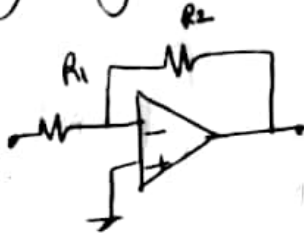• We will be seeing negative feedback in LICD:



• Let's build a cruise control system:-

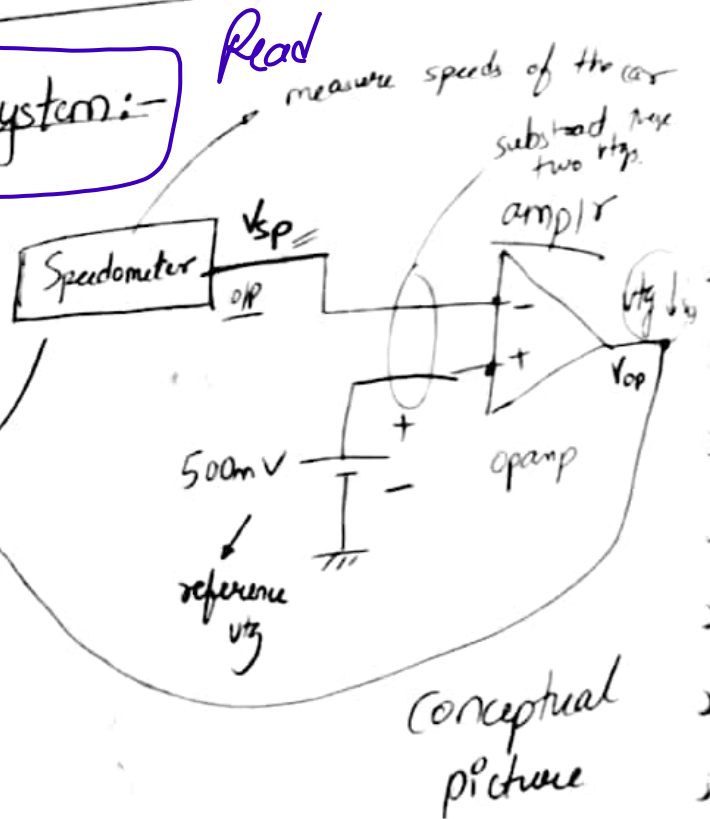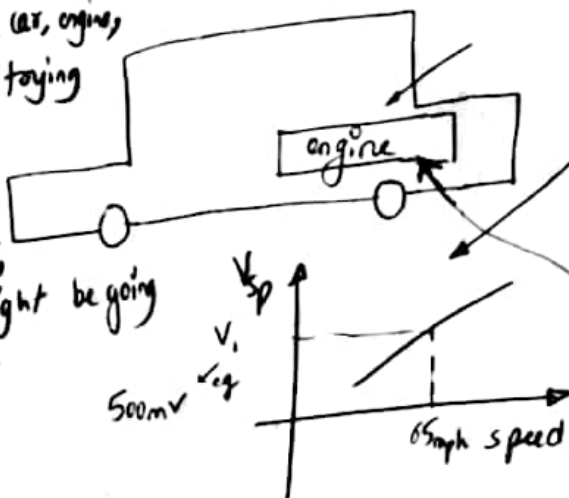• loop consisting of the car, engine, speedometer, amplifier → trying to make sure that the speed of car is relatively constant, even though we might be going up slope or down the slope.



Conceptual picture

→ faster the car goes, higher is V_{sp}

→ Car want to speed up → beyond 65mph; V_{sp} rises beyond 500mV ($V^- > V^+$) → V_{op} goes down.


(conversely, upper slope, car want to go slowly, $V^- < V^+$ → V_{op} ↑ → engine faster → back to 65mph)

car goes max slowly → engine slows down

→ This is an example of a negative f/b system. **INDERJIT SINGH**

General negative feedback system:

05

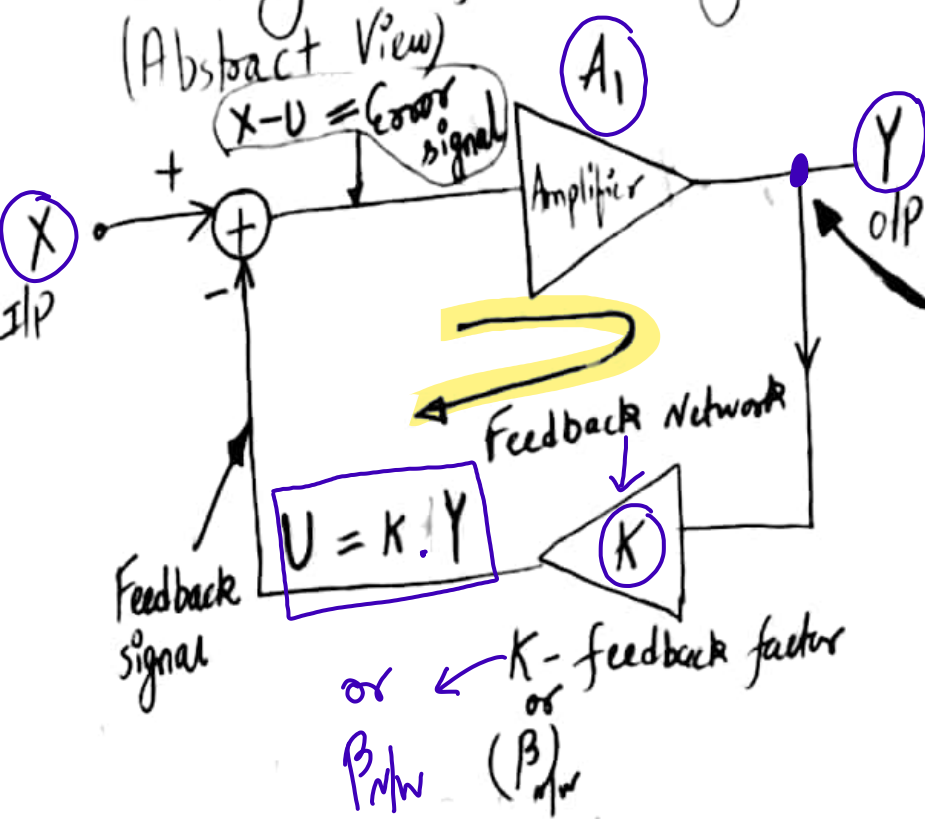

4 components

- ① A₁: Feed forward system (eg car + engine)
- ② Sensing Mechanism (Speedometer)
- ③ Feedback network (just a wire)
- ④ Subtractor (opamp) (comparing X & U)

Notes: (Have clear understanding of the points below)


① Negative feedback (-fb' sig is subtracted from I/P)

② Direction of signal flow (↻)


③ Error signal = $X - U$ must be minimized. How and why?

④ Open loop system (No feedback)

$K = 0$

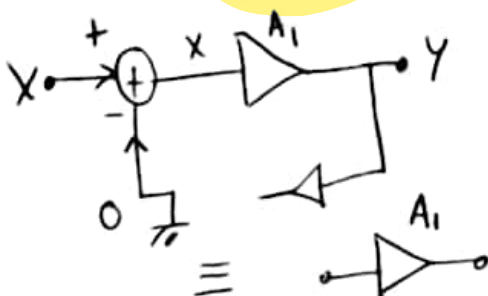

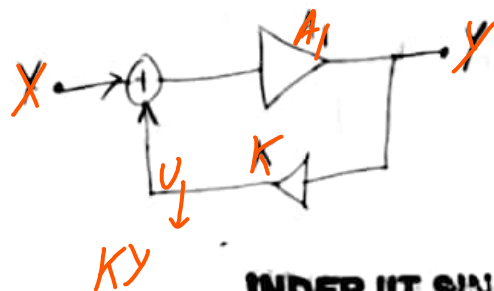
closed-loop system (with feedback)
 $K \neq 0$ 5/7



INDERJIT SINGH

Transfer function of closed-loop system :-

$$Y = A_1(X - U) = A_1(X - KY)$$

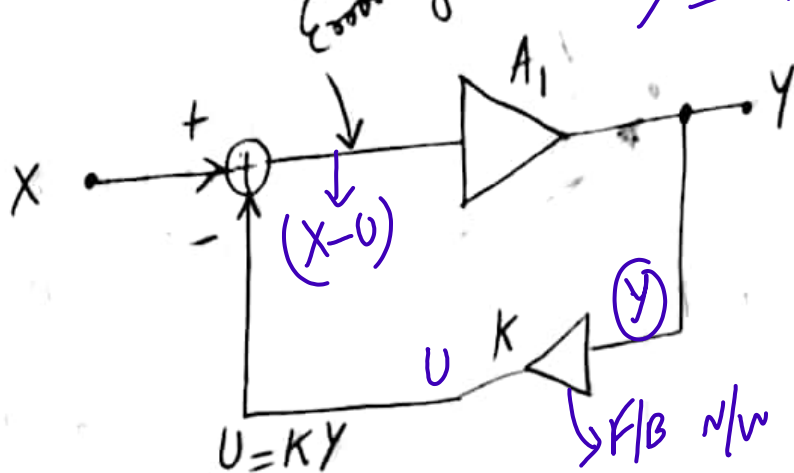

$$\frac{Y}{X} = ?$$

$$\left(\frac{Y}{X}\right) = ?$$

→ Error Signal = $X - U = X - KY$

→ $Y = A_1(X - KY) = A_1X - A_1KY$

$$\frac{Y}{X} = \frac{A_1}{1 + KA_1}$$

We will examine this eqⁿ from many different perspectives

Memorize this eqⁿ for the rest of your life
This eqⁿ tells us so much about negative feedback

A_1 - open-loop gain

$\frac{A_1}{1 + KA_1}$ - closed loop gain

→ A_1 : open-loop gain

→ $\left[\frac{A_1}{1 + KA_1}\right]$: closed-loop gain

→ $K, A_1 > 0$ (K & A_1 are positive)

⇒ Closed-loop gain < open-loop gain

Why do we reduce the gain?

How do we implement the subtractor?

What is the purpose of the feedback network?

07

Quiz: Determine the error signal in terms of the input X ?
 $U = KY$

$$\text{Error signal} = X - U = X - KY = X - K \left(\frac{A_1}{1 + KA_1} \right) X$$

$$\boxed{\text{Error sig} = \frac{X}{1 + KA_1}}$$


$1 + KA_1 \uparrow$ $K \rightarrow \beta_{N/W}$
 $(KA_1) \uparrow \uparrow$ $A_1 \rightarrow \text{Amplifier gain.}$

- To minimize this error \Rightarrow we have to maximize KA_1
- This quantity " KA_1 " play a profound role in the performance of this overall system.

Observation: If the error is minimized,
 $(X - U)$ becomes small $\Rightarrow \boxed{X = U}$

\Rightarrow Feedback signal is a good replica/
Copy of the input.

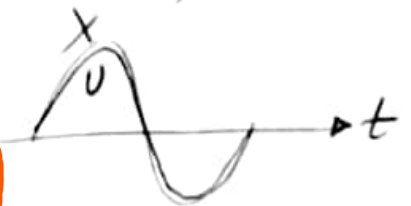
$$X - U \rightarrow 0$$
$$\boxed{X = U}$$



INDERJIT SINGH

Review : (Story so far)

[$X - U = \text{Error signal}$]

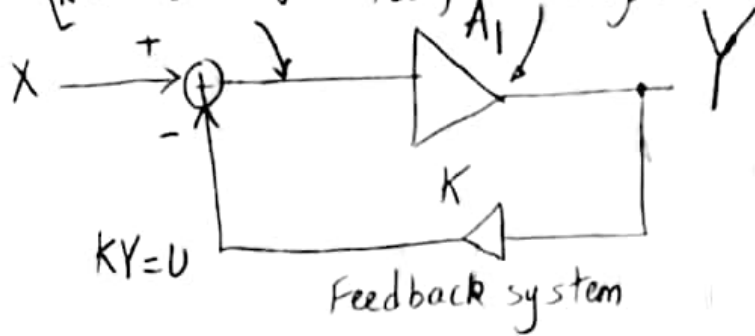

$$\frac{Y}{X} = \frac{A_1}{1 + KA_1}$$


Open-loop gain $\rightarrow A_1$
Closed-loop gain $\rightarrow \frac{Y}{X}$

$$E_{\text{error}} = \frac{X}{1 + KA_1}$$

If error is small; $U \approx X$

Golden Rule:

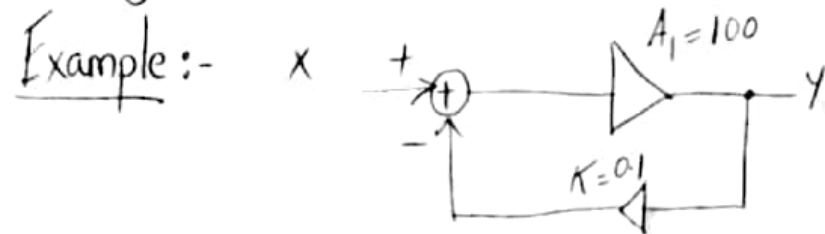- In a well-designed negative-feedback system, the feedback signal U is a good copy (replica) of the input signal X .




$$\frac{Y}{X} = \frac{A_1}{1 + KA_1} = \frac{100}{1 + 10} = \frac{100}{11} \approx 9.09$$

$100 \rightarrow 9.09$
 $0.1 \rightarrow 10$

Example: What happens if A_1 drops to 50 in the previous example?

$$\frac{Y}{X} = \frac{50}{1 + 5} = \frac{50}{6} \approx 8.33$$

$$\frac{Y}{X} \rightarrow 8.33$$

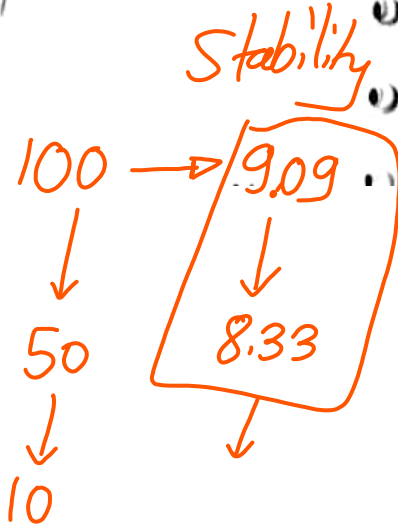

• Even though the open-loop gain changed by a factor of 2, ⁰² the closed-loop gain changed by only 10%

↳ Most important result:-
 ↳ Significant change in A_1 leads to a minor change in closed-loop gain. $\left(\frac{A_1}{1+KA_1}\right)$

Observation: If $KA_1 \gg 1$, \Rightarrow $KA_1 \gg 1$

$$\boxed{\frac{Y}{X} \approx \frac{1}{K}}$$

\Rightarrow Closed-loop gain is relatively independent of open-loop gain.

\Rightarrow We should try to maximize KA_1 .

Observation: K is usually chosen ≤ 1

$$\boxed{\frac{Y}{X} \approx \frac{1}{K}}$$

$$\frac{Y}{X} = \frac{A_1}{1+KA_1}$$

$$\frac{Y}{X} = \frac{1}{K} \cdot \frac{1}{\left(\frac{1}{KA_1}\right) + 1}$$

• Loop gain: KA_1 : in a well-designed negative feedback system, the loop gain $\gg 1$.
 \Rightarrow Closed-loop gain $\approx \frac{1}{K}$

$KA_1 \rightarrow$ loop gain

Important Property: If $KA_1 \gg 1 \Rightarrow$

$$\frac{Y}{X} \approx \frac{1}{K} \text{ and relatively indep. of } A_1$$



Summary of feedback concepts:-

① We sacrifice the open-loop gain to benefit from negative feedback.

② The feedback signal is a good copy (replia) of the input signal.

③ $Y = \frac{U}{K}$ is a good copy of X but with a scaling factor. eg if $K=0.1$, $Y \approx 10X$

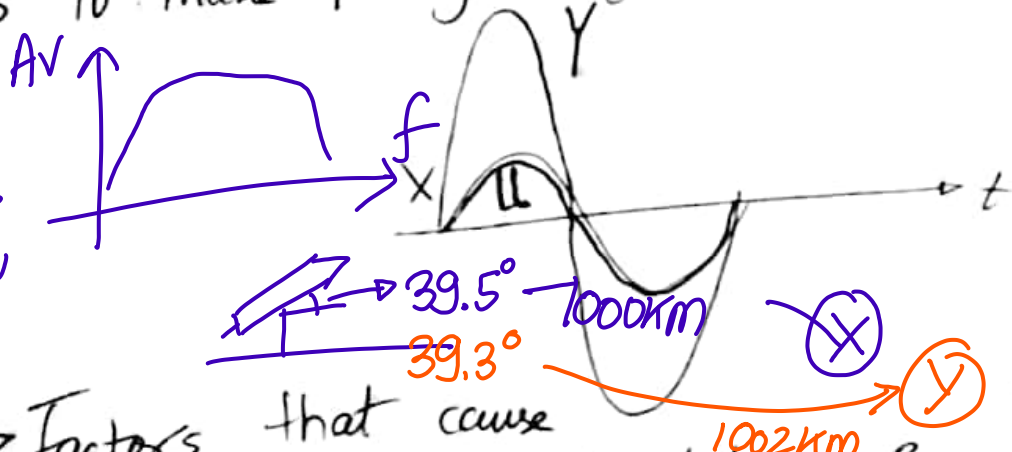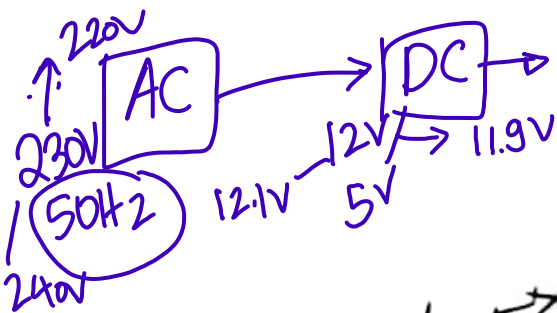
⇒ The loop wants to make Y a good (scaled) copy of X .



④ If $KA_1 \gg 1$ ⇒ Factors that cause A_1 to vary have less effect on the closed-loop gain.

$$A_v = -g_m R_c || R_L$$


$$g_m = \frac{I_c}{V_T}$$

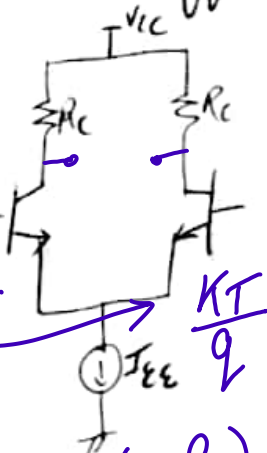

open-loop gain

Factors that cause A to vary:

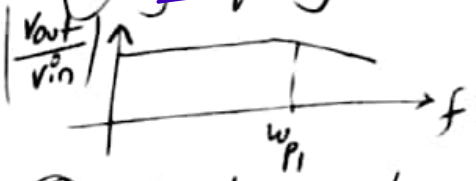- ① Temperature ✓
- ② Supply voltage ✓
- ③ Frequency



④ load impedance ($\sim R_L$)