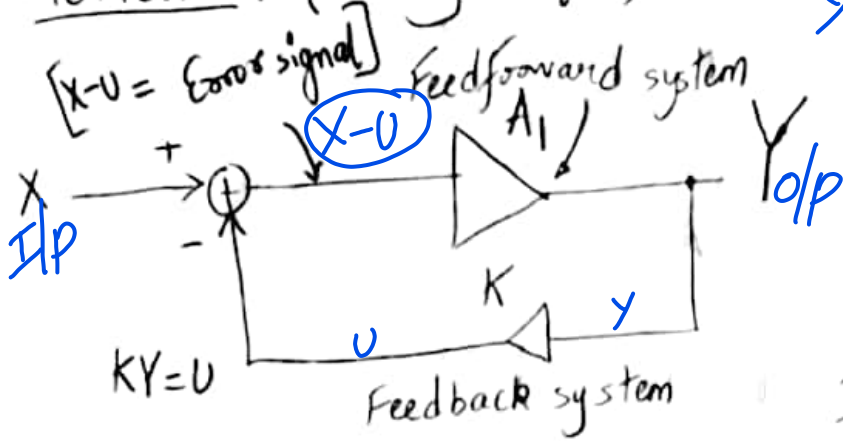


Review : (Story so far) $K = \frac{U}{Y}$



$$\frac{Y}{X} = \frac{A_1}{1 + KA_1}$$


Open-loop gain (A_{OL}) $\rightarrow A_1$
 Closed-loop gain $\rightarrow KA_1 \rightarrow \text{loop gain} < A_{OL}$

$$C_{\text{error}} = \frac{X}{1 + KA_1}$$

If error is small; $U \approx X$

Golden Rule:

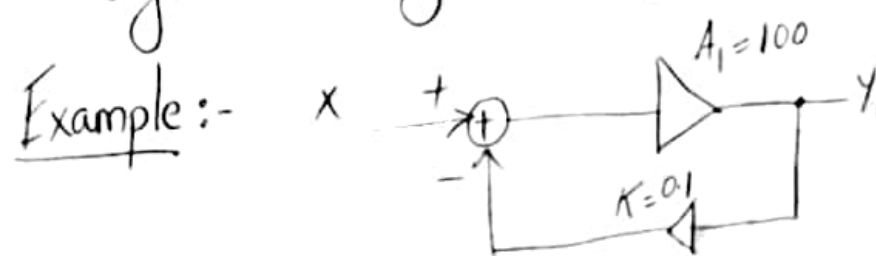- In a well-designed negative-feedback system, the feedback signal is a good copy (replica) of the input signal.



$$\frac{Y}{X} = \frac{A_1}{1 + KA_1} \approx \frac{100}{1 + 10} = \frac{100}{11}$$

$$\frac{Y}{X} \approx 9.09$$

100 \rightarrow 50
 9.09 \downarrow 8.33

Example: What happens if A_1 drops to 50 in the previous example? $A_1 = 50$

$$\frac{Y}{X} = \frac{50}{1 + 5} = \frac{50}{6} \approx 8.33$$

INDERJIT SINGH

• Even though the open-loop gain changed by a factor of 2,⁰² the closed-loop gain changed by only 10%

↳ Most important result:-

↳ Significant change in A_1 leads to a minor change in closed-loop gain.

Observation: If $KA_1 \gg 1$, \Rightarrow

$$\boxed{\frac{Y}{X} \approx \frac{1}{K}}$$

\Rightarrow Closed-loop gain is relatively independent of open-loop gain.

\Rightarrow We should try to maximize KA_1 .

Observation: K is usually chosen ≤ 1


• Loop gain: KA_1 : in a well-designed negative feedback system, the loop gain $\gg 1$.
 \Rightarrow Closed-loop gain $\approx \frac{1}{K}$

Important Property: If $KA_1 \gg 1 \Rightarrow$

$$\frac{Y}{X} \approx \frac{1}{K} \text{ and relatively indep. of } A_1$$



Summary of feedback concepts:-

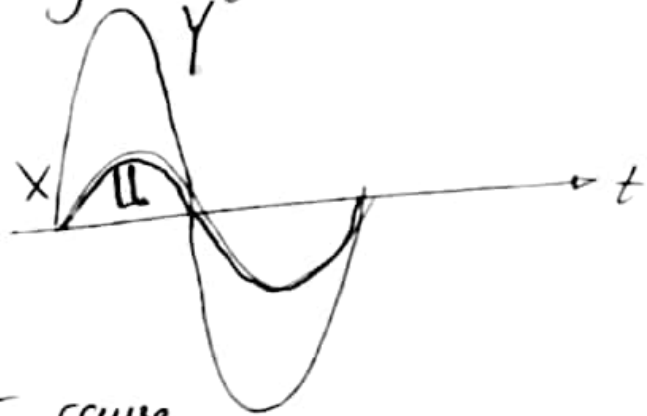- ① We sacrifice the open-loop gain to benefit from negative feedback.
 - ② The feedback signal is a good copy (replia) of the input signal.
 - ③ $Y = \frac{V}{K}$ is a good copy of X but with a scaling factor. eg if $K=0.1$, $Y \approx 10X$
- ⇒ The loop wants to make Y a good (scaled) copy of X .



- ④ If $KA_1 \gg 1 \Rightarrow$ Factors that cause A_1 to vary have less effect on the closed-loop gain.

$$A_v = -g_m(R_C || R_L)$$

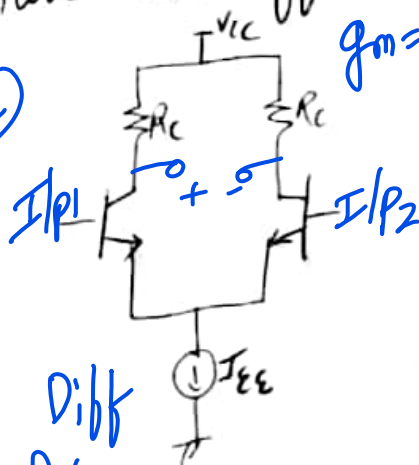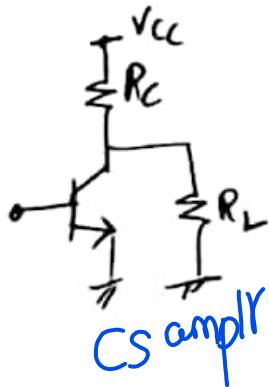


$$g_m = \frac{I_C}{V_T}$$


① Temperature.

② Supply voltage.

③ frequency.

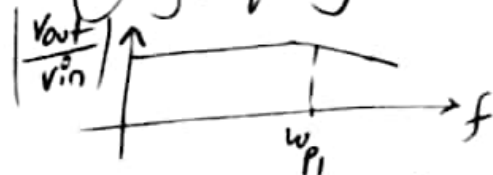

④ load impedance ($\sim R_L$)

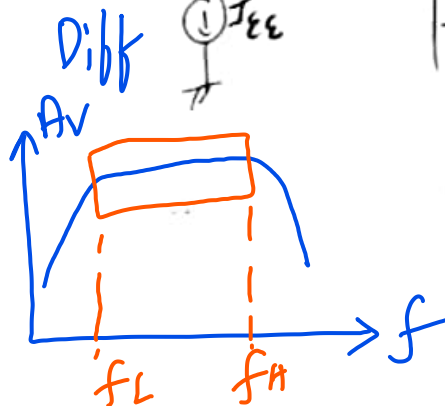

$$BW = f_H - f_L$$

- Properties of Negative Feedback:

$$\frac{Y}{X} = \frac{A_1}{1 + KA_1} \approx \frac{1}{K} \text{ if } KA_1 \gg 1$$

(1) Gain Desensitization $\Rightarrow \frac{Y}{X}$ is less sensitive to temperature, supply, etc than A_1 is.

$$\frac{Y}{X} = \frac{A_1}{1 + KA_1} \approx \frac{1}{K} \quad KA_1$$


$$\frac{Y}{X} = \frac{\frac{A_1}{KA_1}}{\frac{1}{KA_1} + 1} \approx \frac{1}{K}$$

Gain \times BW = constant

Gain \downarrow

100 \rightarrow A_{OL}


10 \rightarrow A_{CL}

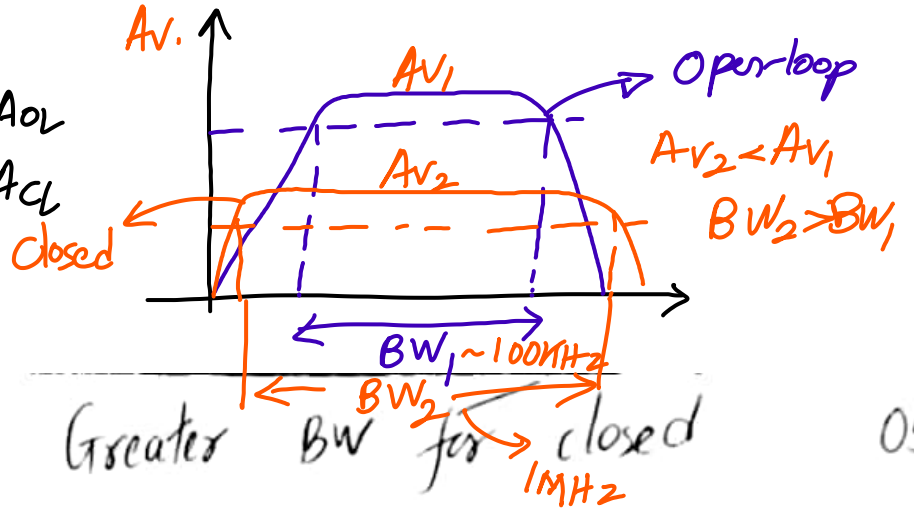


2) Bandwidth Extension: Greater BW for closed-loop system

05

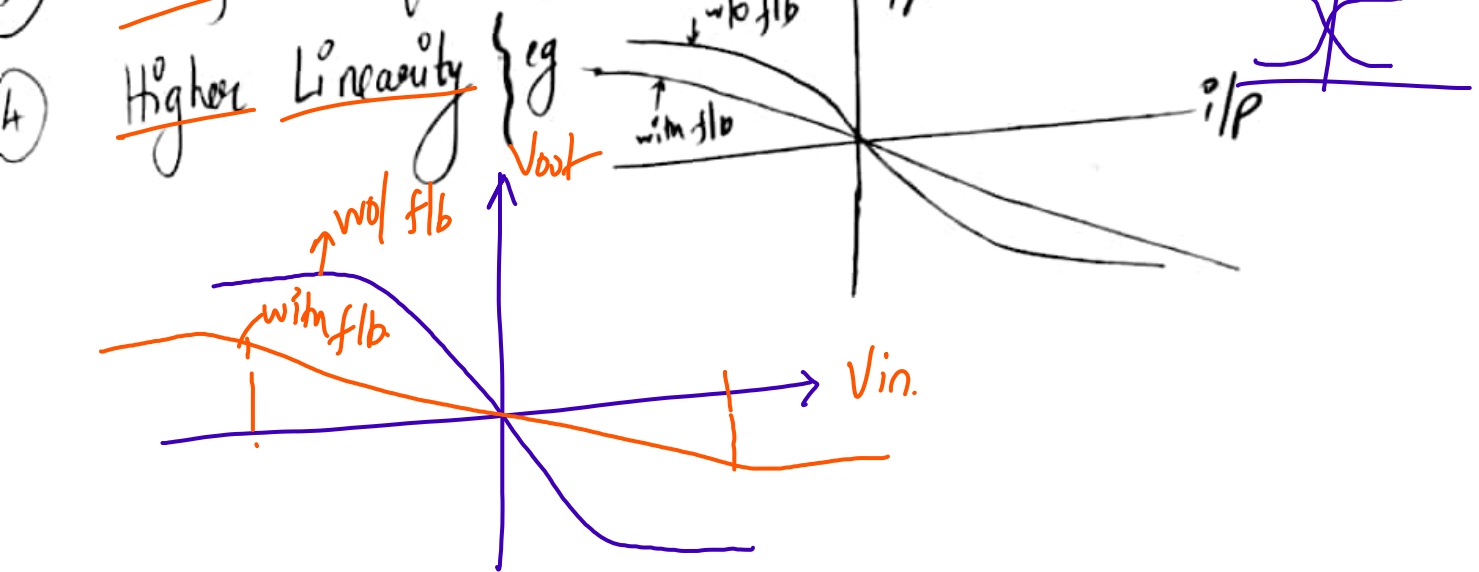3) Modification of Input and output impedances.



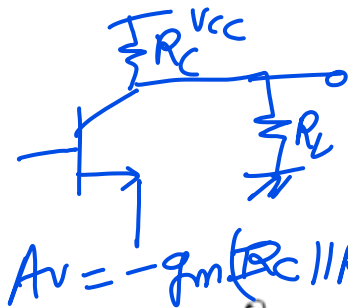Properties of Negative feedback :- I_{CQ} $g_m = \frac{I_C}{V_T}$



2/3/1

① Gain Desensitization :-

If A_1 (open-loop gain) changes due to various factors (temperature, supply, frequency, load impedance), the closed-loop gain does not change as much.

→ The closed-loop gain ($\frac{Y}{X}$) of the amplifier with negative feedback is,

$$\frac{Y}{X} = A_f = \frac{A_1}{1 + A_1 K} \quad \text{--- (1)}$$

A_f → closed-loop gain with negative f/b

→ Differentiating eqⁿ (1) w.r.t A_1 , we have

$$\left| \frac{dA_f}{dA_1} \right| = \frac{(1 + A_1 K) \cdot 1 - A_1 K}{(1 + A_1 K)^2} = \frac{1}{(1 + A_1 K)^2}$$

i.e. $dA_f = \frac{dA_1}{(1 + A_1 K)^2}$

→ Dividing both sides by A_f , we get $A_f = \frac{A_1}{1 + KA_1}$

$$\frac{dA_f}{A_f} = \frac{dA_1}{(1 + A_1 K)^2} \times \frac{1}{A_f} = \frac{dA_1}{(1 + A_1 K)^2} \times \left(\frac{1 + KA_1}{A_1} \right)$$

i.e. $\boxed{\frac{dA_f}{A_f} = \frac{dA_1/A_1}{1 + KA_1}} \quad \text{--- (2)}$

$$\frac{dA_f}{A_f} = \frac{dA_1/A_1}{1 + KA_1}$$

INDERJIT SINGH

$$\frac{dA_f/A_f}{dA_1/A_1} = \frac{1}{1+KA_1}$$

ie $\boxed{\frac{dA_f}{A_f} = \frac{dA_1/A_1}{1+KA_1}}$ *

02

where, $\frac{dA_f}{A_f} \rightarrow$ represents the fractional/percentage change in voltage gain with f/b.

$\frac{dA_1}{A_1} \rightarrow$ represents the fractional/percentage change in voltage gain without f/b.

2/9

\rightarrow Sensitivity = $\boxed{\left[\frac{dA_f/A_f}{dA_1/A_1} \right] = \frac{1}{1+KA_1}}$ - (3)


\rightarrow Reciprocal of sensitivity is called "desensitivity" (D)

$\boxed{D = 1+KA_1}$ - Desensitivity

$K \propto \beta \propto \beta_{N/w}$ $\beta_{N/w}$

$\boxed{D = 1+KA_1}$

INDERJIT SINGH

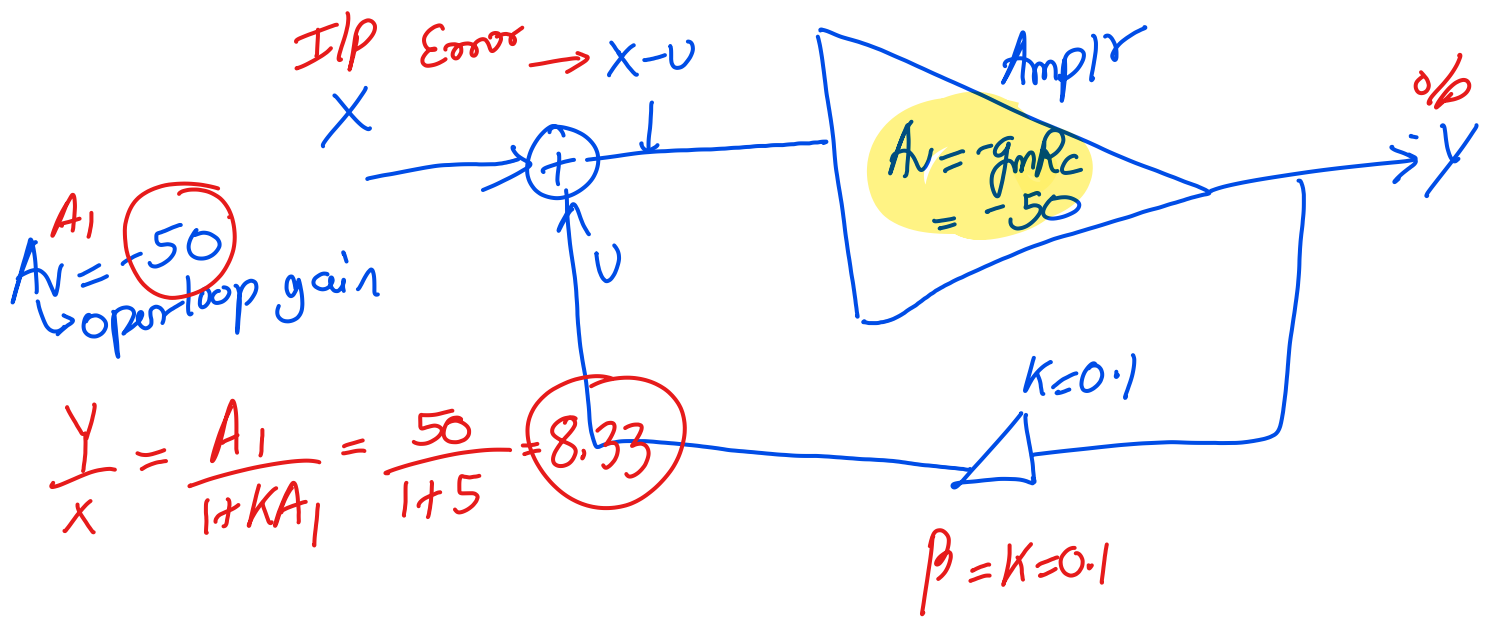

Q1: An amplifier has an open-loop gain of 1000 and a feedback ratio of 0.04. If the open-loop gain changes by 10% due to temperature, find the % change in gain of the amplifier with feedback.

$\frac{dA_1}{A_1} = 10\%$ $\frac{dA_f}{A_f} = ?$

Solⁿ: Given: $A_1 = 1000$, $K = 0.04$, $\frac{dA_1}{A_1} = 10\% = 0.1$

$$\frac{dA_f}{A_f} = \frac{dA_1}{A_1} \times \frac{1}{1 + A_1 K} = 0.1 \times \frac{1}{1 + 1000 \times 0.04} = 0.25\%$$

2) * An amplifier has voltage gain with flb of $\frac{100}{A_f}$. If the gain without flb changes by 20% and the gain with flb should not vary more than 2%, determine the value of open-loop gain and feedback ratio.

Solⁿ:- Given:- $A_f = 100$, $\frac{dA_f}{A_f} = 2\% = 0.02$

$$\frac{dA_1}{A_1} = 20\% = 0.2$$

$A_1? K?$

$$\rightarrow \frac{dA_f}{A_f} = \frac{dA_1}{A_1} \times \frac{1}{1 + KA_1} \Rightarrow 0.02 = 0.2 \times \frac{1}{1 + KA_1}$$

$$\text{ie } 1 + KA_1 = \frac{0.2}{0.02} = 10$$

$$\text{ie } \textcircled{D} = 10 = 1 + KA_1$$

$\frac{Y}{X} \Rightarrow A_f$
 \hookrightarrow gain with f/b

$$\text{Now, } \textcircled{A_f} = \frac{A_1}{1 + KA_1} \Rightarrow 100 = \frac{\textcircled{A_1}}{10}$$

$$\text{ie } \underline{A_1 = 1000} \quad \text{--- open-loop gain}$$

$\textcircled{A_1 > 1}$

$$\rightarrow 1 + KA_1 = 10$$

$$\text{ie } KA_1 = 9$$

$$K = \frac{9}{1000} = \textcircled{0.009} \rightarrow \text{f/b ratio}$$

$\textcircled{K < 1}$


4/9

② Bandwidth Extension:


As an example, $A_1(s)$

$$A_1(s) = \frac{A_0}{1 + s/\omega_{p0}}$$

↑
open-loop
amp/

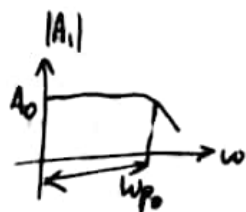

$$\underline{BW = \omega_{p0}}$$

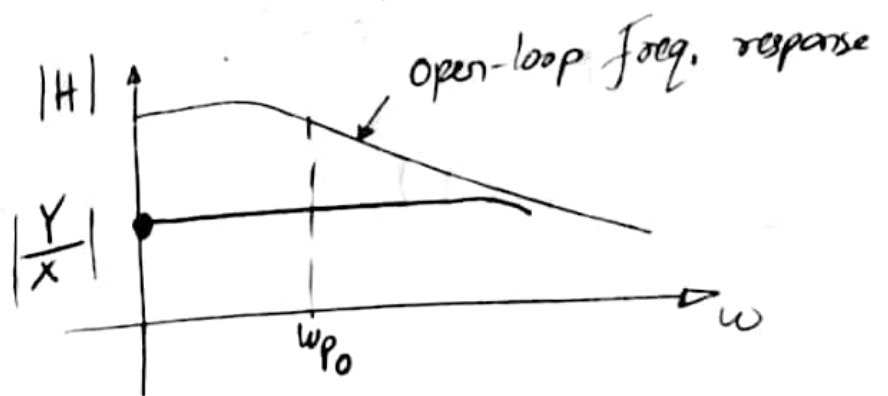

$$\frac{Y}{X}(s) = \frac{A_1}{1+KA_1} = \frac{\frac{A_0}{1+s/\omega_{p0}}}{1+K \cdot \left(\frac{A_0}{1+s/\omega_{p0}} \right)}$$

$$\frac{Y}{X}(s) = \frac{A_0}{1+KA_0 + s/\omega_{p0}}$$

Multiply by $\frac{1+s/\omega_{p0}}{1+s/\omega_{p0}}$

$$X \left(1 + \frac{s}{\omega_{p0}} \right)$$

$$\frac{Y}{X}(s) \approx \frac{\frac{A_0}{1+KA_0}}{1 + \frac{s}{(1+KA_0)\omega_{p0}}}$$

Transfer function


Divide nr & dr by loop gain

If $s=0 \Rightarrow \frac{Y}{X} = \frac{A_0}{1+KA_0}$

pole freq \Rightarrow Closed-loop pole :-

$$-\omega_{p0}(1+KA_0)$$

$$BW_f = BW(1+KA_1)$$

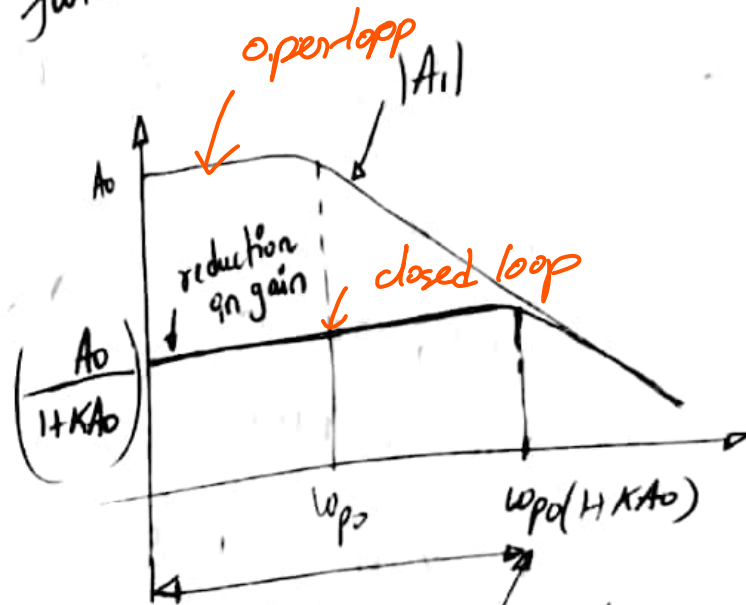

$$BW_{new} = \omega_{p0}(1+KA_0)$$

new pole 6/9

BW with feedback

BW extension with negative feedback.

An amplifier has a mid-band gain of A_1 and a bandwidth of 250 KHz (BW). $K = 4\% = 0.04$

a) If 4% negative feedback is introduced, find the new bandwidth and gain. $(BW_f)_{new}$ (A_f)

b) If the bandwidth is restricted to 1 MHz, find the feedback ratio K'

Soln: Given: $A_1 = 125$, $BW = 250 \text{ KHz}$, $K = 4\% = 0.04$

a) $BW_f = BW(1 + KA_1) = 250 \times 10^3 (1 + 125 \times 0.04)$
 $= 1.5 \text{ MHz}$

Bandwidth with flb $\rightarrow BW_f$

Gain with feedback;

$A_f = \frac{A_1}{1 + KA_1} = \frac{125}{1 + 125 \times 0.04} = 20.83$

gain with flb \leftarrow

$K' \rightarrow$ new feedback ratio

b) $BW_f = (1 + A_1 K) BW$


i.e. $1 \times 10^6 = (1 + 125 K') \times 250 \times 10^3$

i.e. $(1 + 125 K') = \frac{10^6}{250 \times 10^3} = 4$

$K' = \frac{3}{125} = 0.024 = 2.4\%$

Modification of Input and output impedances: (Read) 07

without feedback

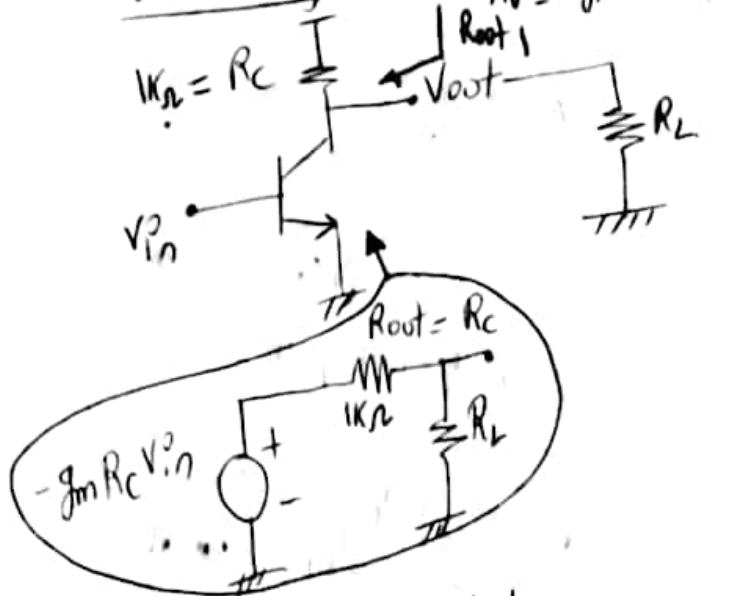


If $R_L = 1k\Omega \Rightarrow$ the gain drops by a factor of 2
 \Rightarrow the output voltage swing drops by a factor of 2.

eg	$A_v = -50$ (w/o load)
	$A_v = -25$ (with $R_L = 1k\Omega$)

- open-loop system

with feedback

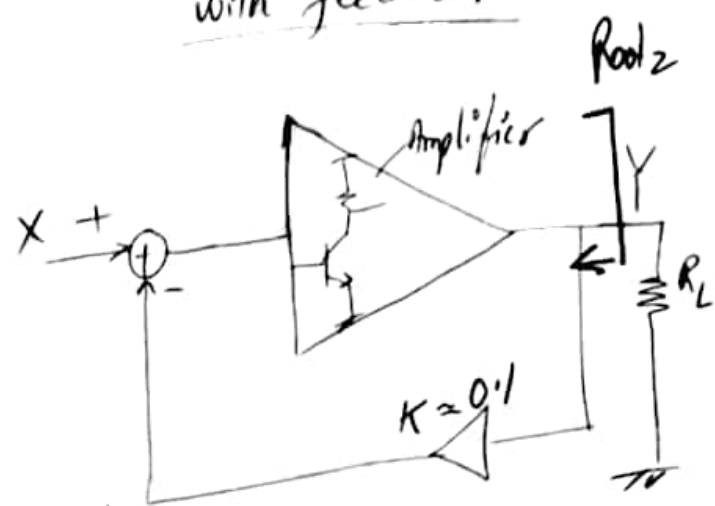

without R_L

$$A_v = \frac{50}{1+5} = 8.33$$


with $R_L = 1k\Omega$,

$$A_v = \frac{25}{1+2.5} = \frac{25}{3.5} = 7.2$$

\rightarrow gain drop by may be by 15%

This circuit is less sensitive to load impedance.

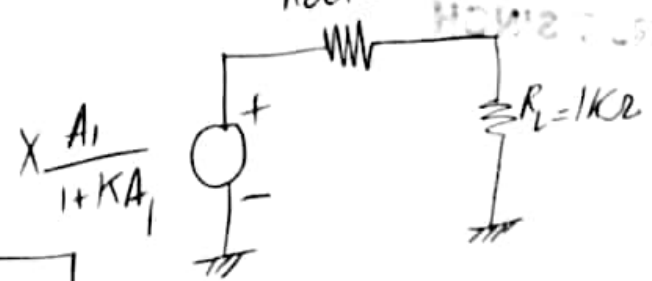- closed-loop system
 $R_{out} = ? < 1k\Omega$





Key point

$R_{out2} < R_{out1}$

o/p impedance of is less than w/o feedback negative feedback

INDERJIT SINGH

④ Higher Linearity : Diffamp.

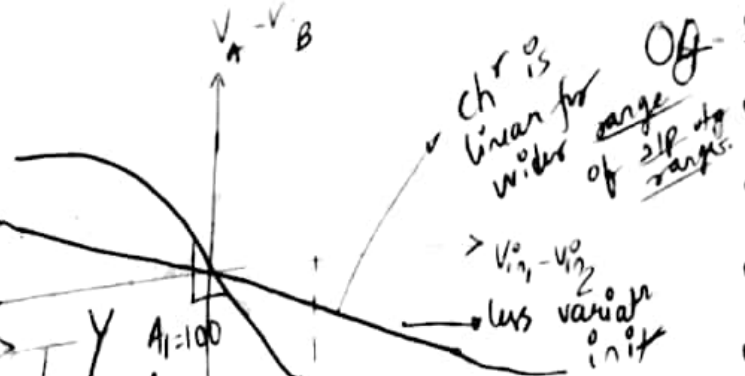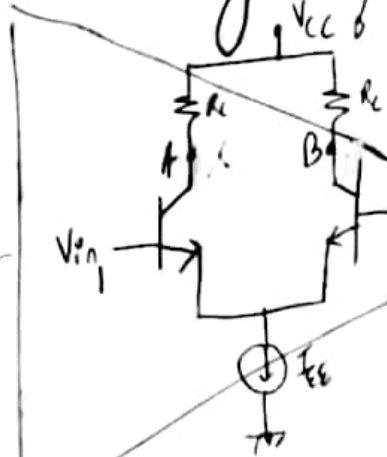

eg $A_1 = 100, A_1 = 50$

$$\text{closed-loop gain} = \frac{A_1}{1 + KA_1} = \frac{100}{11} = 9.1$$

$$\text{closed-loop gain} = \frac{A_1}{1 + KA_1} = \frac{50}{11.5} = 8.33$$

$K \approx 0.1$
 (Closed-loop system)
 have less gain variation

→ Higher Linearity means that characteristics is linear for wider range of 2/p. voltages.