

Hartley Oscillator

Hartley's oscillator:-

$$L_{eq} = L_1 + L_2$$

Amplifier

$$f_o = \frac{1}{2\pi\sqrt{L_{eq}C_3}}$$


Tank circuit

$$f_o = \frac{1}{2\pi\sqrt{L_{eq}C_3}}$$

$$L_{eq} = L_1 + L_2$$

$$|A_v| \geq \left| \frac{L_1}{L_2} \right|$$

LC Tank circuit

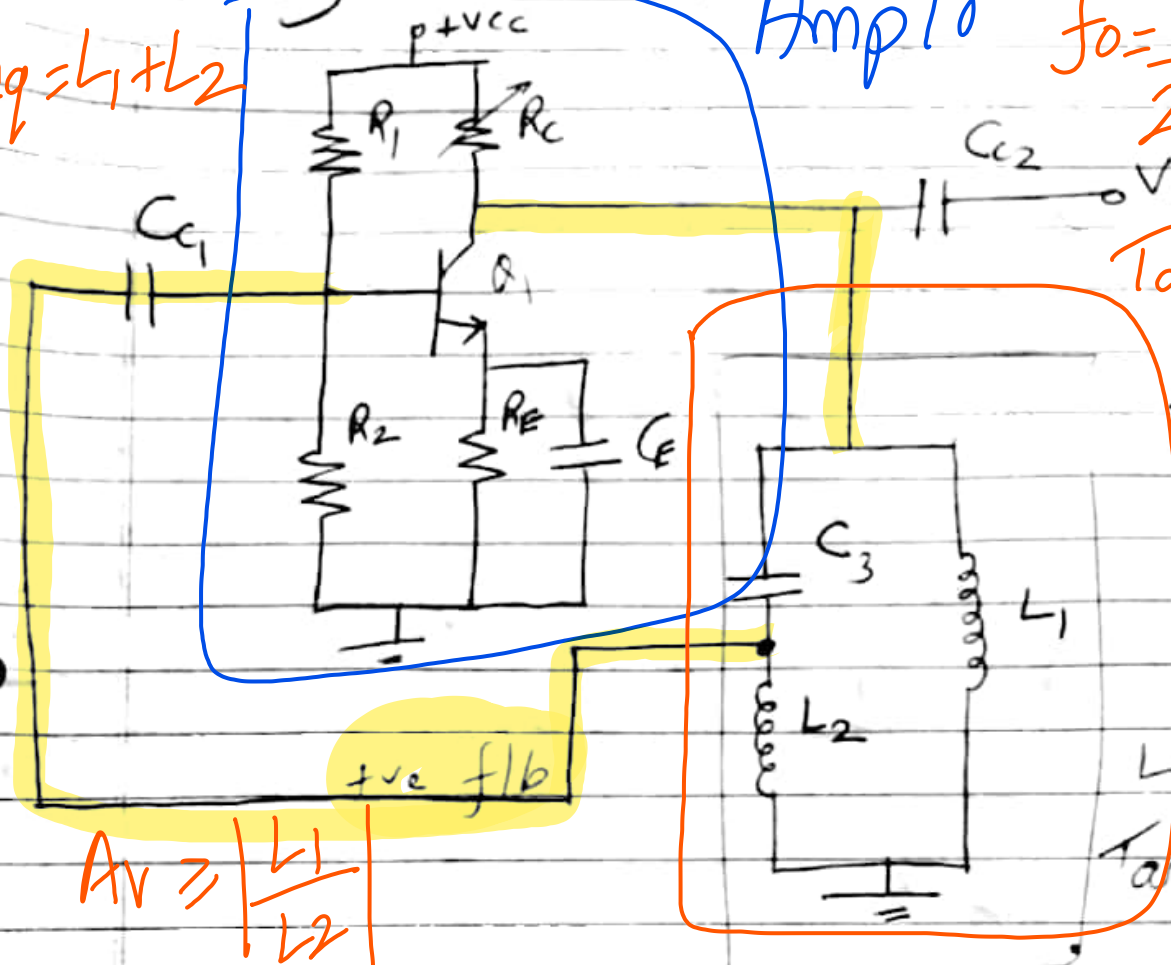

CE amplifier - 180°

LC tank circuit - 180°

Total Phase shift - 0° or 360°

Gain(A_v) of amplifier is adjusted such that $A\beta \geq 1$
 R_1, R_2, R_E - provide dc bias to bjt

LC tank circuit - acts as a resonant filter that passes only desired frequency of oscillations

- Hartley oscillator consists of a single-stage CE BJT amplifier which provides the voltage gain A_v and a phase shift of 180° between its I/P and O/P terminals.
- It consists of a LC tank circuit in the feedback network which provides a 180° phase shift. Thus, the total phase-shift around the circuit is 0° or 360° .
- Capacitor C_2 is coupling capacitor which permits only ac currents to pass to the LC tank ckt. i.e. it blocks dc voltages and currents.
- Capacitor C_1 blocks the dc current reaching the base of Q_1 .
- Resistors R_1 , R_2 and R_E are used to establish dc bias for the BJT.

The LC tank in the feedback network contains ²¹ $(L_1, L_2 \text{ and } C)$; which not only provide a phase shift of 180° , but also it acts as a resonant filter that passes only the desired frequency of oscillations.

• Working:-

1. When the circuit is energized by switching on the dc supply, small oscillations in form of noise voltage appears at the base of Q_1 . This small noise voltage is further amplified by the amplifier and is fed back to LC tank circuit.

2. Small oscillations are produced in the tank ckt, which are again feedback to base of transistor Q_1 & are amplified again.
3. This process continues, till the gain of the amplifier is sufficient to produce sustained oscillations at the resonant frequency of the LC tank circuit.
4. In this way, sustained oscillations are produced due to +ve f/b from the tank circuit.
5. A stable sinusoidal o/p waveform is obtained at the o/p of oscillator by varying the potentiometer R_c [till a sustained oscillations (constant frequency and amplitude) are obtained].

freqⁿ of oscillatⁿ is given by

$$f_0 = \frac{1}{2\pi \sqrt{L_{eq} C_3}}$$

$$L_{eq} = L_1 + L_2$$

$$A_v = \left| \frac{L_1}{L_2} \right|$$

Expression for f_0 :- Tank ckt is responsible for development of noise & f_0 is dependent on tank ckt itself.

Hence, $X_1 = \omega L_1$, $X_2 = \omega L_2$ and $X_3 = -\frac{1}{\omega C_3}$

From eqⁿ (6a),

$$X_1 + X_2 + X_3 = 0$$

$$\omega L_1 + \omega L_2 - \frac{1}{\omega C_3} = 0$$

$$\omega (L_1 + L_2) = \frac{1}{\omega C_3}$$

$$\omega^2 = \frac{1}{(L_1 + L_2) C_3}$$

Let $L_{eq} = L_1 + L_2$

$$f_0 = \frac{1}{2\pi \sqrt{L_{eq} C_3}}$$

w/o mutual inductance

Considering mutual inductance M .

$$L_{eq} = L_1 + L_2 + 2M$$

Inductor not wound on same core
 $M = 0$

- f_o can be varied by varying C_3 .


$$AK = 1 = -A_v \frac{X_2}{X_1} \quad \text{from eq}^n (7)$$

$$A_v = \frac{X_1}{X_2} = \frac{-j\omega L_1}{j\omega L_2}$$

$$|A_v| = \left| \frac{L_1}{L_2} \right| \Rightarrow$$

$$A_v \approx \left| \frac{L_1}{L_2} \right|$$

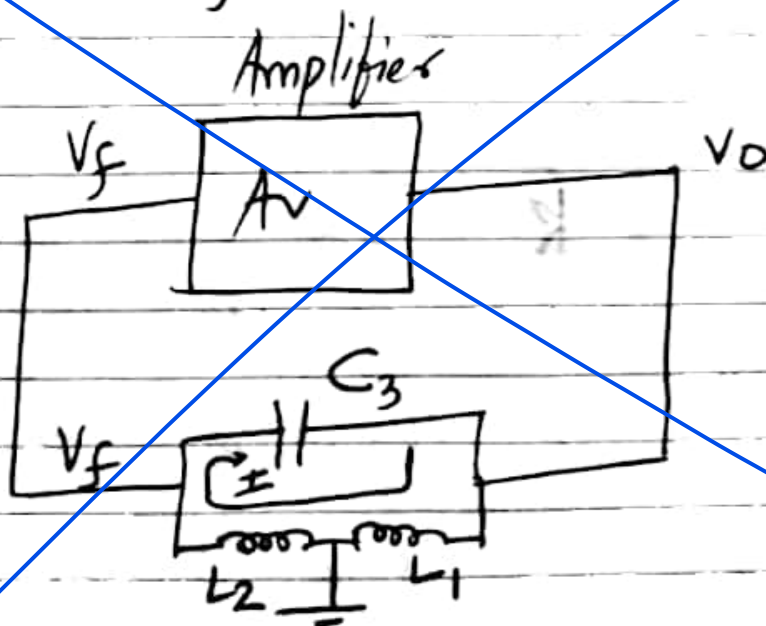→ Conditions for oscillations & Start-up.



K (fb fraction) of LC tank ckt is,

$$K = \frac{V_f}{V_o}$$

- Due to CRT being energized by dc source, the circulating tank current is flowing through L_1 & L_2 .

The vty developed across L_1 is oscillator's o/p vty V_o & vty developed across L_2 is the flb vty V_f

$$K = \frac{V_f}{V_o} = \frac{I X_{L2}}{I X_{L1}} = \frac{X_{L2}}{X_{L1}}$$

$$K = \frac{2\pi f_0 L_2}{2\pi f_0 L_1}$$

$$K = \frac{L_2}{L_1}$$

$$\text{ie } |A_v K| \geq 1$$

$$|A_v| \geq \frac{1}{K} \geq \frac{L_1}{L_2}$$

ie vty gain of ampt $\geq \frac{L_1}{L_2}$ for oscillation's to be self-starting & sustained.

- Advantages:
- 1) It is extremely simple to change the frequency of the oscillations by changing the tuning capacitor C .
 - 2) It can operate over a wide frequency range up to 50 MHz to 500 MHz .
 - 3) It is possible to obtain oscillations at very high frequencies.

- Disadvantages:
- 1) It offers poor frequency stability.
 - 2) This oscillator ckt will have loading effect due to i/p impedance of BJT, thus lowering its resonant frequency value.
 - 3) It works for quality factor $[Q > 10]$

Applications: -

- 1) They have wide variety of applications in Radio (FM) receiver, in function generators, as local oscillator in TV receivers.